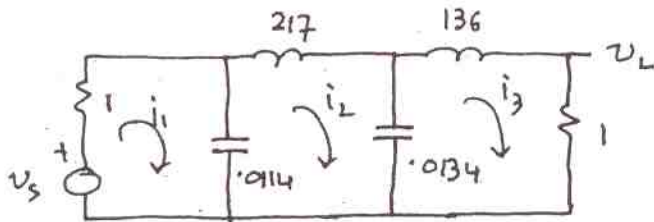


2.1

The network:



The loop matrix eqn:

$$\begin{bmatrix} 1 + \frac{1}{s(0.0114)} & -\frac{1}{s(0.0114)} & 0 \\ -\frac{1}{s(0.0114)} & s(217) + \frac{1}{s(0.0114)} + \frac{1}{s(0.0134)} & -\frac{1}{s(0.0134)} \\ 0 & -\frac{1}{s(0.0134)} & 1 + s(136) + \frac{1}{s(0.0134)} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} v_s \\ 0 \\ 0 \end{bmatrix}$$

The determinant



$$\Delta = \frac{1}{s^2} \left[2588988.93 s^3 + 29512 s^4 + 57308.2 s^2 + 2310976.7 s + 13092.4 \right]$$

$$i_3 = \frac{1}{\Delta} \cdot \frac{v_s}{s^2(0.0114)(0.0134)} \quad ; \quad v_L = i_3 \cdot 1$$

$$\frac{v_L}{v_s} = \frac{6.5462 \times 10^3}{29512 s^4 + 2588988.93 s^3 + 57308.2 s^2 + 2310976.7 s + 13092.4}$$

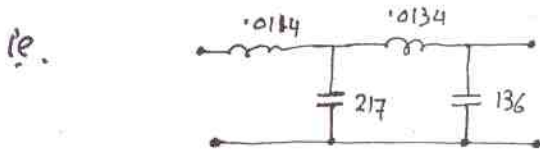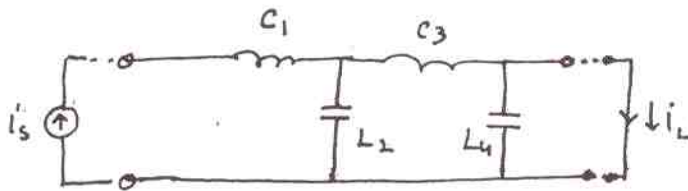2-1 (contd.)

N has to be the dual of the given network



2.2 Use loop system

$$\begin{bmatrix} 1.5\Delta + \frac{1}{1.33\Delta} & -\frac{1}{1.33\Delta} \\ -\frac{1}{1.33\Delta} & 1 + 1.5\Delta + \frac{1}{1.33\Delta} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_s \\ 0 \end{bmatrix}$$

$$\Delta = \frac{1}{\Delta} \cdot (1.5\Delta^2 + 0.75\Delta^3 + 1.504\Delta + 0.7519)$$

$$i_2 = \frac{1}{\Delta} \begin{vmatrix} 1.5\Delta + \frac{1}{1.33\Delta} & v_s \\ -\frac{1}{1.33\Delta} & 0 \end{vmatrix} = \frac{1}{\Delta} \frac{v_s}{1.33\Delta}$$

$$v_o = i_2 \cdot 1 \quad ; \quad \frac{v_o}{v_s} = \frac{1}{1.33} \cdot \frac{1}{0.75\Delta^3 + 1.5\Delta^2 + 1.504\Delta + 0.7519}$$

~~3.6.~~

2.3.


(a) See p. 211 for the derivation to show that the chain matrix of the network is

$$[a]_N = \begin{bmatrix} 1 & 0 \\ 0 & \frac{z_2 z_4}{z_1 z_3} \end{bmatrix}$$

Thus, this corresponds to a GIC with $K_1(s) = 1$
 and $K_2(s) = \frac{z_2 z_4}{z_1 z_3}$ (See Table 2.2)

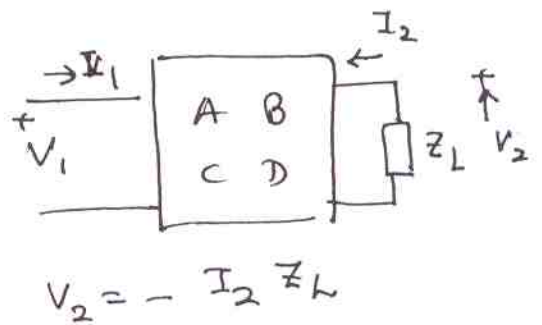(b) $\frac{V_1}{I_1} = \dots$

$$\begin{aligned} Z_{in} &= \frac{V_1}{I_1} = \frac{AV_2 - BI_2}{CV_2 - DI_2} \\ &= \frac{A(-I_2 z_L) - BI_2}{C(-I_2 z_L) - DI_2} \\ &= \frac{AZ_L + B}{Cz_L + D} \end{aligned}$$



(c) $[a]_N$ with given values reduces to $\begin{bmatrix} 1 & 0 \\ 0 & \frac{G}{sC} \end{bmatrix}$


$$\therefore Z_{in} = \frac{R_L}{G/sC} = sCR R_L$$

$\therefore Z_{in} = s(CR)R_L$, an inductance of value $(CR)R_L$.

2.4. Consider the AT with R_3, R_4 resistances as a VCVS of gain $K = 1 + \frac{R_4}{R_3}$. Then apply nodal analysis with the principle of constraint. Convert V_i in series with R_1 to the Norton equivalent of $I_i = V_i/R_1$ in shunt with R_1 before embarking on nodal analysis.

~~2.5-2.8~~
2.6, 2.8 : Proceed using the method of constraints.
Convert input series network to equivalent Norton network before embarking on nodal analysis.

2.5

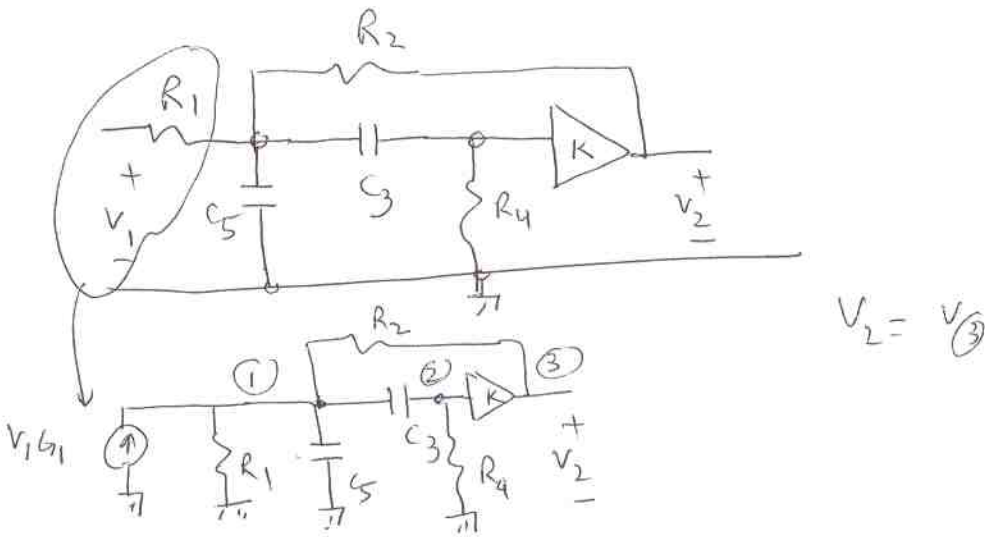

$$\begin{matrix} \textcircled{1} & \textcircled{2} & \textcircled{3} \end{matrix} \begin{bmatrix} G_1 + G_2 + sC_5 + sC_3 & -sC_3 & -G_2 \\ -sC_3 & sC_3 + G_4 & 0 \\ -G_2 & 0 & G_2 \end{bmatrix} \begin{bmatrix} V_{\textcircled{1}} \\ V_{\textcircled{2}} \\ V_{\textcircled{3}} \end{bmatrix} = \begin{bmatrix} I_1 \\ 0 \\ 0 \end{bmatrix} \quad ; I_1 = V_1 G_1$$

$$V_{\textcircled{3}} = K V_{\textcircled{2}}$$

$$\begin{pmatrix} G_1 + G_2 + sC_3 + sC_5 & -sC_3 - KG_2 \\ -sC_3 & sC_3 + G_4 \\ -G_2 & KG_2 \end{pmatrix} \begin{pmatrix} V_{\textcircled{1}} \\ V_{\textcircled{2}} \end{pmatrix}$$

discarded, being the node corresponding to the output of a VCVS

$$\begin{bmatrix} G_1 + G_2 + sC_3 + sC_5 & -sC_3 - KG_2 \\ -sC_3 & sC_3 + G_4 \end{bmatrix} \begin{pmatrix} V_{\textcircled{1}} \\ V_{\textcircled{2}} \end{pmatrix} = \begin{bmatrix} I_1 \\ 0 \end{bmatrix}$$

$$\begin{aligned} \Delta &= (G_1 + G_2 + sC_3 + sC_5)(sC_3 + G_4) - (sC_3 + KG_2)sC_3 \\ &= (G_1 + G_2)G_4 + (G_1 + G_2)sC_3 + \cancel{s^2 C_3^2} + sG_4 C_3 + s^2 C_3 C_5 + sC_5 G_4 \\ &\quad - \cancel{s^2 C_3^2} - KG_2 sC_3 \end{aligned}$$

2.5

$$\Delta = (G_1 + G_2)G_4 + s \left[C_3(G_1 + G_2) + G_2 C_3 + G_4 C_5 - K G_2 C_3 \right] + s^2 C_3 C_5$$

$$V_2 = \frac{1}{\Delta} \begin{vmatrix} G_1 + G_2 + sC_3 + sC_5 & I_1 \\ -sC_3 & 0 \end{vmatrix} = \frac{I_1 s C_3}{\Delta}$$


$$V_3 = K V_2 = \frac{K s C_3}{\Delta} \cdot G_1 V_1 = V_2$$

$$S_o \frac{V_2}{V_1} = \frac{K s G_1 C_3}{s^2 C_3 C_5 + s \left\{ C_3(G_1 + G_2) + C_3(G_4) + C_5 G_4 - K C_3 G_2 \right\} + (G_1 + G_2) G_4}$$

$$\frac{V_2}{V_1} = \frac{K G_1 C_3 s}{s^2 C_3 C_5 + s \left\{ C_3(G_1 + G_2) + C_3 G_2 (1 - K) + C_5 G_4 \right\} + G_4 (G_1 + G_2)}$$

2.6 Follow the method in P 2.5

2.7

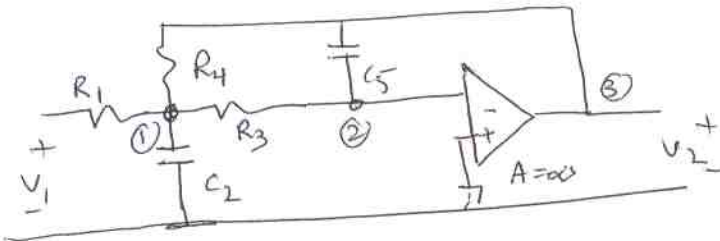

$$\begin{matrix} \textcircled{1} & \textcircled{2} & \textcircled{3} \\ \left[\begin{array}{ccc} G_1 + G_4 + G_3 + sC_2 & -G_3 & -G_4 \\ -G_3 & G_3 + sC_5 & -sC_5 \\ -G_4 & -sC_5 & sC_5 + G_4 \end{array} \right] \begin{bmatrix} V_{\textcircled{1}} \\ V_{\textcircled{2}} \\ V_{\textcircled{3}} \end{bmatrix} = \begin{bmatrix} V_1 G_1 \\ 0 \\ 0 \end{bmatrix} \end{matrix}$$

$\nearrow I_s$

2.7 Since OA gain $\rightarrow \infty$, $V_{(2)} \rightarrow 0$.

Discarding column ~~2~~ for $V_{(2)}$ and then row for $V_{(3)}$

$$\begin{pmatrix} G_1 + G_4 + G_3 + sC_2 & -G_4 \\ -G_3 & -sC_5 \end{pmatrix} \begin{pmatrix} V_{(1)} \\ V_{(3)} \end{pmatrix} = \begin{pmatrix} V_1 G_1 \\ 0 \end{pmatrix}$$


$$\begin{aligned} \Delta &= -sC_5 (G_1 + G_3 + G_4 + sC_2) - G_3 G_4 \\ &= - [s^2 C_2 C_5 + s C_5 (G_1 + G_3 + G_4) + G_3 G_4] \end{aligned}$$

$$V_{(3)} = \frac{1}{\Delta} \cdot \begin{vmatrix} G_1 + G_4 + G_3 + sC_2 & V_1 G_1 \\ -G_3 & 0 \end{vmatrix} = -V_1 \frac{G_1 G_3}{s^2 C_2 C_5 + s C_5 (G_1 + G_3 + G_4) + G_3 G_4}$$

$$\therefore \frac{V_2}{V_1} = \frac{V_{(3)}}{V_1} = - \frac{G_1 G_3}{s^2 C_2 C_5 + s C_5 (G_1 + G_3 + G_4) + G_3 G_4}$$

2.8 Follow on in P2.7

2.9 See ch 5 PS. 29

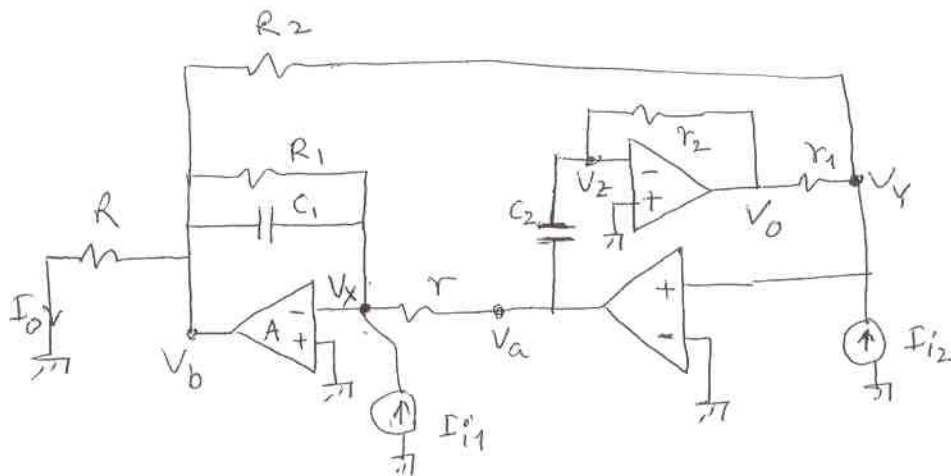

At V_x node: $-I_{i1} + (V_a - V_x)g - (G_1 + sC_1)(V_b - V_x) = 0$

$\Rightarrow I_{i1} = -V_a g + V_x g - (G_1 + sC_1)(V_b + \frac{V_b}{A})$

① $I_{i1} = -V_a g + V_x g - V_b \left(1 + \frac{1}{A}\right)(G_1 + sC_1)$; $V_x = -\frac{V_b}{A}$
 $= -V_a g - V_b \left[\frac{g}{A} + \left(1 + \frac{1}{A}\right)(G_1 + sC_1)\right]$

At V_Y node: $-(V_b - V_Y)g_2 + (V_0 - V_Y)g_1 - I_{i2} = 0$

② $\Rightarrow I_{i2} = -V_b g_2 + V_Y g_2 + V_0 g_1 + V_Y g_1 = -V_b g_2 + V_0 g_1 + \frac{V_a}{A}(g_2 + g_1)$

At V_z node: $+(V_a - V_z)sC_2 + (V_0 - V_z)g_2 = 0$

$\Rightarrow V_a sC_2 - V_z sC_2 + V_0 g_2 - V_z g_2 = 0$ But $V_z = -\frac{V_0}{A}$

$V_a sC_2 + V_0 g_2 + (g_2 + sC_2)\frac{V_0}{A} = 0$

③ $\Rightarrow V_a sC_2 + V_0 \left(g_2 + \frac{g_2 + sC_2}{A}\right) = 0$

From ③ $V_0 = -V_a \frac{sC_2}{g_2 + \frac{g_2 + sC_2}{A}}$

From ① with $I_{i1} = 0$ (assuming only one input source I_{i2})

$V_a = -V_b \left[\frac{1}{A} + \frac{G_1 + sC_1}{g} \left(1 + \frac{1}{A}\right)\right]$

So $V_0 = + V_b \left[\frac{1}{A} + \frac{G_1 + sC_1}{g} \left(1 + \frac{1}{A}\right)\right] \frac{sC_2}{g_2 + \frac{g_2 + sC_2}{A}}$

2.10
cont.

Subst. in (2)

$$\hat{I}_{i2} = -V_b g_2 - V_b g_1 \left[\frac{1}{A} + \frac{g_1 + sC_1}{g} \left(1 + \frac{1}{A} \right) \right] \left(\frac{sC_2}{g_2 + \frac{g_2 + sC_2}{A}} \right)$$

$$- V_b \cdot \left[\frac{1}{A} + \frac{g_1 + sC_1}{g} \left(1 + \frac{1}{A} \right) \right] \frac{g_2 + g_1}{A}$$

$$- \hat{I}_{i2} = V_b \left\{ g_2 + g_1 \left[\frac{1}{A} + \frac{g_1 + sC_1}{g} \left(1 + \frac{1}{A} \right) \right] \left[\frac{sC_2}{g_2 + \frac{g_2 + sC_2}{A}} \right] + \left(\frac{1}{A} + \frac{g_1 + sC_1}{g} \left(1 + \frac{1}{A} \right) \right) \frac{g_2 + g_1}{A} \right\}$$

$$V_b = - \frac{\hat{I}_{i2}}{D}$$

$$\text{where } D = g_2 + g_1 \left[\frac{1}{A} + \frac{g_1 + sC_1}{g} \left(1 + \frac{1}{A} \right) \right] \frac{sC_2}{g_2 + \frac{g_2 + sC_2}{A}} + \left[\frac{1}{A} + \frac{g_1 + sC_1}{g} \left(1 + \frac{1}{A} \right) \right] \frac{g_2 + g_1}{A}$$

$$I_o = V_b G$$



$$\text{So } \frac{I_o}{\hat{I}_{i2}} = - \frac{G}{1/R}$$

$$= - \frac{\frac{1}{R_2} + \frac{1}{r_1} \left[\frac{1}{A} + \frac{\frac{1}{R_1} + sC_1}{\frac{1}{r}} \left(1 + \frac{1}{A} \right) \right] \frac{sC_2}{\frac{1}{r_2} + \frac{\frac{1}{r_2} + sC_2}{A}} + \left(\frac{1}{A} + \frac{\frac{1}{R_1} + sC_1}{\frac{1}{r}} \left(1 + \frac{1}{A} \right) \right) \frac{1/R_2 + 1/r_1}{A}}{1/R}$$


$$\frac{I_o}{\hat{I}_{i2}} = - \frac{\frac{1}{R_2} + \left[\frac{1}{A} + \frac{\frac{1}{R_1} + sC_1}{\frac{1}{r}} \left(1 + \frac{1}{A} \right) \right] \left[\frac{sC_2 / r_1}{\frac{1}{r_2} + \frac{\frac{1}{r_2} + sC_2}{A}} + \frac{1/R_2 + 1/r_1}{A} \right]}{1/R}$$

Multiplying num. & denom. by $\frac{1}{r}$, we get the result shown in the book.


2.11

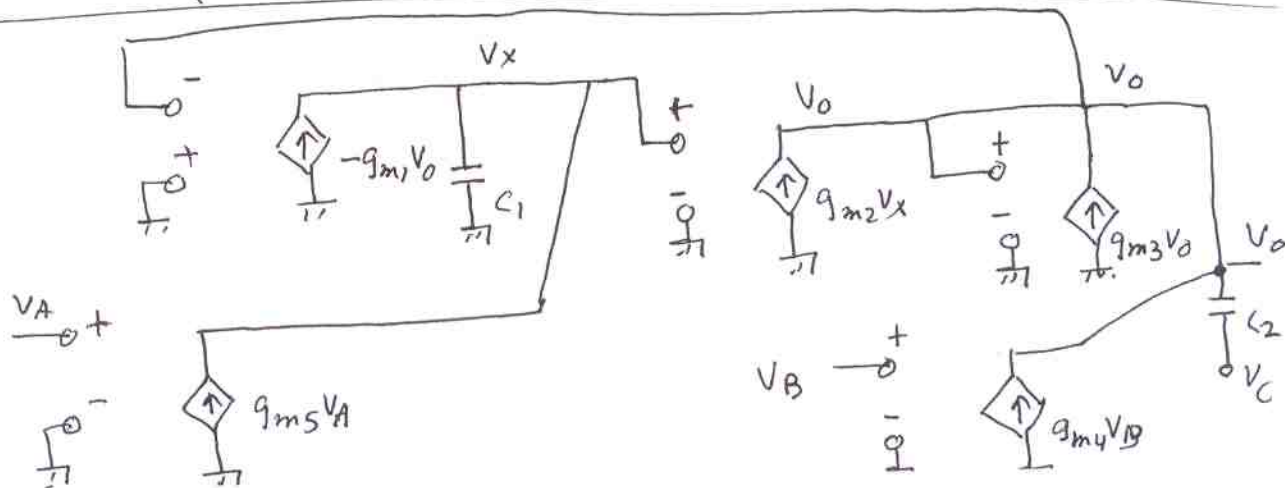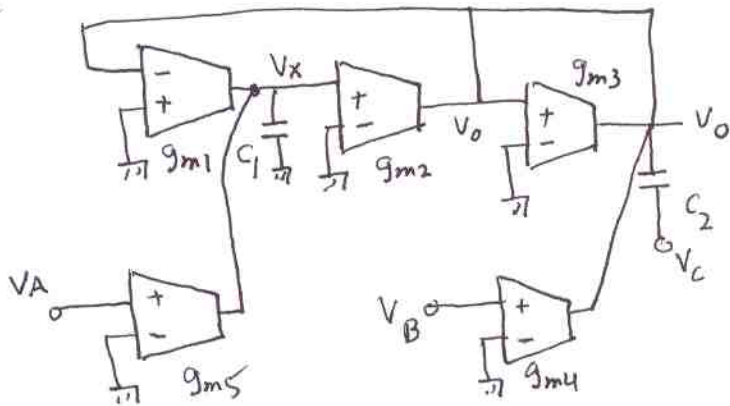


2.12

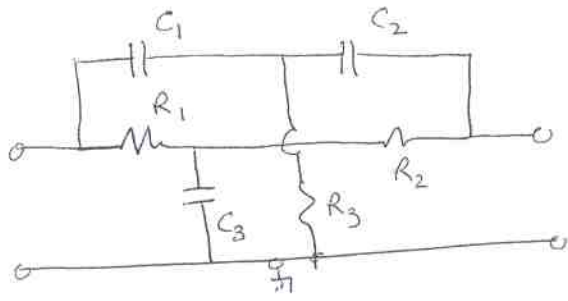

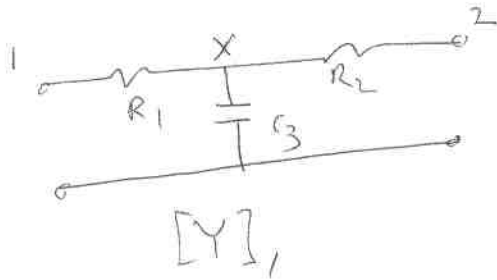The subset of 2-port parameters will be the Y-parameters of



and

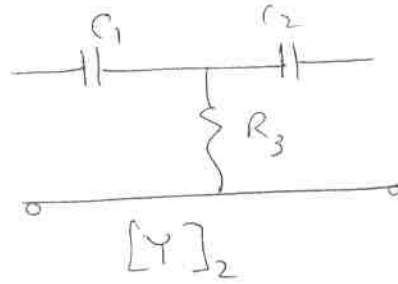

Then overall $[Y] = [Y]_1 + [Y]_2$

For $[Y]_1 \rightarrow \begin{bmatrix} G_1 & -G_1 & 0 \\ -G_1 & G_1 + G_2 + sC_3 & -G_2 \\ 0 & -G_2 & G_2 \end{bmatrix}$. Then suppress node \textcircled{x}


$$\begin{bmatrix} G_1 & 0 \\ 0 & G_2 \end{bmatrix} = \frac{1}{G_1 + G_2 + sC_3} \begin{bmatrix} -G_1 \\ -G_2 \end{bmatrix} \begin{bmatrix} -G_1 & -G_2 \end{bmatrix}$$

$$[Y]_1 \rightarrow \begin{bmatrix} G_1 & 0 \\ 0 & G_2 \end{bmatrix} = \frac{1}{G_1 + G_2 + sC_3} \begin{bmatrix} G_1^2 & G_1 G_2 \\ G_1 G_2 & G_2^2 \end{bmatrix}$$

Continue with $[Y]_2$ in a similar way.

Let $\det [Y] = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$, then VTF is $\frac{V_2}{V_1} \Big|_{I_2=0} = -\frac{Y_{21}}{Y_{22}}$

2.13

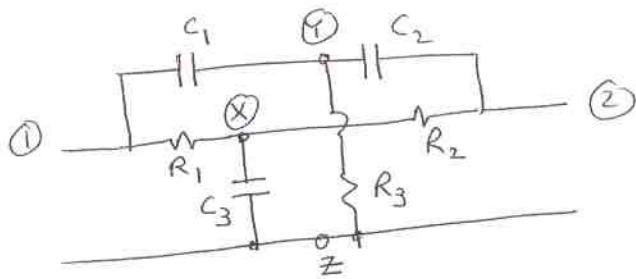

$$\begin{bmatrix} \textcircled{1} & \textcircled{X} & \textcircled{Y} & \textcircled{Z} & \textcircled{2} \\ G_1 + sC_1 & -G_1 & -sC_1 & 0 & 0 \\ -G_1 & G_1 + G_2 + sC_3 & 0 & -sC_3 & -G_2 \\ -sC_1 & 0 & sC_1 + sC_2 + G_3 & -G_3 & -sC_2 \\ 0 & -sC_3 & -G_3 & G_3 + sG_3 & 0 \\ 0 & -G_2 & -sC_2 & 0 & G_2 + sC_2 \end{bmatrix}$$

If \textcircled{Z} is grounded, discard row & column for \textcircled{Z}

$$\begin{bmatrix} \textcircled{1} & \textcircled{X} & \textcircled{Y} & \textcircled{2} \\ G_1 + sC_1 & -G_1 & -sC_1 & 0 \\ -G_1 & G_1 + G_2 + sC_3 & 0 & -G_2 \\ -sC_1 & 0 & sG_1 + sG_2 + G_3 & -sC_2 \\ 0 & -G_2 & -sC_2 & G_2 + sC_2 \end{bmatrix}$$

Suppress \textcircled{X}

$$\begin{bmatrix} G_1 + sC_1 & -sC_1 & 0 \\ -sC_1 & sG_1 + sG_2 + G_3 & -sC_2 \\ 0 & -sC_2 & G_2 + sC_2 \end{bmatrix} - \frac{1}{G_1 + G_2 + sC_3} \begin{bmatrix} -G_1 \\ 0 \\ -G_2 \end{bmatrix} \begin{bmatrix} -G_1 & 0 & -G_2 \end{bmatrix}$$

$$= \begin{bmatrix} G_1 + sC_1 & -sC_1 & 0 \\ -sC_1 & sG_1 + sC_2 + G_3 & -sC_2 \\ 0 & -sC_2 & G_2 + sC_2 \end{bmatrix} - \frac{1}{G_1 + G_2 + sC_3} \begin{bmatrix} G_1^2 & 0 & G_1 G_2 \\ 0 & 0 & 0 \\ G_1 G_2 & 0 & G_2^2 \end{bmatrix}$$

2,13
(contd.)

$$\rightarrow [Y] \begin{matrix} \textcircled{1} & & \textcircled{2} \\ \left[\begin{array}{c} G_1 + sC_1 - \frac{G_1^2}{G_1 + G_2 + sC_3} \\ -sC_1 \\ -\frac{G_1 G_2}{G_1 + G_2 + sC_3} \end{array} \right] & \begin{matrix} -sC_1 \\ sG_1 + sC_2 + G_3 \\ -sC_2 \end{matrix} & \left[\begin{array}{c} -\frac{G_1 G_2}{G_1 + G_2 + sC_3} \\ -sC_2 \\ G_2 + sC_2 - \frac{G_2^2}{G_1 + G_2 + sC_3} \end{array} \right] \end{matrix}$$

Suppress $\textcircled{2}$

$$\left[\begin{array}{c} G_1 + sC_1 - \frac{G_1^2}{G_1 + G_2 + sC_3} \\ -\frac{G_1 G_2}{G_1 + G_2 + sC_3} \end{array} \right] - \frac{1}{sC_1 + sC_2 + G_3} \begin{bmatrix} -sC_1 \\ -sC_2 \end{bmatrix} \begin{bmatrix} -sC_1 & -sC_2 \end{bmatrix}$$

$$= \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}, \text{ where}$$


$$Y_{11} = \frac{G_1 G_2 + s(G_1 G_3 + G_1 C_1 + G_2 C_1) + s^2 C_1 C_3}{G_1 + G_2 + sC_3} - \frac{s^2 C_1^2}{s(C_1 + C_2) + G_3}$$

etc:

Voltage transfer function $-Y_{21}/Y_{22}$

$$= \frac{s^3 C_1 C_2 C_3 + s^2 (C_1 C_2 G_1 + C_1 C_2 G_2) + (C_1 G_1 G_2 + G_2 G_1 G_2) s + G_1 G_2 G_3}{s^3 G_1 G_2 G_3 + s^2 (G_2 G_2 G_3 + G_1 G_1 G_2 + G_2 G_1 G_3 + G_2 C_1 C_2 + G_3 G_2 G_3) + s(G_1 G_2 C_1 + G_1 G_2 C_2 + G_1 G_3 C_2 + G_2 G_3 C_3 + G_2 G_3 C_2) + G_1 G_2 G_3}$$

2.14

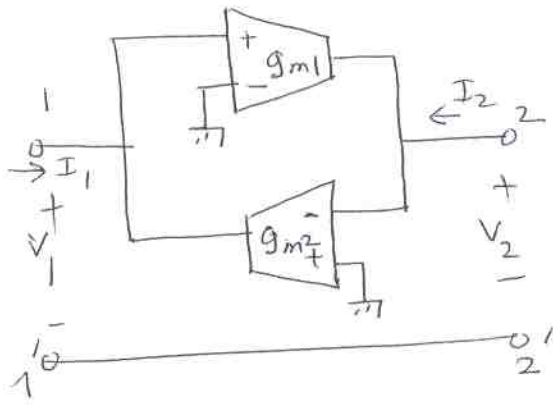

$$I_2 = -g_{m1} V_1$$

$$I_1 = g_{m2} V_2$$

Thus

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{g_{m2}} \\ -g_{m1} & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$$

(a) From Table 2.2, the $[A]$ matrix is

$$\begin{bmatrix} 0 & -\frac{1}{g_{m2}} \\ -g_{m1} & 0 \end{bmatrix} \rightarrow \begin{bmatrix} 0 & \frac{1}{g_1} \\ g_2 & 0 \end{bmatrix}; \text{ Then } \frac{g_2}{g_1} = \frac{g_{m1}}{g_{m2}} > 0.$$

So it is a PII (positive impedance inverter).


(b) With Z_L connected at (2), $V_2 = -I_2 Z_L = +g_{m1} V_1 Z_L$

$$\text{But } V_2 = \frac{I_1}{g_{m2}} = +g_{m1} V_1 Z_L. \text{ Then } \frac{V_1}{I_1} = \frac{Z_L}{g_{m1} g_{m2}} = Z_1$$

(c) If $Z_L = \frac{1}{sC}$; $Z_1 = Z_{in} = \frac{sC}{g_{m1} g_{m2}} \rightarrow \text{inductor } L = \frac{C}{g_{m1} g_{m2}}$

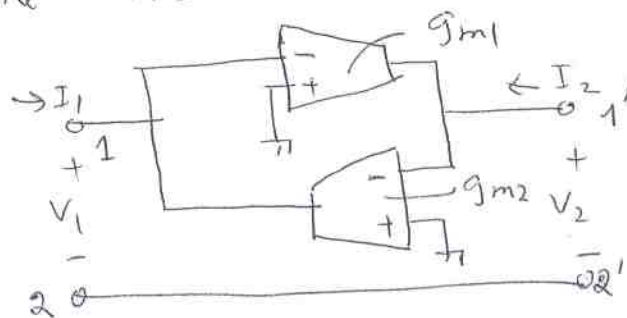
2.15

In Table 2.2, we see $g_2/g_1 < 0$ produces an NII. Thus in problem P2.14, g_{m1} and g_{m2} should be such that $-g_{m1}$ and $-\frac{1}{g_{m2}}$ be of opposite sign. This can be easily achieved by reversing the input terminals of one of the OTAs. Thus



is a possible NII system.

2.16.

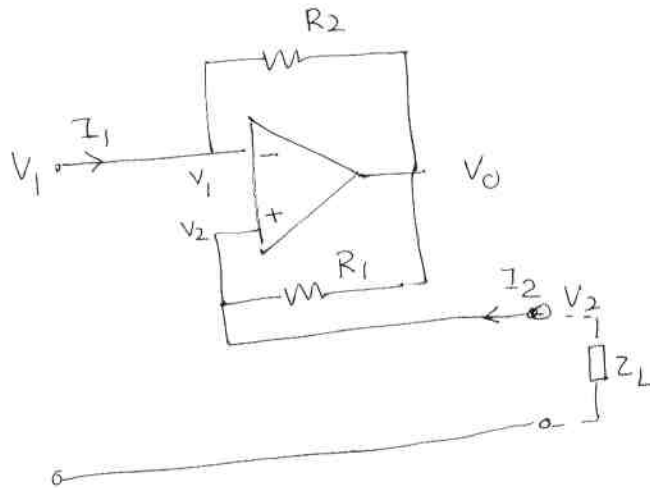

$$V_1 - V_2 = 0 \quad \therefore V_1 = V_2$$

$$V_1 - V_0 = I_1 R_2, \quad V_2 - V_0 = I_2 R_1$$

$$\therefore V_1 - V_0 = I_1 R_2 = I_2 R_1$$

$$I_2 = + \frac{R_2}{R_1} I_1$$

$$\Rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & -\frac{R_2}{R_1} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\therefore [a] = \begin{bmatrix} 1 & 0 \\ 0 & -R_2/R_1 \end{bmatrix}, \text{ which is the } [a] \text{ of a CNIC (Page 17)}$$

Hence The given network represents a CNIC if Z_L is connected at port 2, $V_2 = -I_2 Z_L$

$$\therefore V_2 = -\frac{R_2}{R_1} Z_L I_1$$

Since $V_1 = V_2$, we get $V_1 = -\left(\frac{R_2}{R_1}\right) Z_L I_1$

$$\text{or } Z_{in} = \frac{V_1}{I_1} = -\left(\frac{R_2}{R_1}\right) Z_L$$

Hence Z_{in} corresponds to a negative impedance.

2.17: Assume $A \rightarrow \infty$ and work out.