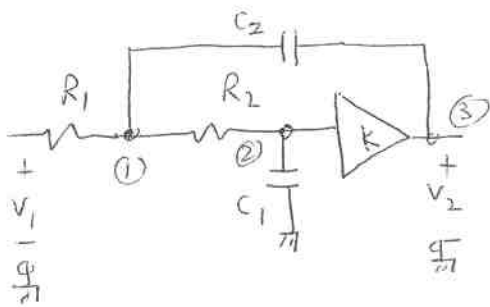


3.1

(a)



$$\begin{bmatrix} G_1 + G_2 + sC_2 & -G_2 & -sC_2 \\ -G_2 & G_2 + sC_1 & 0 \\ -sC_2 & 0 & sC_2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$\therefore V_3 = K V_2$

$$\begin{bmatrix} G_1 + G_2 + sC_2 & -G_2 - KsC_2 \\ -G_2 & G_2 + sC_1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$= \begin{bmatrix} V_1 G_1 \\ 0 \\ 0 \end{bmatrix}$$

output node of VCS

$$\Delta = \frac{-sC_2}{0 + KsC_2} = (G_1 + G_2 + sC_2)(G_2 + sC_1) - (G_2 + sK C_2) G_2$$

$$= s^2 C_1 C_2 + \{C_1 G_1 + C_1 G_2 + (1-K) C_2 G_2\} s + G_1 G_2$$

$$V_2 = \frac{1}{\Delta} \begin{vmatrix} G_1 + G_2 + sC_2 & 0 \\ -G_2 & 0 \end{vmatrix} = + V_1 \frac{G_1 G_2}{\Delta}$$

Using the values given

$$\frac{V_2}{V_1} = \frac{1.3}{s^2 \cdot 1 + \{3 + 1 + (1-2)\} s + 3} = \frac{3}{s^2 + 3s + 3}$$


$\frac{V_2}{V_1} = K \frac{V_0}{V_1}$   $\omega_p = \sqrt{3}$ ,  $\frac{\omega_p}{\omega_p} = 3$ ;  $\omega_p = \frac{\omega_p}{3} = \frac{1}{\sqrt{3}}$

3.1(b)  $s \rightarrow \frac{1}{s}$ , The HP function becomes

$$\frac{6}{s^2 + 3s + 3} \leftrightarrow \frac{6s^2}{3s^2 + 3s + 1}$$

LP  $\leftrightarrow$  HP, subst.  $K=2$

The filter structure will be

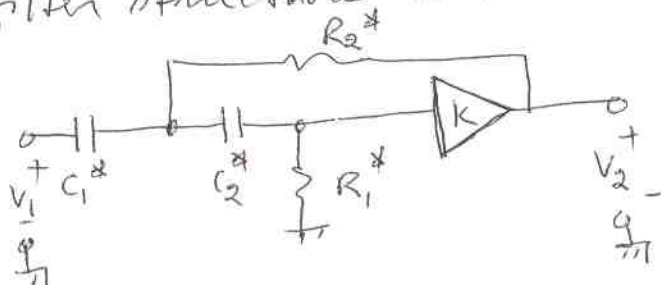


$$C_1^* = \frac{1}{3}$$

$$C_2^* = 1$$

$$R_1^* = R_2^* = 1$$

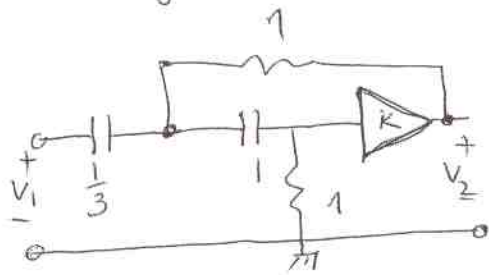3.1 (c) By impedance transformation the TF does not change. So it is:




$$\frac{6s^2}{3s^2 + 3s + 1}$$

$\frac{1}{\frac{1}{3}} \rightarrow \frac{Z(s)}{3s} \rightarrow \frac{1}{3s^2}$   
 $\frac{1}{1} \rightarrow \frac{1}{s} \rightarrow \frac{1}{s^2}$   
 $\frac{1}{1} \rightarrow 1 \rightarrow \frac{1}{s}$   
 $\frac{1}{1} \rightarrow 1 \rightarrow \frac{1}{s}$

The capacitances change to frequency dependent reactances (negative resistance) and resistors change to capacitances.

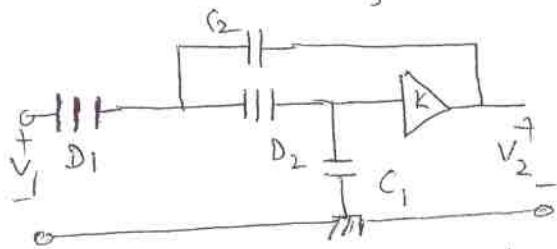Letting  $D_1(s) = \frac{1}{3s^2} \rightarrow \frac{1}{D_1}$   
 $D_2(s) = \frac{1}{s^2} \rightarrow \frac{1}{D_2}$



$$H(s) = \frac{2s^2}{s^2 + s + \frac{1}{3}}$$


$\omega_p \uparrow$        $\omega_p^2 \uparrow$   
 $\frac{\omega_p}{Q_p}$        $\frac{1}{Q_p}$

$$\omega_p = \frac{1}{\sqrt{3}}$$


$$\frac{\omega_p}{Q_p} = 1 ; Q_p = \frac{\omega_p}{1} = \frac{1}{\sqrt{3}}$$

3(a)  $\omega_p = \frac{1}{\sqrt{3}} ; Q_p = \frac{1}{\sqrt{3}}$

3.2

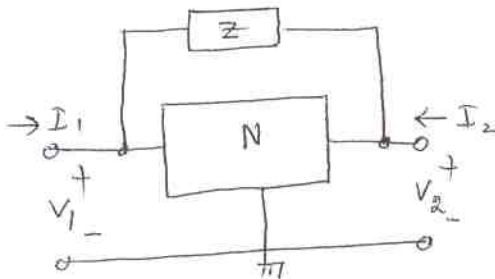

(a)

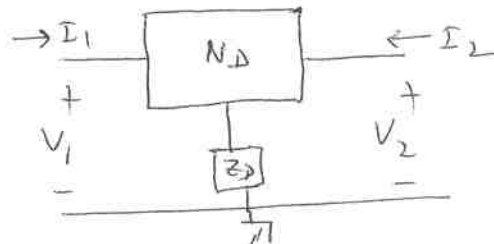

(b)

$$Z \cdot Z_D = f(s) ; Z = \frac{f(s)}{Z_D} \quad \& \quad Z_D = \frac{f(s)}{Z}$$

$$[N] \cdot [N_D] = f(s)$$


Then

$$\frac{3.2}{\text{Cont.}} \quad [a]_N = \begin{bmatrix} A & B \\ C & D \end{bmatrix}; \quad [a]_{N_D} = \begin{bmatrix} D & C f(s) \\ \frac{B}{f(s)} & A \end{bmatrix}$$

In (a),  $[N]$  and  $Z$  are in parallel.

$$\begin{aligned} \text{So } [Y]_{N \parallel Z} &= [Y]_N + [Y]_Z = [Y]_N + \begin{bmatrix} \frac{1}{Z} & -\frac{1}{Z} \\ -\frac{1}{Z} & \frac{1}{Z} \end{bmatrix} \\ &= \begin{bmatrix} \frac{D}{B} & -\frac{A_a}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix} + \begin{bmatrix} \frac{1}{Z} & -\frac{1}{Z} \\ -\frac{1}{Z} & \frac{1}{Z} \end{bmatrix} \quad \underline{\Delta_a = AD - BC} \end{aligned}$$
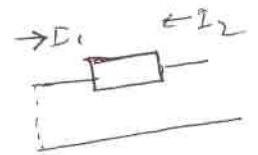
$$= \begin{bmatrix} \left(\frac{D}{B} + \frac{1}{Z}\right) & -\left(\frac{A_a}{B} + \frac{1}{Z}\right) \\ -\left(\frac{1}{B} + \frac{1}{Z}\right) & \left(\frac{A}{B} + \frac{1}{Z}\right) \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$



$$\text{Then } [a]_{N \parallel Z} = \begin{bmatrix} -\frac{Y_{22}}{Y_{21}} & -\frac{1}{Y_{21}} \\ -\frac{\Delta_y}{Y_{21}} & -\frac{Y_{11}}{Y_{21}} \end{bmatrix}, \quad \Delta_y = Y_{11}Y_{22} - Y_{12}Y_{21}$$

For Fig(b), the two networks are in series

$$\text{So } [Z]_{N_D + Z_D} = \begin{bmatrix} \frac{A_D}{C_D} & \frac{\Delta_{aD}}{C_D} \\ \frac{1}{C_D} & \frac{D_D}{C_D} \end{bmatrix} + \begin{bmatrix} Z_D & -Z_D \\ -Z_D & Z_D \end{bmatrix}$$

note:  
 $\Delta_{aD} \equiv \Delta_a$   
 $= AD - BC$

$$= \begin{bmatrix} \frac{D f(s)}{B} & \frac{\Delta_a \cdot f(s)}{B} \\ \frac{f(s)}{B} & \frac{A f(s)}{B} \end{bmatrix} + \begin{bmatrix} Z_D & Z_D \\ Z_D & Z_D \end{bmatrix} \quad Z_D = \frac{f}{Z}$$

$$= \begin{bmatrix} \frac{D}{B} f(s) + Z_D & \frac{\Delta_a}{B} f(s) + Z_D \\ \frac{f(s)}{B} + Z_D & \frac{A}{B} f(s) + Z_D \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

3.2 / ~~word~~. Then  $[a]_{N_D + Z_D} = \begin{bmatrix} \frac{z_{11}}{z_{21}} & \frac{\Delta z}{z_{21}} \\ \frac{1}{z_{21}} & \frac{z_{22}}{z_{21}} \end{bmatrix}$

$$\Delta z = z_{11} z_{22} - z_{21} z_{12}$$

Using the original notations:

Let  $AP_{ij} = (i, j)$  element of  $N^{\parallel} z$

$AS_{ij} = (i, j)$  element of  $N_D + Z_D$

$$AP_{11} = \frac{Az + B}{z + B}$$

$$AP_{12} = \frac{Bz}{z + B}$$

$$AP_{21} = \frac{DzA + B\Delta + AB - zA_a - BA_a - B}{B(z + B)}$$

$$AP_{22} = \frac{Dz + B}{z + B}$$

---


$$AS_{11} = \frac{Dz + B}{z + B} ; AS_{12} = \frac{(zA) + B\Delta + AB - zA_a - BA_a - B}{B(z + B)}$$


$$AS_{21} = \frac{Bz}{f(z + B)} ; AS_{22} = \frac{Az + B}{z + B}$$

Clearly,  $AS_{11} = AP_{22} ; AS_{12} = f AP_{21} ; AS_{21} = \frac{1}{f} AP_{12}$


And  $AS_{22} = AP_{11}$

Hence  $[N_a + z_a]$  is dual of  $[N^{\parallel} z]$

3.3

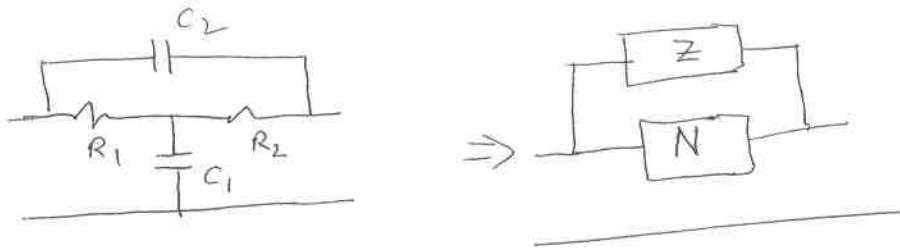

$Z \rightarrow$  ; in shunt with

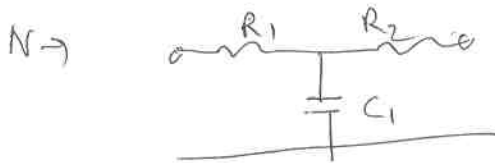

For , the Y-matrix is:  $\begin{bmatrix} sC_2 & -sC_2 \\ -sC_2 & sC_2 \end{bmatrix}$

For , the Y-matrix is calculated as:

$$\begin{bmatrix} \textcircled{1} & \textcircled{2} & \textcircled{3} \\ g_1 & -g_1 & 0 \\ -g_1 & g_1 + g_2 + sC_1 & -g_2 \\ 0 & -g_2 & g_2 \end{bmatrix} \rightarrow \begin{bmatrix} g_1 & 0 \\ 0 & g_2 \end{bmatrix} - \frac{1}{g_1 + g_2 + sC_1} \begin{bmatrix} -g_1 \\ -g_2 \end{bmatrix} \begin{bmatrix} -g_1 & -g_2 \end{bmatrix}$$

$2 \times 1$        $1 \times 2$

$$= \begin{bmatrix} g_1 & 0 \\ 0 & g_2 \end{bmatrix} - \begin{bmatrix} g_1^2 & g_1 g_2 \\ g_1 g_2 & g_2^2 \end{bmatrix} \frac{1}{(g_1 + g_2 + sC_1)}$$

$$= \begin{bmatrix} g_1 - \frac{g_1^2}{g_1 + g_2 + sC_1} & -\frac{g_1 g_2}{g_1 + g_2 + sC_1} \\ -\frac{g_1 g_2}{g_1 + g_2 + sC_1} & g_2 - \frac{g_2^2}{g_1 + g_2 + sC_1} \end{bmatrix}$$

$$= \begin{bmatrix} \frac{g_1(g_2 + sC_1)}{g_1 + g_2 + sC_1} & -\frac{g_1 g_2}{g_1 + g_2 + sC_1} \\ -\frac{g_1 g_2}{g_1 + g_2 + sC_1} & \frac{g_2(g_1 + sC_1)}{g_1 + g_2 + sC_1} \end{bmatrix}$$

3.3  
(cont.)

$$\text{Let } Y_N = \begin{bmatrix} Y_{N11} & Y_{N12} \\ Y_{N21} & Y_{N22} \end{bmatrix}$$

$$\text{with } Y_{N11} = \frac{G_1(G_2 + SC_1)}{G_1 + G_2 + SC_1} ; Y_{N12} = - \frac{G_1 G_2}{G_1 + G_2 + SC_1}$$

$$Y_{N21} = - \frac{G_1 G_2}{G_1 + G_2 + SC_1} ; Y_{N22} = \frac{G_2(G_1 + SC_1)}{G_1 + G_2 + SC_1}$$

$$\text{Then } [a]_N = \begin{bmatrix} - \frac{Y_{N22}}{Y_{N21}} & \frac{-1}{Y_{N21}} \\ - \frac{\Delta Y}{Y_{N21}} & \frac{-Y_{N11}}{Y_{N21}} \end{bmatrix}$$

$$[a]_N = \begin{bmatrix} \frac{G_1 + SC_1}{G_1} & \frac{G_1 + G_2 + SC_1}{G_1 G_2} \\ SC_1 & \frac{G_2 + SC_1}{G_2} \end{bmatrix}$$



$$[a]_{ND} \rightarrow \begin{bmatrix} D & C f(s) \\ \frac{B}{f(s)} & A \end{bmatrix}$$

$$[a]_{ND} = \begin{bmatrix} \frac{G_2 + SC_1}{G_2} & C_1 \\ \frac{(G_1 + G_2 + SC_1) S}{G_1 G_2} & \frac{G_1 + SC_1}{G_1} \end{bmatrix} \text{ using } f(s) = \frac{1}{s}$$

$$[z]_{ND} = \begin{bmatrix} \frac{(G_2 + SC_1) G_1}{(G_1 + G_2 + SC_1) S} & \frac{G_1 G_2}{(G_1 + G_2 + SC_1) S} \\ \frac{G_1 G_2}{(G_1 + G_2 + SC_1) S} & \frac{(G_1 + SC_1) G_2}{(G_1 + G_2 + SC_1) S} \end{bmatrix}$$

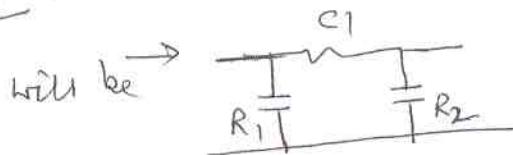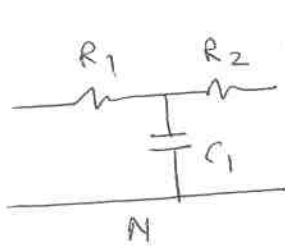3.3  
Contd.

Adopting the method of element by element substitution for capacitive dual, we can infer that the capacitive dual of



$N_D \leftarrow$  capacitive dual

For  $N_D$  we can find  $Z_{11} = \frac{1}{sR_1} \parallel \left[ C_1 + \frac{1}{sR_2} \right] = \frac{G_1}{s} \parallel \left[ C_1 + \frac{G_2}{s} \right]$

$$Z_{11} = \frac{G_1(G_2 + sC_1)}{(G_1 + G_2 + sC_1)s} ; Z_{22} = \frac{G_2(G_1 + sC_1)}{(G_1 + G_2 + sC_1)s}$$

} These are same as the z-elements of  $[Z]_{N_D}$

$$Z_{12} = Z_{21} = \frac{G_1 G_2}{(G_1 + G_2 + sC_1)s}$$



For  $\frac{1}{C_2} \Rightarrow sC_2 = Y = \begin{bmatrix} sC_2 & -sC_2 \\ -sC_2 & sC_2 \end{bmatrix}$

$$[a]_{z = \frac{1}{sC_2}} = \begin{bmatrix} -\frac{sC_2}{-sC_2} & \frac{1}{sC_2} \\ 0 & -\frac{sC_2}{-sC_2} \end{bmatrix} = \begin{bmatrix} 1 & \frac{1}{sC_2} \\ 0 & 1 \end{bmatrix}$$

$$[a]_D = \begin{bmatrix} 1 & 0 \cdot f(s) \\ \frac{1}{sC_2} \cdot \frac{1}{f(s)} & 1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{C_2} & 1 \end{bmatrix}, \text{ using } f(s) = \frac{1}{s}$$

$$[Z]_D = \begin{bmatrix} C_2 & C_2 \\ C_2 & C_2 \end{bmatrix} \rightarrow \text{a resistance of value } C_2$$

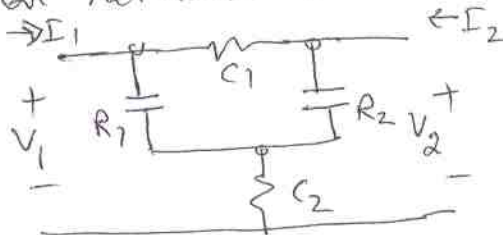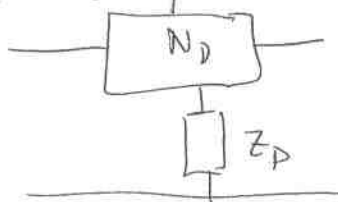Hence the capacitive dual network will be



3.4.

(a)  $[a]_{VCCS} = \begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix}$ ,  $[a]_{r_m} = \begin{bmatrix} 1 & r_m \\ 0 & 1 \end{bmatrix}$

$[a]_{CCCS} = \begin{bmatrix} 0 & 0 \\ 0 & 1 \end{bmatrix}$

$\therefore$  The chain matrix of the overall network is,

$[a]_N = \begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & r_m \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & 0 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 0 & r_m \\ 0 & 0 \end{bmatrix}$

This corresponds to a VCCS with a transadmittance  $g_m = 1/r_m$ .

(b) Using Theorem 3.2, the chain matrix of dual of  $N$  is

$[a]_{N_D} = \begin{bmatrix} 0 & 0 \\ \frac{r_m}{r_m r_n} & 0 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 1/r_n & 0 \end{bmatrix}$

$\therefore$  The dual of  $N$ ,  $N_D$  is nothing but a CCVS of transresistance  $r_n$ .

Let us now see what the different subnetworks.

For the VCVS, the chain matrix of dual is  $\begin{bmatrix} 0 & 0 \\ 0 & 1 \end{bmatrix}$  which is a unity gain CCVS.



3.4  
(Contd.)

For the series resistor  $r_m$ , the dual element's chain matrix is

$$\begin{bmatrix} 1 & 0 \\ \frac{r_m}{r_m r_n} & 1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{r_n} & 1 \end{bmatrix}$$


This corresponds to a shunt resistor of value  $\frac{1}{r_n}$

Finally, the dual of the cccs has the chain matrix

$$\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix}$$

which corresponds to a vcvS of unity gain.

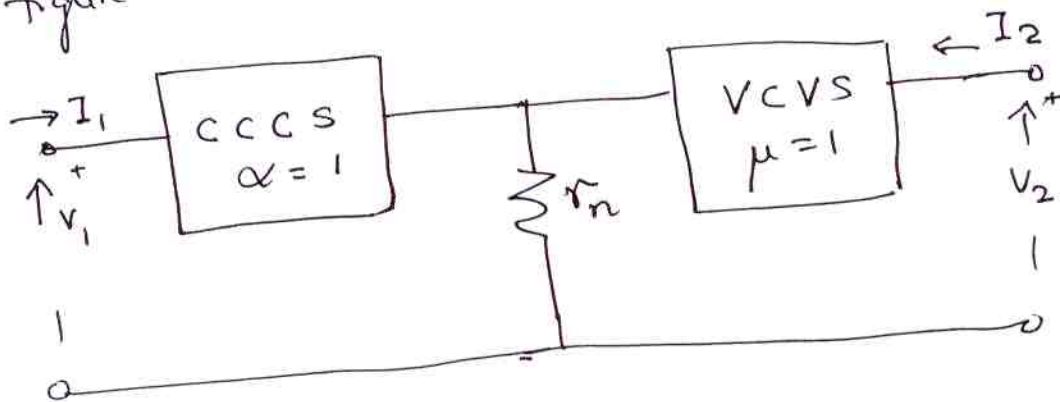Thus, from Theorem 3.1, we see that a ccvs of transresistance  $r_n$  can be realized as a cascade combination of a <sup>unity gain</sup> cccs, a shunt resistor of value  $r_n$  and a vcvS of unity gain, as shown in the figure below.



3.4  
(contd.)

(c) The chain matrix of the <sup>reversed network</sup> transposed is given by

$$[a]_{N^T} = \begin{bmatrix} D & B \\ C & A \end{bmatrix}$$

$$\text{if } [a]_N = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

Since  $N$  is a VCCS of transadmittance  $Y_{tm}$  with a chain matrix  $\begin{bmatrix} 0 & r_m \\ 0 & 0 \end{bmatrix}$ , its transposed reverse has the chain matrix  $\begin{bmatrix} 0 & r_m \\ 0 & 0 \end{bmatrix}$ . This is nothing but a VCCS. Thus the ~~chain~~ transpose of a VCCS is itself with its input and output reverse

$$(d) [a]_{N_D} = \begin{bmatrix} 0 & 0 \\ Y_{rn} & 0 \end{bmatrix}$$

$\therefore$  The chain matrix of  $[N_D]^R$  is given by

$$\begin{bmatrix} 0 & 0 \\ Y_{rn} & 0 \end{bmatrix}$$

which is a CCVS of transresistance  $r_n$ .

~~Hence, the transposed reverse network of a~~  
Hence, the transpose of a CCVS is itself with its input and output ports reversed.

3.5

$$(a) [a]_{VCCS} = \begin{bmatrix} 0 & 1/g_m \\ 0 & 0 \end{bmatrix}$$

$$[a]_{CCVS} = \begin{bmatrix} 0 & 0 \\ 1/r_n & 0 \end{bmatrix}$$

$$\therefore [a]_N = \begin{bmatrix} 0 & 1/g_m \\ 0 & 0 \end{bmatrix} \begin{bmatrix} 0 & 0 \\ 1/r_n & 0 \end{bmatrix} = \begin{bmatrix} 1/g_m r_n & 0 \\ 0 & 0 \end{bmatrix}$$
$$= \begin{bmatrix} r_m/r_n & 0 \\ 0 & 0 \end{bmatrix}$$

This is nothing but a VCVS of gain  $r_n/r_m$ .  
(In the book there is printing error, where gain is given as  $r_m/r_n$ )

(b) If the positions of the VCCS and CCVS are


reversed to form a network  $N'$ , then

$$[a]_{N'} = \begin{bmatrix} 0 & 0 \\ 1/r_n & 0 \end{bmatrix} \begin{bmatrix} 0 & 1/g_m \\ 0 & 0 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 0 & r_m/r_n \end{bmatrix}$$

This  $N'$  corresponds to CCCS of gain  $r_m/r_n$

(In the book there are 2 printing errors. In (b) VCVS should be VCCS and  $r_m/r_n$  should have been  $r_n/r_m$ .)

3.6

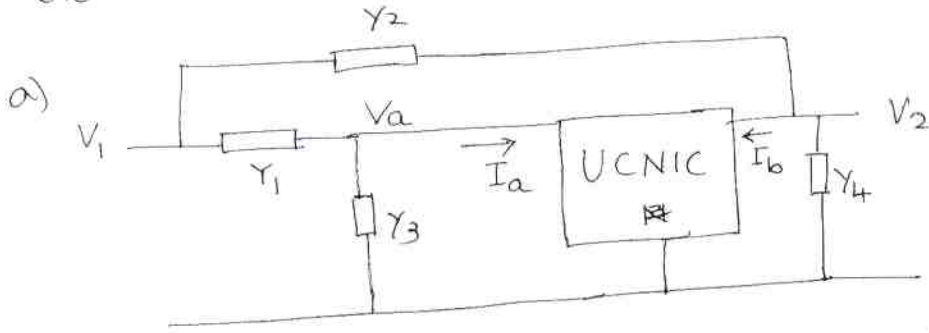

Assume the UCNIC to be a 3-T device. Since its chain matrix is given by

$$[a]_{\text{UCNIC}} = \begin{bmatrix} 1 & 0 \\ 0 & -1 \end{bmatrix},$$

we have

$$\begin{aligned} V_a &= V_2 \\ I_a &= I_b \end{aligned}$$


Now,  $(V_1 - V_a) Y_1 = V_a Y_3 + I_a$

$$(V_1 - V_2) Y_2 = I_b + V_2 Y_4$$

Using  $V_a = V_2$  and  $I_a = I_b$ , we get

$$\frac{V_2}{V_1} = \frac{Y_1 - Y_2}{(Y_1 - Y_2) + (Y_3 - Y_4)}$$

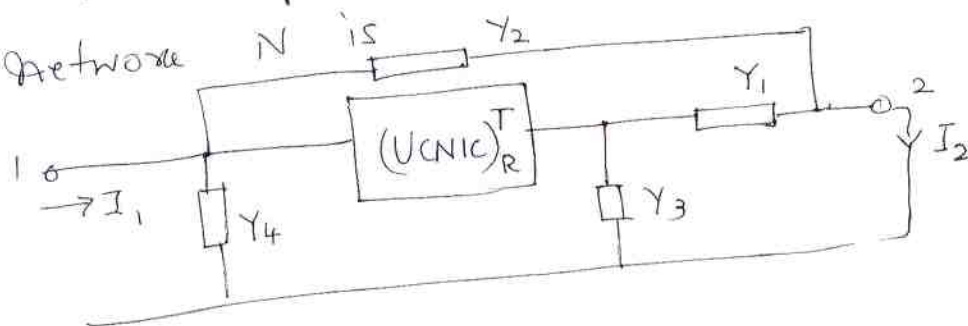(b) The transposed network  $N_R^T$  corresponding to given




3.6  
(Contd.)

From Eq (3.21) we know that if  $\begin{bmatrix} A & B \\ C & D \end{bmatrix}$  is the chain matrix of a network, then its transposed-reverse network has the chain matrix  $\begin{bmatrix} D & B \\ C & A \end{bmatrix}$ . Hence the [a] of the transposed-reverse element corresponds to UCNIC is  $\begin{bmatrix} -1 & 0 \\ 0 & 1 \end{bmatrix}$ , which corresponds to a UVNIC. Using this, it can easily be shown that the ~~CTF~~ short-circuit CTF of the transpo  $N_R^T$  is


$$\frac{I_2}{I_1} = \frac{Y_1 - Y_2}{(Y_1 - Y_2) + (Y_3 - Y_4)}$$

the same as the VTF of the original network.

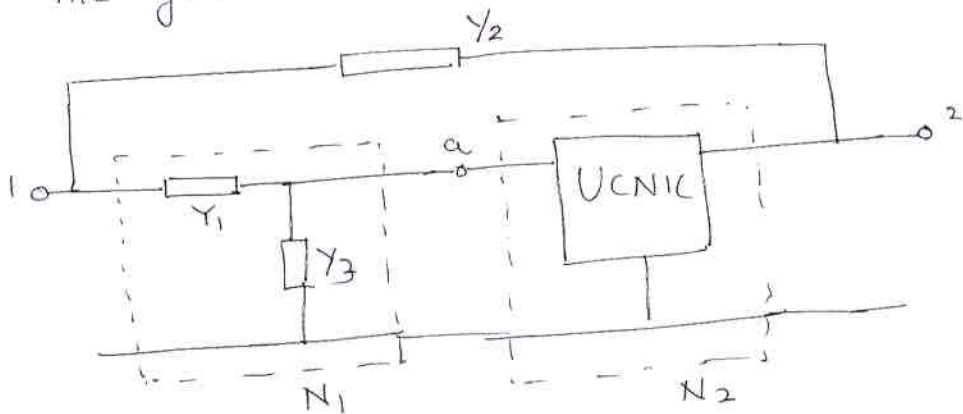(c) The given network N can be rewritten as



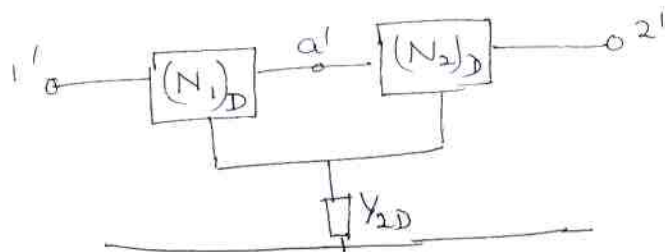Using Theorem 3.1 and the result of Problem P.3.2, we see that the dual of the above is as shown below




3.6  
(Contd.)

Assuming we are taking capacitive duals (page 45), the chain matrix of  $(N_2)_D$  is given by

$$\begin{bmatrix} D & c \frac{1}{s} \\ Bs & A \end{bmatrix} = \begin{bmatrix} -1 & 0 \\ 0 & 1 \end{bmatrix}$$

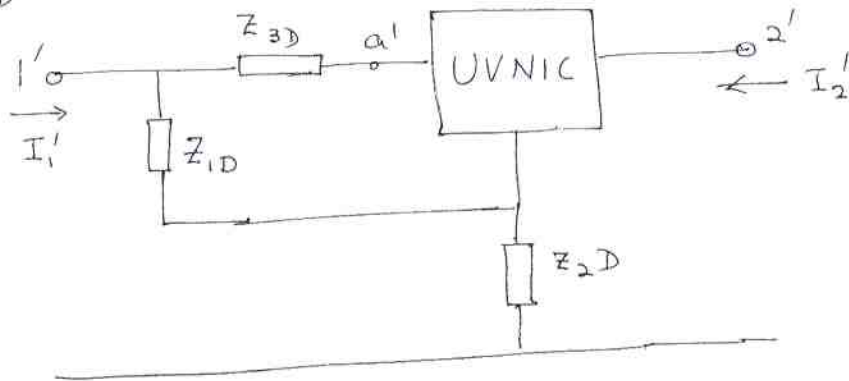which corresponds to UVNIC. Hence the network  $(N)_D$  is as follows, where  $Z_{iD} = \frac{1}{s} Y_i$



It can be shown using Kirchoff's laws that the shunt circuit CTF of the above network is the same as the open circuit VTF of the original network.

(d) Just as  $N_R^T$  was obtained from  $N$  in section (b), we can find the structure for  $(N_D)^T$  and show that its open circuit VTF is the same as that of the original.

3.7

$$A_p = 3 \text{ dB}, \quad A_s = 25 \text{ dB}$$

$$f_s/f_c = 4 \quad \text{MFM approx.}, \quad \text{BUT-response}$$

$$\epsilon = .997 \quad n = 3$$

$$H_N(s) = \frac{1}{s^3 + 2s^2 + 2s + 1} \quad (\text{using Tables})$$

$$\text{If } A_p = 1 \text{ dB}, \quad \epsilon = .5088, \quad n = 3$$

roots of $D(s)$ :	1.2526, 0	1
	.6263, 1.0847	1
	-0.6263, 1.0847	2
	-1.253, 0	3
	-0.6263, -1.0847	4
	0.6263, -1.0847	5

HINTS / ANSWERS  
 PROBLEM SET Ch. 3

$$\begin{aligned}
 H_N(s) &= \frac{1}{((s + 0.6263) + j1.0847)((s + 0.6263) - j1.0847)(s + 1.253)} \\
 \text{Chosen to} & \\
 \text{make } |H(0)| &= 1. \quad \rightarrow 1.9657 \\
 &= \frac{1.9657}{(s + 1.253)(s^2 + 1.2526s + 1.5688)}
 \end{aligned}$$

This is the normalized filter function

Alt: Use  $H_N(s)$  for BUT function and let this be  $H(\hat{s})$

$$H(\hat{s}) = \frac{1}{\hat{s}^3 + 2\hat{s}^2 + 2\hat{s} + 1}$$

Then use  $s \rightarrow \hat{s} \epsilon^{-1/n}$  i.e.  $\hat{s} = \epsilon^{1/n} s$

Now  $\epsilon = .5088$ ;  $(.5088)^{1/3} = .7983$

$$\begin{aligned}
 \text{So } H_N(s) &= \frac{1}{(.7983s)^3 + 2(.7983s)^2 + 2(.7983s) + 1} \\
 &= \frac{1.9658}{s^3 + 2.5056s^2 + 3.1386s + 1.9658}
 \end{aligned}$$

which is same as:

$$\frac{1.9658}{(s + 1.253)(s^2 + 1.2526s + 1.5688)}$$

3.8

BUT-LPF, so  $A_p = 3$  dB $f_c = 10^3$  Hz,  $A_s = 28$  dB at  $f = 2f_c$  (2 octave)

So

 $A_p = 3$  dB at  $f = 10^3$  $A_s = 28$  dB at  $f = 2 \times 10^3$ 

$$\epsilon = 0.997 \approx 1.$$

$$n = 5$$

Normalized ...  $H_N(s) = \frac{1}{\Delta^5 + 3.2361\Delta^4 + 5.2361\Delta^3 + 5.2361\Delta^2 + 3.2361\Delta + 1}$

(use Tables). Now de-normalize using  $\Delta \rightarrow \Delta / (2\pi \times 10^3)$

1. MFM approximation

 $f_c = 8$  kHz,  $A_p = 1$  dB $f_s = 12$  kHz with  $A_s = 15$  dB

Work like prob 3.1

$$\epsilon = 0.5088, n = 6$$

First use  $H(\hat{s})$  for  $n=6$  in BUT-function

$$H_N(\hat{s}) = \frac{1}{\hat{\Delta}^6 + 3.8637\hat{\Delta}^5 + 7.4641\hat{\Delta}^4 + 9.1416\hat{\Delta}^3 + 7.4641\hat{\Delta}^2 + 3.8637\hat{\Delta} + 1}$$

(from Table)

Then use  $\Delta \rightarrow \hat{\Delta} \epsilon^{-1/n}$  i.e.  $\hat{\Delta} = \Delta \epsilon^{1/n} = (0.5088)^{1/6} \Delta$

$$= 0.8935 \Delta$$

$$So H_N(s) = \frac{1}{(\cdot 8935 \Delta)^6 + 3.8637(\cdot 8935 \Delta)^5 + 7.4641(\cdot 8935 \Delta)^4 + 9.1416(\cdot 8935 \Delta)^3 + 7.4641(\cdot 8935 \Delta)^2 + 3.8637(\cdot 8935 \Delta) + 1}$$

$$H_N(s) = \frac{1.9653}{\Delta^6 + 4.3242 \Delta^5 + 9.7495 \Delta^4 + 12.8156 \Delta^3 + 11.7111 \Delta^2 + 6.7847 \Delta + 1.9653}$$

This is the normalized LPF. Use  $\Delta \rightarrow \Delta / (2\pi \times 8 \times 10^3)$  for de-normalization to get the desired TF.  $H(s)$



3.10  
2-4.4

Equiripple passband → } CHEB - approximation  
monotonic stopband → }

$$\left. \begin{aligned} A_p &= 0.5 \text{ dB}, & f_c &= 6 \text{ kHz} \\ A_s &\geq 30 \text{ dB}, & f_s &\geq 15 \text{ kHz} \end{aligned} \right\} \begin{aligned} \epsilon &= 0.3493 \\ n &= 4 \end{aligned}$$

Consulting Tables, for  $n=4$ ,  $D(s)$  in CHEB for  $\epsilon=0.3493$   
i.e.  $A_p=0.5 \text{ dB}$

$$D(s) = s^4 + 1.197s^3 + 1.717s^2 + 1.025s + 0.379$$

$$\text{Then } H_N(s) = \frac{1 / (2^{n-1} \cdot \epsilon)}{s^4 + 1.197s^3 + 1.717s^2 + 1.025s + 0.379}$$

$$H_N(s) = \frac{0.3578}{s^4 + 1.197s^3 + 1.717s^2 + 1.025s + 0.379}$$

Note: at  $j\omega=0$  i.e. d.c.  $|H(0)| = \frac{0.3578}{0.379} = 0.944$  which is  
 $= \frac{1}{\sqrt{1+\epsilon^2}} = 0.944$  since the order is "even"

Now de-normalize  $s \rightarrow s / (2\pi \times 6000)$

3.11 &  
4.5

Equiripple passband } CHEB approximation  
Monotonic stopband }

$$\omega_{CH} = 2\pi \times 15 \times 10^3; \quad \omega_{SH} = 7.8 \times 10^3 \times 2\pi$$

$$\omega_s = \frac{15}{7.8} \quad A_p = 0.5 \text{ dB}, \quad A_s \geq 35 \text{ dB. Calculate } n=5$$

$$\downarrow \epsilon = 0.3493$$

From Tables, norm. (i.e.  $\omega_c=1$ ) LPF (use  $A_p > 0.5 \text{ dB}$  in Tables)

$$H_{NLPF}(s) = \frac{0.1789}{s^5 + 1.17251s^4 + 1.9374s^3 + 1.3096s^2 + 0.7525s + 0.1789}$$

[ note: for 'odd' order  $|H(0)| = 1$  ]

together  $s \rightarrow \frac{\omega_{CH}}{s}$

Frequency transformation  $s \rightarrow \frac{1}{s}$  (LP  $\rightarrow$  HP)

$$H_N(s) \Big|_{HPF} = \frac{0.1789 s^5}{1 + 1.17251s + 1.9374s^2 + 1.3096s^3 + 0.7525s^4 + 0.1789s^5}$$

Frequency scale  $s \rightarrow \frac{s}{2\pi \times 15 \times 10^3}$  (i.e.  $s \rightarrow \frac{s}{\omega_{CH}}$ )

$$H(s) \Big|_{HPF} = \frac{0.1789 s^5}{(2\pi \times 15 \times 10^3)^5 + 1.17251 (2\pi \times 15 \times 10^3)^4 s + 1.9374 (2\pi \times 15 \times 10^3)^3 s^2 + 1.3096 (2\pi \times 15 \times 10^3)^2 s^3 + 0.7525 (2\pi \times 15 \times 10^3) s^4 + 0.1789 s^5}$$

is the desired TF. of the HPF.

3.12

$$A_p = 0.5 \quad ; \quad A_s = 60 \quad \text{when} \quad \omega_s = \frac{\omega_a}{\omega_c} = 10$$

$$\epsilon = 0.3493 \quad , \quad n = 3$$

Using formula and Table

$$H_N(s) = \frac{\frac{1}{2} \epsilon^{\frac{3-1}{2}}}{s^3 + 1.253s^2 + 1.535s + 0.716}$$

is the normalized LPF transfer function

3.13

The equivalent normalized LPF has

$$\omega_c = 2\pi(20-15) \times 10^3$$

$$\omega_a = 2\pi(35-86) \times 10^3 \quad \left\{ \begin{array}{l} \text{so } \omega_s = \frac{26.4}{5} = 5.28 \end{array} \right.$$

$A_p = 1 \text{ dB}$ ,  $A_s = 40 \text{ dB}$ . The approximation is MEM

find  $\epsilon = 0.5088$ ,  $n = 4$

So  $H_N(\hat{s})|_{\text{LPF}} = \frac{1}{\hat{s}^4 + 2.613\hat{s}^3 + 3.414\hat{s}^2 + 2.613\hat{s} + 1}$

from Table of BUT-function where  $\epsilon = 1$

For  $\epsilon = 0.5088$ , use  $\hat{s} = s \epsilon^{1/n} = 0.8446s$

$$H_N(s)|_{\text{LPF}} = \frac{1}{[(0.8446)^4 s^4 + 2.613(0.8446)^3 s^3 + 3.414(0.8446)^2 s^2 + 2.613(0.8446)s + 1]}$$

$$= \frac{1.9651}{s^4 + 3.0938s^3 + 4.7859s^2 + 4.3369s + 1.9651}$$

Apply LP  $\leftrightarrow$  BP transformation.

$$B = 2\pi \cdot 5 \times 10^3 \quad ; \quad \omega_0 = (\sqrt{20 \times 15})^3 \cdot 2\pi \times 10$$

Change:  $s \rightarrow \frac{2\pi \times 10^3 \sqrt{20 \times 15}}{2\pi \times 10^3 \times 5} \left[ \frac{s}{2\pi \times 10^3 \sqrt{20 \times 15}} + \frac{2\pi \times 10^3 \sqrt{20 \times 15}}{s} \right]$

$$\rightarrow \frac{3.183 \times 10^{-5} s + 3.7699 \times 10^5}{s^2 + 1.184352529 \times 10^{10}}$$

$$\rightarrow \frac{3.183 \times 10^{-5} s + 3.7699 \times 10^5}{31415.92654 s}$$

3.13 / Note that

$$f(s) = \frac{b_0}{s^4 + a_1 s^3 + a_2 s^2 + a_3 s + a_4}$$

under  $s \rightarrow \frac{s^2 + \Omega_0^2}{B s}$  transformation changes to  $\bar{f}(s)$

$$\bar{f}(s) = \frac{b_0 \cdot B^4 s^4}{(s^2 + \Omega_0^2)^4 + a_1 B s (s^2 + \Omega_0^2)^3 + a_2 B^2 s^2 (s^2 + \Omega_0^2)^2 + a_3 B^3 s^3 (s^2 + \Omega_0^2) + a_4 B^4 s^4}$$

The denominator can be simplified to

$$s^8 + a_4 B s^7 + (a_2 B^2 + 4 \Omega_0^2) s^6 + (3 a_1 B \Omega_0^2 + a_3 B^3) s^5 + (a_4 B^4 + 2 a_2 B^2 \Omega_0^2 + 6 \Omega_0^4) s^4 + (3 a_1 B \Omega_0^4 + a_3 B^3 \Omega_0^2) s^3 + (a_2 B^2 \Omega_0^4 + 4 \Omega_0^6) s^2 + a_1 B \Omega_0^6 s + \Omega_0^8$$

In the present case:

$$H_N(s) \Big|_{LPF} \Rightarrow H(s) \Big|_{BPF} = \frac{1.9651 \cdot (2\pi \times 10^3 \times 5 s)^4}{(s^2 + 1.1843 \times 10^{10})^4 + 3.0938 \times 3.142 \times 10^4 s (s^2 + 1.1843 \times 10^{10})^3 + 4.7859 \times (3.142 \times 10^4)^2 s^2 (s^2 + 1.1843 \times 10^{10})^2 + 4.3367 \times (3.142 \times 10^4)^3 s^3 (s^2 + 1.1843 \times 10^{10}) + 1.9651 (3.142 \times 10^4)^4 s^4}$$

$$\approx \frac{4.7879 \times 10^{20} s^4}{[250 s^8 + 24302 \times 10^7 s^7 + 1.3024 \times 10^{13} s^6 + 8.9705 \times 10^{17} s^5 + 2.3884 \times 10^{23} s^4 + 1.0624 \times 10^{28} s^3 + 1.8267 \times 10^{33} s^2 + 4.0357 \times 10^{37} s + 4.9179 \times 10^{42}]}$$

3.14

equiripple passband  $\rightarrow$  CHEB filter

$$A_p = 10 \text{ dB}, \quad \epsilon = 0.5089, \quad \Omega_{p1} = 2\pi \cdot 40 \text{ K}, \quad \Omega_{p2} = 2\pi \cdot 100 \text{ K}, \quad A_s = 15 \text{ dB}$$

$$\omega_{a1} = 2\pi \cdot 50 \text{ K}; \quad \omega_{a2} = 2\pi \cdot 80 \text{ K}$$

$$\text{So } \omega_s = \frac{100 - 40}{80 - 50} = \frac{60}{30} = 2, \quad n \geq 2.33 \rightarrow 3$$

$$\text{Then } H_N(s) \Big|_{\text{LPF}} = \frac{1 / (2^{3-1} \times 0.5089)}{s^3 + 0.988s^2 + 1.238s + 0.491}$$

$$\text{Now } \Omega_0 = 2\pi \sqrt{50 \times 80} \times 10^3 \text{ rad/sec} = 397383.5306 \text{ rad/sec}$$

$$B = 2\pi(80 - 50) \times 10^3 = 2\pi \times 30 \times 10^3 = 188495.5592 \text{ rad/sec}$$

$$\text{Apply LP} \rightarrow \text{BS transformation } s \leftrightarrow B \cdot \frac{s}{s^2 + \Omega_0^2}$$

$$H(s) \Big|_{\text{BSF}} = \frac{0.491}{B^3 \frac{s^3}{(s^2 + \Omega_0^2)^3} + 0.988 \cdot B^2 \cdot \frac{s^2}{(s^2 + \Omega_0^2)^2} + 1.238 \cdot B \cdot \frac{s}{(s^2 + \Omega_0^2)} + 0.491}$$

$$= \frac{0.491 (s^6 + 47374 \times 10^{11} s^4 + 7.981 \times 10^{22} s^2 + 3.9378 \times 10^{33})}{[0.491 s^6 + 2.3336 \times 10^5 s^5 + 2.6771 \times 10^{11} s^4 + 8.0598 \times 10^{16} s^3 + 4.2275 \times 10^{22} s^2 + 5.8191 \times 10^{27} s + 1.9335 \times 10^{33}]}$$

3.15  
 (see prob 3.7)

Ripple in passband implies a CHEB response.

$$A_p \leq 1 \text{ dB}; \quad \epsilon = 0.5089$$

$$D = \frac{10^{0.1 A_p} - 1}{10^{1 A_p} - 1} = \frac{10^{0.05} - 1}{10^1 - 1} = \frac{315.23}{9} = 34.89$$

$$\sqrt{D} = 34.89; \quad \text{Order } n \geq \frac{\cosh^{-1} \sqrt{D}}{\cosh^{-1} \omega_s} = \frac{\cosh^{-1}(34.89)}{\cosh^{-1}(1)} \rightarrow f_s/f_c = 9$$

order  $n \geq 2.057$ . Take  $n = 3$

$$S_o \quad H_n(s) = \frac{1}{2\epsilon} \cdot \frac{1}{s^3 + 0.9885s^2 + 1.2385s + 0.491} \quad (\text{from Table})$$

$$= \frac{1}{s^3 + 0.9885s^2 + 1.2385s + 0.491}$$

which is a CHEB-LP filter of order 3

3.16 Elliptic filter function

$$\omega_c = 1 \text{ rad/sec}, \quad \omega_s/\omega_c = 1.2, \quad A_p = 0.5 \text{ dB}, \quad A_s = 45 \text{ dB}$$

$$\text{For MFM} \quad n \geq \frac{\log D}{2 \log(\omega_s/\omega_c)}, \quad D = \frac{10^{0.1 A_s} - 1}{10^{0.5} - 1} = \frac{10^{4.5} - 1}{10^{0.5} - 1} = 259155.69$$

$$n_{\text{MFM}} \geq 34.18 \quad n_{\text{MFM}} = 35$$

$$\text{For CHEB} \quad n \geq \frac{\cosh^{-1} \sqrt{D}}{\cosh^{-1}(1.2)} \Rightarrow \frac{\cosh^{-1}(509.073)}{\cosh^{-1}(1.2)} = 11.13$$

$$S_o \quad n_{\text{CHEB}} = 12$$

For elliptic

$$u(D) = \frac{1}{16D} \left(1 + \frac{1}{2D}\right) = 0.24117 \times 10^{-6}$$

$$v(\omega_s) = \frac{\sqrt{\omega_s} - 1}{2(\sqrt{\omega_s} + 1)} = \frac{\sqrt{1.2} - 1}{2[\sqrt{1.2} + 1]} = 0.02277$$

$$F(u) = \frac{1}{\pi} \ln[u + 2u^5 + 15u^9] = -4.8497$$

$$F(v) = \frac{1}{\pi} \ln[v + 2v^5 + 15v^9] = -1.2037$$

$$\text{order } n \geq F(u)/F(v) = 5.83; \quad S_o \quad n_{\text{ELLIP}} = 6$$

~~3.17~~  
3.17

An MFM filter of order 'n' has

$$|H_n(j\omega)|^2 = \frac{1}{\epsilon^2 \omega^{2n} + 1}$$

$\omega \rightarrow$  normalized frequency  
w.r.t. the pass-band edge  
frequency.

In the case of  $A_p = 1$  dB

$$10 \log |H_n(j\omega)|^2 = -1 = 10 \log_{10} \left[ \frac{1}{\epsilon^2 + 1} \right]$$

$$\epsilon = 10^{0.1 A_p} - 1 = 0.2589$$

For a sixth order MFM,  $n=6$

$$|H_6(j\omega)|^2 = \frac{1}{\epsilon^2 \omega^{12} + 1} = \frac{1}{(0.2589)^2 \omega^{12} + 1}$$

$$\text{with } \omega = \frac{\omega_A}{\omega_C} = 10; \quad |H_6(j\omega)|^2 = \frac{1}{(0.2589)^2 \times 10^{12} + 1} \approx \frac{1}{10^{12}}$$

3.18 Consulting Table B-2 (Huelsman, L.P.)  
 For  $A_p = 1 \text{ dB}$ ,  $A_s > 46 \text{ dB}$ ,  $n = 8$  with  $A_p = 1 \text{ dB}$ ,  $A_s = 49.33 \text{ dB}$

$$T(s) = H \cdot \frac{(s^2 + 1.1139)}{s^2 + 0.5482s + 1.1915} \cdot \frac{(s^2 + 1.243)}{s^2 + 1.2607s + 1.6404} \cdot \frac{(s^2 + 1.9061)}{s^2 + 1.0845s + 1.9118} \cdot \frac{(s^2 + 11.0467)}{s^2 + 0.182s + 0.9994}$$

$H \rightarrow$  choose suitably

3.19 normalized frequency is  $700 \times 2.5 \times 10^{-3} = 1.75$

Delay error  $< 3\%$

Magnitude error  $< 3 \text{ dB}$  for up to  $1000 \text{ rad/sec}$ .

We will try to look for a magnitude error of  $< 2$  or  $2.5 \text{ dB}$  until  $\omega = 700 \text{ rad/sec}$  which has been used for calculating the normalized frequency.

A more ~~conservative~~ conservative case will be to look for the BT filter function using  $\omega = 1000 \text{ rad/sec}$ ,

normalized frequency  $\gamma = 1000 \times 2.5 \times 10^{-3} = 2.5$ .

Then surely for  $\omega = 700 \text{ rad/sec}$ , all the specs. will be satisfied.

From Fig 3.16 (a), (b)  $n = 6$  for magn. error  $< 3 \text{ dB}$

$n = 5$  for delay error  $< 3\%$ .

So we need a BT filter of order 6.

Using  $700 \text{ rad/sec}$  to calculate the normalized frequency could lead to  $n = 4$ . But  $n = 6$  is a better choice.

$$T(s) = \frac{10395}{s^6 + 21s^5 + 210s^4 + 1260s^3 + 4725s^2 + 10395s + 10395}$$

Using Table A-5 for  $n = 6$

3.20

Consider a BT filter as an AP filter.

$$\text{Then } \gamma = \omega_0 \tau = 4 \times 10^3 \times 2\pi \times 300 \times 10^{-6} = 7.54$$

From Fig 3.16(b), for delay error  $< 1.5\%$ ,  $n = 11$

The AP function is an 11<sup>th</sup> order BT filter.

Use eqn. (3.83), (3.84) to derive the expression for the function.