

Hints & Solutions to Problems in Ch. 4

(4.1)

Considering Tables of BUT function


$$H_N(s) = \frac{1}{s^3 + 2s^2 + 2s + 1} = \frac{1}{\underbrace{2s^2+1}_{M_2} + \underbrace{s^3+2s}_{M_1}}$$

$$Y_{22} = \frac{M_2}{M_1} = \frac{2s^2+1}{s^3+2s}, \text{ quotient will be of degree } < 1 \text{ in } s$$

So consider $\frac{1}{Y_{22}}$ instead i.e.

$$\frac{M_1}{M_2} = \frac{s^3+2s}{2s^2+1}$$

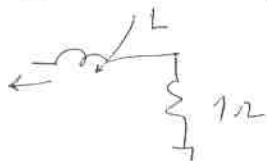As a result, we begin with a series inductance at the load end, i.e.,




$$2s^2+1) \overline{s^3+2s} \quad (0.5s \rightarrow \text{inductance } L = 0.5H = L_1$$

$$\underline{1.5s} \quad 2s^2+1 \quad (1.33s \rightarrow \text{capacitance } C = 1.33F = C_2$$

$$\underline{1.5s} \quad 1.5s \quad (1.5s \rightarrow \text{inductance } L = 1.5H = L_3$$

So the network is

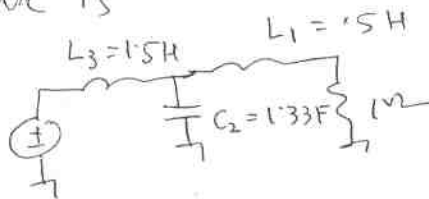

1Ω is the load.
Excitation is an ideal voltage source i.e. with $R_s = 0$.

(4.2)

The specs are $A_p = 3 \text{ dB}$ at $f_c = 1 \text{ kHz}$
 $A_a = 25 \text{ dB}$ at $f_c = 2 \text{ kHz}$

Then $n_{BUT} = 5$.

$$H_N(s) = \frac{1}{s^5 + 3.2361s^4 + 5.2361s^3 + 5.2361s^2 + 3.2361s + 1} \quad \text{from Tables}$$

$$\text{Then } M_2(s) = 3.2361s^4 + 5.2361s^2 + 1$$

$$M_1(s) = s^5 + 5.2361s^3 + 3.2361s$$

4.2
4.2

Using eq. 3.22 (Ch 3) with $R_s = 1$, $R_L = \infty$ (OA input impedance)


$$\frac{V_2}{V_s} = \frac{1}{A+C} = \frac{Z_{21}}{1+Z_{11}} \quad \text{using the equiv between}$$

A, B, C, D to $[Z]$ parameters.

Following the discussion in section 4.3, we need to realize Z_{11} as $\frac{m(s)}{n(s)}$ (if $\deg m(s) > \deg n(s)$) or as $\frac{n(s)}{m(s)}$ (if $\deg n(s) > \deg m(s)$) where m & n are respectively the even and odd parts of $D(s)$, i.e.

$$H(s) = \frac{V_2}{V_s} = \frac{N(s)}{D(s)}$$

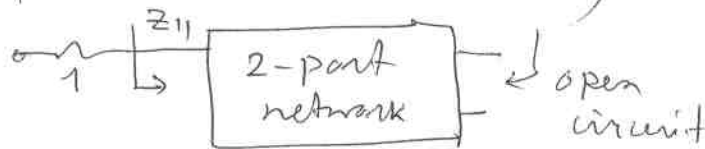For all-pole function, $N(s)$ will be a constant (i.e. no finite transmission zeros)



For a 3rd order BUT filter $D(s) = s^3 + 2s^2 + 2s + 1$

$$m(s) = 2s^2 + 1; \quad n(s) = s^3 + 2s, \quad \deg n(s) > \deg m(s)$$

realize Z_{11} as $\frac{h(s)}{D(s)} = \frac{s^3 + 2s}{2s^2 + 1}$


$$\frac{2s^2 + 1}{s^3 + 2s} \left(\frac{s}{2} \rightarrow \text{inductor, first series element from } R_s \text{ side!} \right)$$

continue ... as in Example 4.3

The normalized filter with $R_s = 1 \Omega$ is then



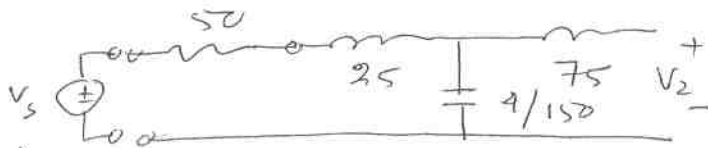For $R_s = 50 \Omega$, use impedance scaling



4.3

Contd.

$Y_{22} = \frac{M_2}{M_1}$ of degree < 1 . So start with $1/Y_{22}$ instead. The first element at the load end will be an inductance L .

$$\frac{3 \cdot 2361 s^4 + 5 \cdot 2361 s^2 + 1}{s^5 + 5 \cdot 2361 s^3 + 3 \cdot 2361 s} (0.309 s \rightarrow \underline{0.309 H})$$


$$\frac{3 \cdot 6181 s^3 + 2 \cdot 9271 s}{3 \cdot 2361 s^4 + 5 \cdot 2361 s^2 + 1} (0.894 s \rightarrow \underline{0.894 F})$$

$$\frac{2 \cdot 6181 s^2 + 1}{3 \cdot 6181 s^3 + 2 \cdot 9271 s} (1.382 s \rightarrow \underline{1.382 H})$$

$$\frac{1 \cdot 5451 s}{2 \cdot 6181 s^2 + 1} (1.694 s \rightarrow \underline{1.694 F})$$

$$\frac{1}{1 \cdot 5451 s} (1.5451 s \rightarrow \underline{1.5451 H})$$


Normalized filter:

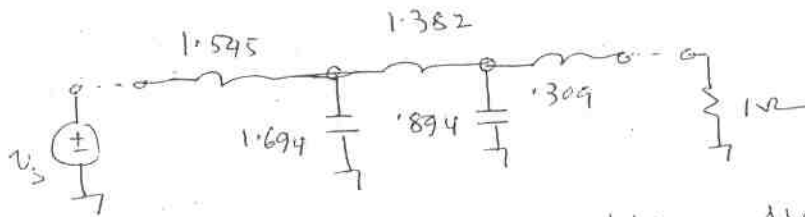


To have $f_c = 1 \text{ kHz}$, $\omega_c = 6283.18 \text{ rad/sec}$. Scale all components

like $L \rightarrow L/6283.18$, $C \rightarrow C/6283.18$

Frequency denormalized filter is given:

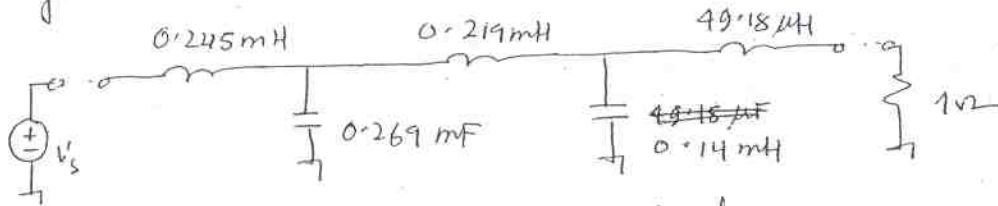

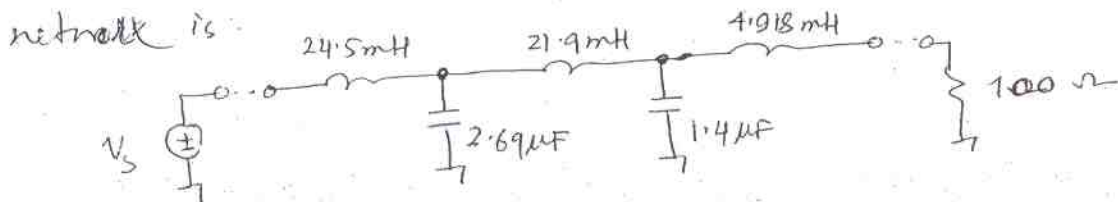For a load $R_L = 100 \Omega$, impedance scale $L \rightarrow L \times 100$, $C \rightarrow C/100$. Final filter



4.4

The filter has CHEB magnitude response. The order is $n_{CHEB} = 4$ with $\epsilon = 0.3493$.

Then $H_N(s) = \frac{1}{2^3 \cdot \epsilon (s^4 + 1.197s^3 + 1.717s^2 + 1.025s + 0.379)}$

Consider $D(s) = s^4 + 1.197s^3 + 1.717s^2 + 1.025s + 0.379$

$M_2(s) = s^2 + 1.717s + 0.379$

$M_1(s) = 1.197s^2 + 1.025s$

$\therefore \text{deg}(M_2) > \text{deg}(M_1)$, we start with $Y_{22} = \frac{M_2}{M_1}$ as it is.


$(1.197s^2 + 1.025s) \left(\frac{s^2 + 1.717s + 0.379}{s^2 + 1.856s} \right) \rightarrow \frac{1}{1} \cdot 0.835 F$

$(0.861s^2 + 0.379) \left(\frac{1.197s^2 + 1.025s}{1.197s^2 + 0.527s} \right) \rightarrow \frac{1.39 H}{1}$

$(0.498s) \left(\frac{0.861s^2 + 0.379}{0.861s^2} \right) \rightarrow \frac{1}{1} \cdot 1.729 F$


$(0.379) \left(\frac{0.498s}{0.498s} \right) \rightarrow \frac{1.314 H}{1}$

The frequency normalized filter is:

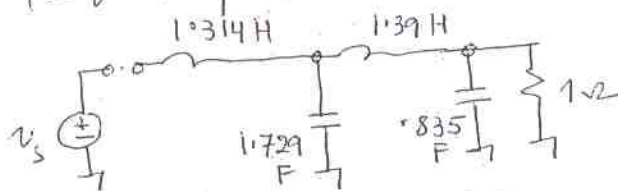

Frequency denormalized filter is:

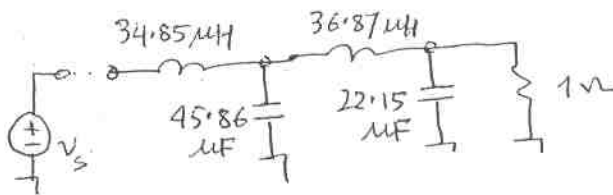$L \rightarrow \frac{L}{2\pi \times 6000}$
 $C \rightarrow \frac{C}{2\pi \times 6000}$




4.5


CHEB filter, $n_{CHEB} = 5$, $\epsilon = 0.3493$

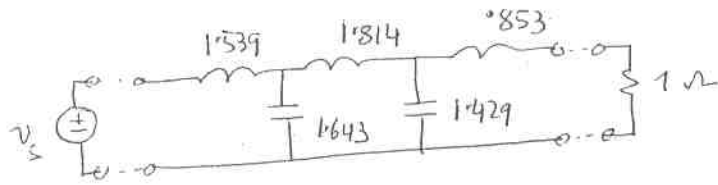4.5
(cont.)

cont. The normalized LP filter structure is:



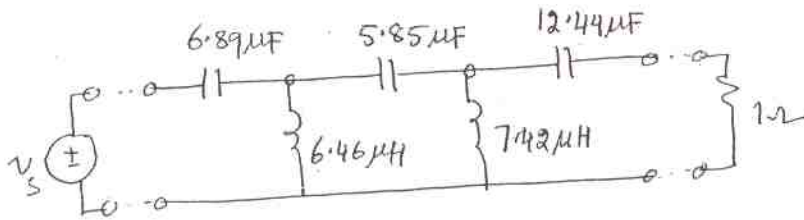The frequency denormalized HPF is (by component transformation formulae): $L_{HP} \rightarrow \frac{1}{\omega_{CH} C_{LP}}$; $C_{HP} \rightarrow \frac{1}{\omega_{CH} L_{LP}}$



$$\omega_{CH} = 2\pi \times 15 \times 10^3$$

4.6

With order $n=3$ and $A_p=0.5$ dB, $\epsilon = 0.3493$
Using eqn. (16) in ch 6,

$$q = \frac{1}{2} \left[\left(\frac{1}{\epsilon} + \sqrt{1 + \frac{1}{\epsilon^2}} \right)^{1/n} - \left(\frac{1}{\epsilon} + \sqrt{1 + \frac{1}{\epsilon^2}} \right)^{-1/n} \right] = 0.6265$$

$$k_m \approx n/2 = 1$$

$$\text{Then } C_1 = \frac{2}{qR_s} \cdot \sin \frac{\pi}{2n} = 1.596 \text{ with } R_s = 1 \Omega$$

$$C_1 L_2 = \frac{4 \sin \left(\frac{4k-1}{2n} \pi \right) \sin \left(\frac{4k-3}{2n} \pi \right)}{q^2 + \sin^2 \left(\frac{2k-1}{n} \pi \right)}$$


$$\text{with } C_1 = 1.596, k=1$$

$$L_2 = \frac{1}{1.596} \cdot 1.7505 = 1.0968$$

$$C_3 L_2 = \frac{4 \sin \left(\frac{4k-1}{2n} \pi \right) \sin \left(\frac{4k+1}{2n} \pi \right)}{q^2 + \sin^2 \left(\frac{2k}{n} \pi \right)} \text{ with } L_2 = 1.0968$$


$$C_3 = 1.596$$

The normalized LPF network is then

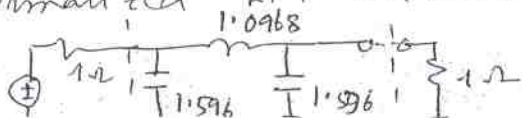

4.6

load.

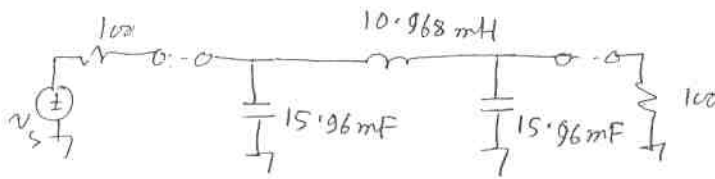For $R_L = R_S = 100 \Omega$, the network will be

4.7

Use the formulae as above.

$$n = 4, \quad A_p = 1 \text{ dB} \rightarrow \epsilon = 0.5088, \quad Q = 1.7293$$

$$\text{With } R_S = 1 \Omega, \quad R_L = [1 + 2\epsilon^2 \pm 2\epsilon\sqrt{1+\epsilon^2}] R_S \\ = 2.6595 \text{ using the + sign before } 2\epsilon\sqrt{1+\epsilon^2}$$


$$R_m < n/2 = 2. \quad \text{So } R_m = 1$$

So $R = 1$ to be taken. Let $R_S = 1 \Omega$ as suggested.

$$C_1 = \frac{2}{Q R_S} \sin \frac{\pi}{2n} \rightarrow 1.0495, \quad L_2 = 1.3059$$

$$C_3 = 1.7667$$
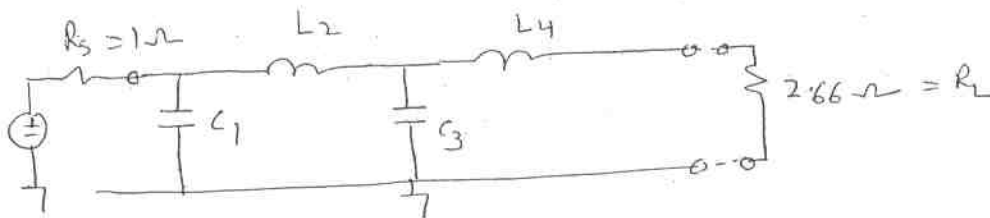
$$L_4 = R_L \frac{2}{Q} \sin \frac{\pi}{2n} = 2.791 \text{ with } R_L = 2.6595$$



4.8

$$n = 5, \quad A_p = 0.5 \text{ dB}, \quad \epsilon = 0.3493$$

$$R_m = 2 \because n = 5, \quad R_m < \frac{5}{2}$$

$k = 1, 2$ can be taken. Assume $R_S = R_L = 1 \Omega$

$$\text{With } R = 1, \quad C_1 = 1.8529, \quad L_2 = 1.3468$$

$$C_3 = 1.6807$$


4.8

Contd.

with $k=2$


$$L_4 = \frac{1}{C_3}$$
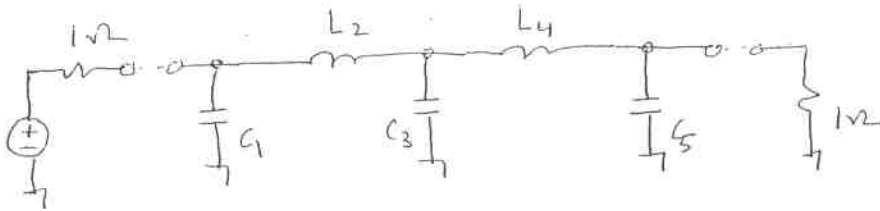
$$\frac{4 \sin\left(\frac{4k-1}{2n} \pi\right) \sin\left(\frac{4k-3}{2n} \pi\right)}{2^2 + \sin^2\left(\frac{2k-1}{n} \pi\right)} = 1.3468$$



And then $C_5 = \frac{1}{R_L} \cdot \frac{2}{Q} \cdot \sin \frac{\pi}{2n} = C_1 = 1.8529 \because R_L = R_S$

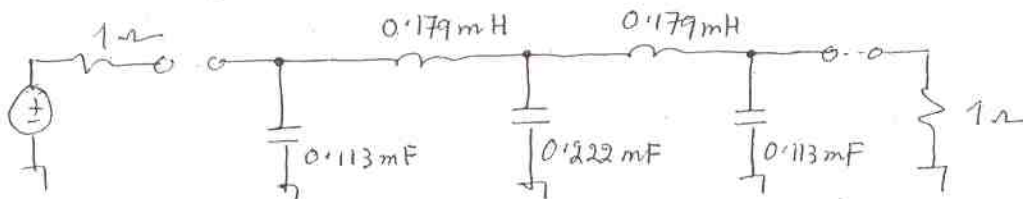The frequency denormalized filter is $C \rightarrow \frac{C_N}{2\pi f_c}$; $L \rightarrow \frac{L_N}{2\pi f_c}$
 where C_N, L_N are the values derived already. $f_c = 1.2 \times 10^3$



4.9


From the given specs, $\omega_c = 2\pi (3168 - 1578) = 2\pi (1590)$

$$\omega_a = 2\pi (5000 - 1000) = 2\pi \times 4000$$

This gives together with $A_p = 3 \text{ dB}$, $A_a = 40 \text{ dB}$,

$n_{\text{BUT}} = 5$ for the normalized L.P.F.

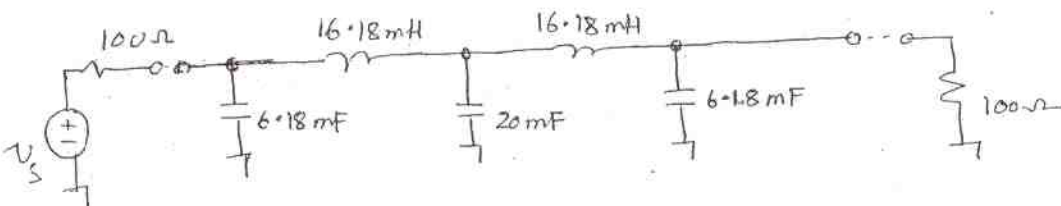Carrying out the necessary calculations, we get the L.P.F., LC structure as: (for 100 ohm terminations)



Use $LP \leftrightarrow BP$ component transformations to the L, C components to get the B.P.F. Note that:

$$\Omega_0 = 2\pi \sqrt{3168 \cdot 1578} = 14048.37 \text{ rad/sec.}$$

$$B = 2\pi \times 1590 = 9990.26 \text{ rad/sec.}$$

4.10. Follow the same procedure as shown in Example 4.7 of the book.

4.1)

$$\eta = \frac{10^{1As} - 1}{10^{1Ap} - 1} = \frac{10^{3.3} - 1}{10^{-1} - 1} = 7702.07$$

$$u(\eta) = \frac{1}{16\eta} \left(1 + \frac{1}{2\eta} \right) ; \quad v(\omega_s) = \frac{\sqrt{\omega_s} - 1}{2(\sqrt{\omega_s} + 1)} \quad ; \quad \omega_s = \frac{2000}{1000} = 2$$

$$= 8.115 \times 10^{-6} \quad = 0.1082$$

order $n = F(u) F(v)$, $F(x) = \frac{1}{\pi} \ln [x + 2x^5 + 15x^9]$


$$= \frac{1}{\pi} \ln [8.115 \times 10^{-6} + 2 \times (8.115 \times 10^{-6})^5 + 15 \times (8.115 \times 10^{-6})^9] \times$$

$$\frac{1}{\pi} \ln [0.1082 + 2 \times (0.1082)^5 + 15 \times (0.1082)^9]$$

$$\approx \frac{1}{\pi^2} \ln (8.115 \times 10^{-6}) \times \ln (0.1082) = \frac{1}{\pi^2} (-11.7218) (-2.229)$$

$$\approx \frac{1}{10} \times 26.128 = 2.61 \approx 3$$

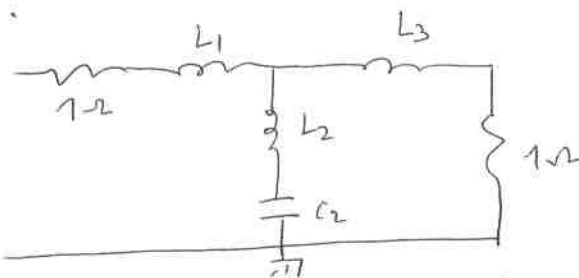Considering Table A-6 (Huelsman, 1993) for $A_p = 1$ dB, $n = 3$, $\omega_s = 2$
 The normalized low-pass elliptic filter components are:




$$L_1 = 1.85199 \text{ H}$$

$$C_2 = 0.85903 \text{ F}$$

$$L_2 = 0.2259 \text{ H}$$

$$L_3 = 1.85199 \text{ H}$$

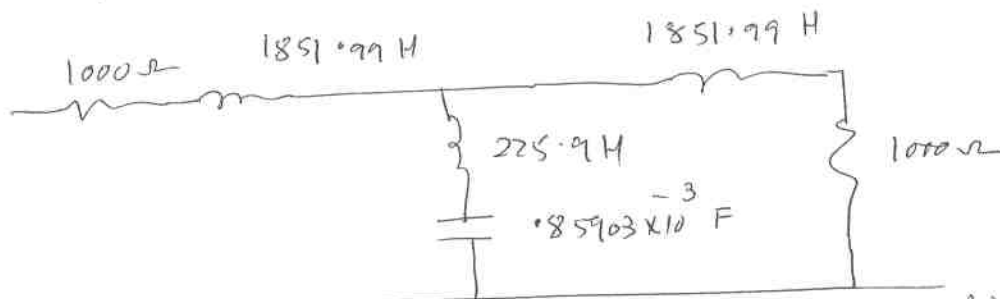For 1000Ω terminations, impedance scale by 1000



For $\omega_p = 1000$ rad., frequency scale by 1000.

$$L_i \Rightarrow \frac{L_i}{1000}$$

$$C_j \Rightarrow C_j / 1000$$