

# Solutions/Hints For Problems in Ch 6

6.1

$$\tau = \frac{L}{\omega} = \frac{1}{2\pi \times 125} = CR, \quad R = \frac{1}{2\pi \times 125 \times 15 \cdot 10^{-12}}$$

84.883 MΩ

$$C_R = \frac{1}{fR} = \frac{1}{100 \times 125 \times 84.883 \times 10^6} = 0.942 \text{ PF.}$$

6.2

The given T.F. is that of a notch filter with  $\omega_z^2 = 1.4212 \times 10^5$ ,  $\omega_p^2 = 6.9833 \times 10^5$ ,  $\frac{\omega_p}{\omega_z} = 1004.2$

(a) For  $f_s = 8 \text{ KHz}$ ,  $\hat{\omega}_p = 2f_s \cdot \tan(\omega_p/2f_s)$ ,  $\hat{\omega}_z = 2f_s \tan(\omega_z/2f_s)$   
and so on (see Table S.4) and

$$H(z) = h_D \cdot (1 + a_{1N}z^{-1} + a_{2N}z^{-2}) / (1 - a_{1D}z^{-1} + a_{2D}z^{-2})$$

with  $h_D = H_N \cdot (a^2 + \hat{\omega}_z^2) / F_2$  where

$H_N$  is the flat gain in the analog filter and

$$F_2 = a^2 + (\hat{\omega}_p/\omega_z) a + \hat{\omega}_p^2, \quad a = 2f_s.$$

In the given function  $H_N = 1$ . Calculations will

give  $h_D = 0.939$ ,  $a_{1D} = 1.8718$ ,  $a_{2D} = 0.8821$  } For  $f_s = 8 \text{ KHz}$ .

$\frac{\hat{\omega}_z}{a} = 0.236$ :  $a_{1N} = -1.9978$ ,  $a_{2N} = 1$

$$H(z) = 0.939 \frac{1 - 1.9978z^{-1} + z^{-2}}{1 - 1.8718z^{-1} + 0.8821z^{-2}}$$

(b) For  $f_s = 128 \text{ KHz}$ , similarly,

$$\frac{\hat{\omega}_z}{a} = 1.473 \times 10^{-3}, \quad H(z) = 0.9961 \frac{1 - 1.9999z^{-1} + z^{-2}}{1 - 1.9921z^{-1} + 0.9922z^{-2}} \quad \left. \vphantom{H(z)} \right\} \text{ For } f_s = 128 \text{ KHz}$$

The attached plots show that the response for  $f_s = 128 \text{ KHz}$  is way off from the desired response  $H(z)$ .

6.2  
Contd.  
(b)

The reason seems to be in the loss of numerical accuracy when  $f = 128 \text{ kHz}$  is used. Since  $T = 1/128 \times 10^3$  is much smaller now, the coefficients  $a_{1N}, a_{1D}, a_{2D}$  are to be calculated with more accuracy and used in the calculation of  $|H(z)|$ . Thus, if we recalculate with more accuracy, we find, for  $f_s = 128 \text{ kHz}$

$$h_D = 0.9960842445 \quad a_{1N} = -1.999991326, \quad a_{2N} = 1$$

$$a_{1D} = 1.992142941 \quad a_{2D} = 0.992185397$$

$$\frac{\hat{\omega}_n}{a} = 1.472610688 \times 10^{-3}$$

On using these values, the calculated  $H(z)$  shows excellent matching with  $H(s)$ .

The MATLAB program for computing  $H(z)$ ,  $H(s)$  is attached with the plots of  $|H(s)|$ ,  $|H(z)|$ . The plot in --- line is for  $H(z)$  with  $f_s = 128 \text{ kHz}$  but for  $a_{1N}, a_{1D}$  retained with less accuracy.

6.3

$$H(s) = \frac{.891975 s^2 + 1.140926 \times 10^8}{s^2 + 356.047 s + 1.140926 \times 10^8} = .891975 \frac{s^2 + 1.27910087 \times 10^8}{s^2 + 356.047 s + 1.140926 \times 10^8}$$

transforms to:

$$H(z) = 0.8909255285 \frac{1 - 1.992198066 z^{-1} + z^{-2}}{1 - 1.990275499 z^{-1} + 0.9972254644 z^{-2}}$$

$$\frac{\hat{\omega}_n}{a} = 4.42074135E-2$$

From fig. 6.20, ignoring L, K, F and assuming  $B=D=1=A$ , we have

$$H_{2,2}(z) = \frac{I + [G - (I+J)]z^{-1} + (J-H)z^{-2}}{1 + (C+E-2)z^{-1} + (1-E)z^{-2}}$$

$$\text{So } I = .8909, \quad J-H = 1, \quad G - (I+J) = -1.9922$$


$$C+E-2 = -1.9903; \quad 1-E = 0.9972$$

I, J, H, G, C, E are unknowns.  $A=B=D=1$  assumed.

```

% a- Ch-2
%analog filter response
a=[1 1004.2 6.9833e5];
b=[1 0 1.4212e5];
f=linspace(10,500,901);
w=2*pi*f;
h=freqs(b,a,w);
mag1=abs(h);
%scf response with Fs=8000
Fs=8e3;
b=[1 -1.9978 1];
a=[1 -1.8718 0.8821];
f=linspace(10,500,901);
w=2*pi*f;
h=freqz(b,a,f,Fs);
mag2=0.939*abs(h);
%scf response with Fs=128000
Fs=128e3;
%b=[1 -1.999991326 1];
b=[1 -1.9999 1];
%a=[1 -1.992142941 0.992185397];
a=[1 -1.9921 0.9922];
f=linspace(10,500,901);
w=2*pi*f;
h=freqz(b,a,f,Fs);
mag3=0.9960842445*abs(h);
plot(f,mag1,f,mag2,f,mag3,'w:')
end

```

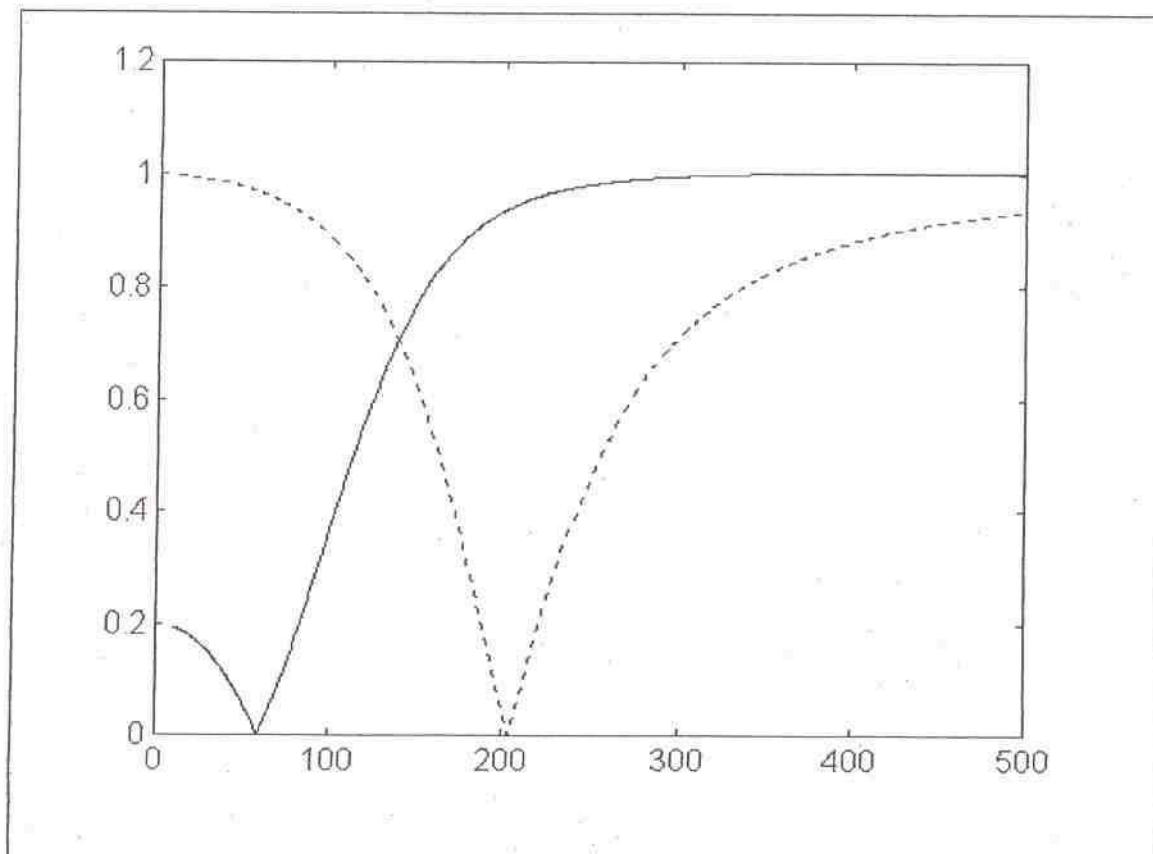

### 6.3 (contd.)

$$H_{2,2}(z) = I \frac{1 + \left(\frac{G}{I} - \frac{I+J}{I}\right) z^{-1} + \frac{J-H}{I} z^{-2}}{1 + (C+E-2) z^{-1} + (1-E) z^{-2}}$$

$$\text{So } I = 0.8909$$

$$J-H = I$$

$$G-I-J = -1.9922 I$$

$$C+E-2 = -1.9903$$

$$1-E = 0.9972$$

J, H, G, C, E → Five capacitance ratios (assuming A, B, D = 1)

Four equations.

$$\text{From } 1-E = 0.9972, \quad E = 1 - 0.9972 = 0.0028$$

$$C+E-2 = -1.9903, \text{ then gives } C = 0.0069$$

$$\text{we have } G-I-J = -1.9922 \times I$$

$$J-H = I$$

$$\text{So } G-J = -0.9922 I = -0.88316$$

$$J-H = 0.8909 \rightarrow J = H + 0.8909$$

$$\text{Let } H=1, \quad J=1.8909$$

$$\text{Then } G = 1.8909 - 0.88316 = 1.00774$$

Thus the solutions are:

$$A=1, B=1, D=1, H=1, I=0.8909$$

$$E=0.0028, C=0.0069, G=1.00774, J=1.8909$$

Scaling the minimum capacitor to be = 1 pF,

$$\text{let } E \rightarrow 1 \text{ pF, scaling factor } 1/0.0028 = 357.1428571$$

$$\text{Then } A=B=D=H \approx 357 \text{ pF}$$

$$I = 0.8909 \times 357.1428571 \approx 318 \text{ pF}$$

$$E \approx 1 \text{ pF}, C \approx 2.5 \text{ pF}, G \approx 360 \text{ pF}, J = 675 \text{ pF}$$

$$C_{\text{Total}} = 2784.5 \text{ pF} \rightarrow 2.7845 \text{ nF}$$

6.3  
Contd.

$$1-E = .9972 \text{ given } E = 0.0028$$

$$C+E-2 = -1.9903 \text{ gives } C = 2-1.9903-E = 0.0069$$

$$\text{Then } J-H=1 ; G-I-J = -1.9922 \text{ gives}$$

$$G-J = -1.9922 + .8909 = -1.1013$$

$$J-H = 1. \text{ Three unknowns } G, I, H, \text{ two}$$

equations.

$$\left. \begin{array}{l} G-J = -1.1013 \\ J-H = 1 \end{array} \right\} G-H = -.1013$$

$$\text{If we let (assume) } H=1, J=2, G=1-.1013 = 0.8987.$$

Thus, the preliminary solutions are:

$$A = B = D = 1 \text{ (assumed)}$$

$$I = .8909$$

$$G = .8987$$

$$J = 2$$

$$H = 1 \text{ (assumed)}$$

$$E = .0028$$

$$C = .0069$$

We can scale up the capacitors making the lowest capacitor = 1 PF. Thus

let  $E = 1 \text{ PF}$ , a scale factor  $1/.0028 = 357.14286$  is to be applied to all others.

$$\text{So } E = 1 \text{ PF.}$$

$$C = 2.46 \text{ PF}$$

$$H = 357.14286 \text{ PF} = 357.143 \text{ PF.}$$

$$J = 714.286 \text{ PF.}$$

$$G = 320.964 \text{ PF.}$$

$$I = 318.178 \text{ PF.}$$

$$A = B = D = 357.143 \text{ PF}$$

} A possible set of solutions



6.4

Using the results from P4.5 (Ch4),  
the HPF is

$$T(s) = \frac{s^5}{s^5 + 396482 s^4 + 0.6504039898 \times 10^{11} s^3 + 0.9069665315 \times 10^{16} s^2 + 0.5173875291 \times 10^{21} s + 0.415936312 \times 10^{26}}$$

We ignored pre-warping since  $f_s = 128 \text{ kHz}$  is  $\gg$  filter cut off frequencies.

Now applying BLT,  $s \rightarrow \frac{2}{T} \frac{1-z^{-1}}{1+z^{-1}} = 2 \times 128 \times 10^3 \frac{1-z^{-1}}{1+z^{-1}}$

$$H(z) = 0.1099511628 \times 10^{11} \frac{(1-z^{-1})^5}{D(z)}$$

$$D(z) = 0.157007829 \times 10^9 z^{-5} + 0.188512713 \times 10^{11} z^{-4} - 0.6444713465 \times 10^{11} z^{-3} + 0.1171053664 \times 10^{12} z^{-2} + 0.1049767527 \times 10^{12} z^{-1} + 0.4662020098 \times 10^{11}$$

6.5

Around OA1

$$V_1^{(1)} = V_i^{(2)} \frac{\bar{z}^{-1/2}}{1-\bar{z}^{-1}} \cdot \frac{H}{D} - V_i^{(1)} \frac{1}{1-\bar{z}^{-1}} \cdot \frac{G}{D} - V_2^{(1)} \frac{1}{1-\bar{z}^{-1}} \cdot \frac{C}{D} - \frac{E}{D} V_2^{(1)}$$

$$= \frac{(H/D) \bar{z}^{-1}}{1-\bar{z}^{-1}} V_i^{(1)} - \frac{G/D}{1-\bar{z}^{-1}} V_i^{(1)} - \frac{C/D}{1-\bar{z}^{-1}} V_2^{(1)} - (E/D) V_2^{(1)}$$

Around OA2 (ignoring  $(\phi_1), (\phi_2)$  phase pair)

$$V_2^{(1)} = V_i^{(2)} \frac{\bar{z}^{-1/2}}{1-\bar{z}^{-1}} \frac{A}{B} - \frac{K}{B} V_i^{(1)} - \frac{F}{B} \frac{1}{1-\bar{z}^{-1}} V_2^{(1)}$$

$$= \frac{(A/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} V_i^{(1)} - (K/B) V_i^{(1)} - \frac{F/B}{1-\bar{z}^{-1}} V_2^{(1)}$$

$$V_2^{(1)} = \frac{(A/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} \left[ \frac{(H/D) \bar{z}^{-1}}{1-\bar{z}^{-1}} V_i^{(1)} - \frac{G/D}{1-\bar{z}^{-1}} V_i^{(1)} - \frac{C/D}{1-\bar{z}^{-1}} V_2^{(1)} - (E/D) \frac{V_2^{(1)}}{\bar{z}^{-1}} \right]$$

$$- (K/B) V_i^{(1)} - \frac{F/B}{1-\bar{z}^{-1}} V_2^{(1)}$$

$$V_2^{(1)} \left[ 1 + \frac{F/B}{1-\bar{z}^{-1}} + \frac{(A/B)(C/D) \bar{z}^{-1}}{(1-\bar{z}^{-1})^2} + \frac{(A/B)(E/D) \bar{z}^{-1}}{1-\bar{z}^{-1}} \right]$$

$$= \frac{(A/B)(H/D) \bar{z}^{-2}}{(1-\bar{z}^{-1})^2} V_i^{(1)} - \frac{(A/B)(G/D) \bar{z}^{-1}}{(1-\bar{z}^{-1})^2} V_i^{(1)} - \frac{K}{B} V_i^{(1)}$$

$$\text{Let } D(z) = 1 + \frac{F/B}{1-\bar{z}^{-1}} + \frac{(AC/BD) \bar{z}^{-1}}{(1-\bar{z}^{-1})^2} + \frac{(AE/BD) \bar{z}^{-1}}{1-\bar{z}^{-1}}$$

$$N(z) = \frac{(AH/BD) \bar{z}^{-2}}{(1-\bar{z}^{-1})^2} - \frac{(AG/BD) \bar{z}^{-1}}{(1-\bar{z}^{-1})^2} - (K/B)$$

$$\text{Then } D(z) = \frac{\left[ (1-\bar{z}^{-1})^2 + (F/B)(1-\bar{z}^{-1}) + (AC/BD) \bar{z}^{-1} + (AE/BD) \bar{z}^{-1} (1-\bar{z}^{-1}) \right]}{(1-\bar{z}^{-1})^2}$$

$$= \frac{1 - 2\bar{z}^{-1} + \bar{z}^{-2} + F/B - (F/B) \bar{z}^{-1} + (AC/BD) \bar{z}^{-1} + (AE/BD) \bar{z}^{-1} - (AE/BD) \bar{z}^{-2}}{(1-\bar{z}^{-1})^2}$$

$$= \frac{1 + F/B + (AC/BD) \bar{z}^{-1} + (AE/BD - F/B - 2) \bar{z}^{-1} + (1 - AE/BD) \bar{z}^{-2}}{(1-\bar{z}^{-1})^2}$$

6.5  
(contd.)

$$\begin{aligned}
 N(z) &= \frac{(AH/BD)z^{-2} - (AG/BD)z^{-1} - (K/B)(1-z^{-1})^2}{(1-z^{-1})^2} \\
 &= \frac{(AH/BD)z^{-2} - (AG/BD)z^{-1} - (K/B)(1-2z^{-1}+z^{-2})}{(1-z^{-1})^2} \\
 &= \frac{-K/B + \left(\frac{2K}{B} - AG/BD\right)z^{-1} + (AH/BD - K/B)z^{-2}}{(1-z^{-1})^2}
 \end{aligned}$$

Hence,  $\frac{V_2(z)}{V_1(z)} = \frac{N(z)}{D(z)}$

$$\begin{aligned}
 &= \frac{-\frac{K}{B} + \left(\frac{2K}{B} - \frac{AG}{BD}\right)z^{-1} + \left(\frac{AH}{BD} - \frac{K}{B}\right)z^{-2}}{1 + \frac{F}{B} + \frac{AC}{BD}z^{-1} + \left(\frac{AE}{BD} - \frac{E}{B} - 2\right)z^{-1} + (1 - AE/BD)z^{-2}} \\
 &= \frac{KD + (AG - 2KD)z^{-1} + (KD - AH)z^{-2}}{BD + FD + (AE + AC - FD - 2BD)z^{-1} + (BD - AE)z^{-2}} \\
 &= \frac{KD + (AG - 2KD)z^{-1} + (KD - AH)z^{-2}}{(B + F)D + (AC + AE - FD - 2BD)z^{-1} + (BD - AE)z^{-2}}
 \end{aligned}$$



6.6

From Fig 6.20, in absence of L, K, F

around OA1:

$$\begin{aligned}
 V_1^{(1)} &= \frac{H}{D} \cdot \frac{\bar{z}^{-\frac{1}{2}}}{1-\bar{z}^{-1}} V_i^{(2)} - \frac{G}{D} \cdot \frac{1}{1-\bar{z}^{-1}} V_i^{(1)} - \frac{C}{D} \cdot \frac{1}{1-\bar{z}^{-1}} V_2^{(1)} - \frac{E}{D} V_2^{(1)} \\
 V_1^{(1)} &= \frac{H}{D} \cdot \frac{\bar{z}^{-1}}{1-\bar{z}^{-1}} V_i^{(1)} - \frac{G}{D} \cdot \frac{1}{1-\bar{z}^{-1}} V_i^{(1)} - \frac{C}{D} \cdot \frac{1}{1-\bar{z}^{-1}} V_2^{(1)} - \frac{E}{D} V_2^{(1)} \\
 &= \frac{\bar{z}^{-1}(H/D) - (G/D)}{1-\bar{z}^{-1}} V_i^{(1)} - \frac{C/D}{1-\bar{z}^{-1}} V_2^{(1)} - \frac{E}{D} V_2^{(1)} \\
 &= \frac{\bar{z}^{-1} \frac{H}{D} - \frac{G}{D}}{1-\bar{z}^{-1}} V_i^{(1)} - \left( \frac{E}{D} + \frac{C/D}{1-\bar{z}^{-1}} \right) V_2^{(1)} \\
 &= \frac{\bar{z}^{-1}(H/D) - G/D}{1-\bar{z}^{-1}} V_i^{(1)} - \frac{(E/D)(1-\bar{z}^{-1}) + C/D}{1-\bar{z}^{-1}} V_2^{(1)}
 \end{aligned}$$

around OA2, ignoring the  $(\phi_1), (\phi_2)$  phases (F → absent)

$$\begin{aligned}
 V_2^{(1)} &= \frac{A}{B} \frac{\bar{z}^{-\frac{1}{2}}}{1-\bar{z}^{-1}} V_1^{(2)} - \frac{I}{B} \frac{1}{1-\bar{z}^{-1}} V_i^{(1)} + \frac{J}{B} \frac{\bar{z}^{-\frac{1}{2}}}{1-\bar{z}^{-1}} V_i^{(2)} \\
 V_2^{(1)} &= \frac{(A/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} V_1^{(1)} - \frac{I/B}{1-\bar{z}^{-1}} V_i^{(1)} + \frac{(J/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} V_i^{(1)} \quad \left( \text{Using } \begin{cases} V_i^{(2)} = \bar{z}^{-\frac{1}{2}} V_i^{(1)} \\ V_1^{(2)} = \bar{z}^{-\frac{1}{2}} V_1^{(1)} \end{cases} \right) \\
 V_2^{(1)} &= \frac{(A/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} \left[ \frac{\bar{z}^{-1}(H/D) - G/D}{1-\bar{z}^{-1}} V_i^{(1)} - \frac{(E/D)(1-\bar{z}^{-1}) + C/D}{1-\bar{z}^{-1}} V_2^{(1)} \right] \\
 &\quad - \frac{I/B}{1-\bar{z}^{-1}} V_i^{(1)} + \frac{(J/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} V_i^{(1)} \\
 &= \frac{(A/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} \cdot \frac{\bar{z}^{-1}(H/D) - G/D}{1-\bar{z}^{-1}} V_i^{(1)} - \frac{I/B}{1-\bar{z}^{-1}} V_i^{(1)} + \frac{(J/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} V_i^{(1)} \\
 &\quad - \frac{(A/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} \cdot \frac{(E/D)(1-\bar{z}^{-1}) + C/D}{1-\bar{z}^{-1}} V_2^{(1)} \\
 V_2^{(1)} & \left[ 1 + \frac{(A/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} \cdot \frac{(E/D)(1-\bar{z}^{-1}) + C/D}{1-\bar{z}^{-1}} \right] \\
 &= \left[ \frac{(A/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} \cdot \frac{(H/D) \bar{z}^{-1} - G/D}{1-\bar{z}^{-1}} - \frac{I/B}{1-\bar{z}^{-1}} + \frac{(J/B) \bar{z}^{-1}}{1-\bar{z}^{-1}} \right] V_i^{(1)}
 \end{aligned}$$

6.6 (cont.)

$$V_2^{(1)} D(z) = N(z) V_1^{(1)}$$

$$D(z) = \frac{(1-z^{-1})^2 + \frac{A}{B} z^{-1} \left\{ \frac{E}{D} (1-z^{-1}) + C/D \right\}}{(1-z^{-1})^2}$$

$$= \frac{(1-z^{-1})^2 + \frac{A}{B} \frac{E}{D} z^{-1} - \frac{A}{B} \frac{E}{D} z^{-2} + \frac{A}{B} \frac{C}{D} z^{-1}}{(1-z^{-1})^2}$$

$$= \frac{1 - 2z^{-1} + z^{-2} + \left( \frac{AE}{BD} + \frac{AC}{BD} \right) z^{-1} - \frac{AE}{BD} z^{-2}}{(1-z^{-1})^2}$$

$$= \frac{1 - \left[ 2 - \left( \frac{AE}{BD} + \frac{AC}{BD} \right) \right] z^{-1} + \left( 1 - \frac{AE}{BD} \right) z^{-2}}{(1-z^{-1})^2}$$

$$N(z) = \frac{(A/B)(H/D) z^{-2} - (A/B)(G/D) z^{-1} - \frac{I/B}{1-z^{-1}} + \frac{(J/B) z^{-1}}{1-z^{-1}}}{(1-z^{-1})^2}$$

$$= \frac{(AH/BD) z^{-2} - (AG/BD) z^{-1} - (I/B)(1-z^{-1}) + (J/B) z^{-1} (1-z^{-1})}{(1-z^{-1})^2}$$

$$= \frac{(AH/BD) z^{-2} - (AG/BD) z^{-1} - (I/B) + (I/B) z^{-1} + (J/B) z^{-1} - (J/B) z^{-2}}{(1-z^{-1})^2}$$

$$= \frac{-(I/B) + (I/B - AG/BD + J/B) z^{-1} - (J/B) z^{-2} + (AH/BD) z^{-2}}{(1-z^{-1})^2}$$

$$\begin{aligned} \text{So } \frac{V_2^{(1)}}{V_1^{(1)}} &= \frac{N(z)}{D(z)} = \frac{-\frac{I}{B} + \left( \frac{I}{B} - \frac{AG}{BD} + \frac{J}{B} \right) z^{-1} + \left( \frac{AH}{BD} - \frac{J}{B} \right) z^{-2}}{1 - \left[ 2 - \left( \frac{AE}{BD} + \frac{AC}{BD} \right) \right] z^{-1} + \left( 1 - \frac{AE}{BD} \right) z^{-2}} \\ &= - \frac{DJ + [AG - D(A+J)] z^{-1} + (DJ - AH) z^{-2}}{BD + (AE + AC - 2BD) z^{-1} + (BD - AE) z^{-2}} \end{aligned}$$

6.7

Eq (6.40) is :

$$H_{22}(z) = \frac{V_2^{(1)}}{V_1^{(1)}} = - \frac{DI + [AG - D(E+J)]z^{-1} + (DJ - AH)z^{-2}}{DB + [A(C+E) - 2DB]z^{-1} + (DB - AE)z^{-2}}$$

$$= -\frac{Y}{X} \text{ (say)}$$

ie.  $\frac{Y}{X} = \frac{DI + [AG - D(E+J)]z^{-1} + (DJ - AH)z^{-2}}{DB + [A(C+E) - 2DB]z^{-1} + (DB - AE)z^{-2}}$

$$Y [DB + [A(C+E) - 2DB]z^{-1} + (DB - AE)z^{-2}] = X [DI + [AG - D(E+J)]z^{-1} + (DJ - AH)z^{-2}]$$

Let  $Y_1 = DB, Y_2 = A(C+E) - 2DB, Y_3 = (DB - AE)$   
 $X_1 = DI, X_2 = AG - D(E+J), X_3 = DJ - AH$



Then  $Y \cdot Y_1 = X (X_1 + X_2 z^{-1} + X_3 z^{-2}) - Y (Y_2 z^{-1} + Y_3 z^{-2})$

$$Y = X \left( \frac{X_1}{Y_1} + \frac{X_2}{Y_1} z^{-1} + \frac{X_3}{Y_1} z^{-2} \right) - Y \left( \frac{Y_2}{Y_1} z^{-1} + \frac{Y_3}{Y_1} z^{-2} \right)$$

$$= X \frac{X_1}{Y_1} + \left( X \frac{X_2}{Y_1} - Y \frac{Y_2}{Y_1} \right) z^{-1} + \left( X \frac{X_3}{Y_1} - Y \frac{Y_3}{Y_1} \right) z^{-2}$$

Let  $\frac{X_1}{Y_1} = B_0, \frac{X_2}{Y_1} = B_1, \frac{Y_2}{Y_1} = B_2, \frac{X_3}{Y_1} = B_3, \frac{Y_3}{Y_1} = B_4$
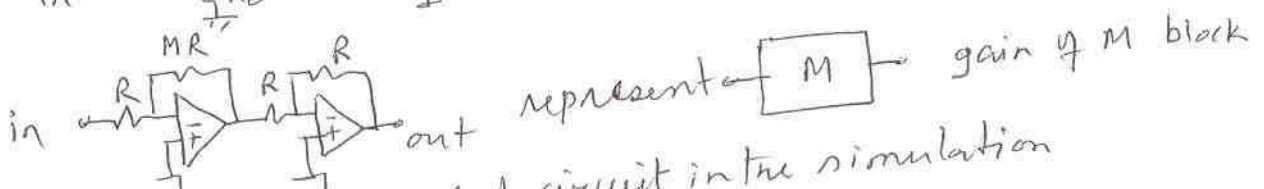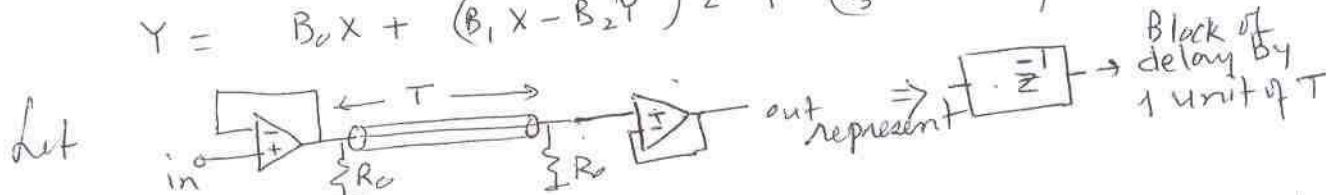
$$Y = B_0 X + (B_1 X - B_2 Y) z^{-1} + (B_3 X - B_4 Y) z^{-2}$$




Each block will be a sub circuit in the simulation program.

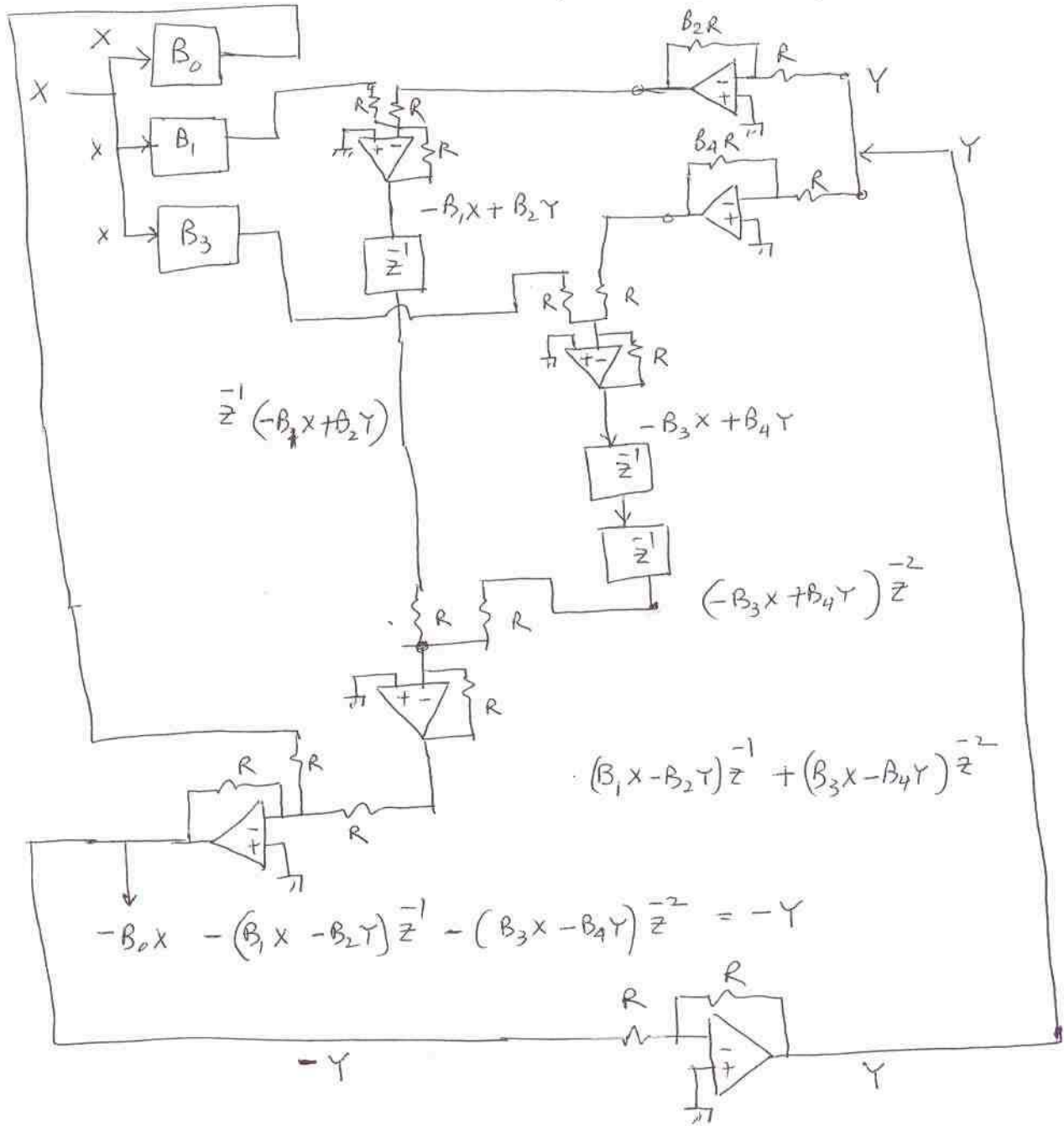6.7  
(contd.)

Consider the eqn

$$Y = B_0 X + (B_1 X - B_2 Y) z^{-1} + (B_3 X - B_4 Y) z^{-2}$$



The above represents the simulation system

6.8 For (P6.3) Given  $H(s) = \frac{0.891975 s^2 + 1.140926 \times 10^8}{s^2 + 356.0475 s + 1.140926 \times 10^8}$

$$= 0.891975 \frac{s^2 + 1.27910087 \times 10^8}{s^2 + 356.0475 s + 1.140926 \times 10^8}$$

Using  $f_s = 64 \text{ kHz}$ ,  
get (see Table 6.4)

$$H(z) = 0.8902645313 \frac{1 - 2.001691586 z^{-1} + z^{-2}}{1 - 1.966764535 z^{-1} + 1.004208024 z^{-2}}$$

For (P6.4) Given (using pre-warping, since  $f_s = 64 \text{ kHz}$  is  
not  $\gg 15 \text{ kHz}$ , the HPF cut off frequency)  
we get  $n = \text{order} = 5$ . Hence

$$H(s) = s^5 / \left[ s^5 + 396482 s^4 + 0.6504039898 \times 10^{11} s^3 + 0.9069665315 \times 10^{16} s^2 + 0.5173875291 \times 10^{21} s + 0.415936312 \times 10^{26} \right]$$

Using  $f_s = 64 \text{ kHz}$  and BLT, we will get

$$H(z) = 0.1099511628 \times 10^{11} \frac{(1 - z^{-1})^5}{D(z)}$$

$$D(z) = 0.157007829 \times 10^9 z^5 + 0.1885127413 \times 10^{11} z^4 - 0.6444713465 \times 10^{11} z^3 + 0.1171053664 \times 10^{12} z^2 - 0.1049767527 \times 10^{12} z + 0.4662020098 \times 10^{11}$$

To implement this 5<sup>th</sup> order function  
by using the structure in Fig. 6.20, we need to  
decompose  $H(z)$  as

$$H(z) = H_1(z) H_2(z) H_3(z) \text{ where}$$

$H_1, H_2$  are second order functions and  
 $H_3$  is a first order function in  $z^{-1}$ .

One can use MATLAB for the decomposition.



6.8  
with caps?

Let  $D=m, A=m$

Then  $h_D = DI$ ;  $I = \frac{h_D}{m}$

$$A_G - DI - DJ = mG - mI - mJ = m(G - I - J)$$

$$= m(G - \frac{h_D}{m} - J) = m(G - J) - h_D = h_D a_{2N}$$

$$DJ - AH = m(J - H) = h_D a_{2N}$$

$$DB = 1; D = m; B = \frac{1}{m}$$

$$AC + AE - 2DB = mC + mE - 2 = -a_{1D}$$

$$m(C+E) = 2 - a_{1D}$$

$$DB - AE = 1 - mE = a_{2D}; E = \frac{1 - a_{2D}}{m}$$

$$A = m; B = \frac{1}{m}$$

$$D = m$$

$$I = \frac{h_D}{m}$$

$$E = \frac{1 - a_{2D}}{m}$$

$$C = \frac{1 - a_{1D} + a_{2D}}{m}$$

$$m(G - J) = h_D(1 + a_{1N})$$

$$m(J - H) = h_D a_{2N}$$

$$m(C + E) = 2 - a_{1D}$$

$$mC = 2 - a_{1D} - mE = 2 - a_{1D} - 1 + a_{2D}$$

$$mC = 1 - a_{1D} + a_{2D}$$

So only  $G, J, H$  remain unknown with two eqns.

$$G - J = \frac{h_D(1 + a_{1N})}{m}$$

$$J - H = \frac{h_D a_{2N}}{m}$$

Let  $J = m$ ?

$$G - m = \frac{h_D(1 + a_{1N})}{m}$$

$$G = m + \frac{h_D(1 + a_{1N})}{m}$$

$$m - H = \frac{h_D a_{2N}}{m}$$

$$H = m - \frac{h_D a_{2N}}{m}$$

'm' should be such that all caps  $> 0$

$$m - \frac{h_D a_{2N}}{m} > 0 \quad \& \quad m + \frac{h_D(1 + a_{1N})}{m} > 0$$

6-8  
(Cont.)

Filter coefficients

$$h_D = 0.8909, \quad a_{1D} = 1.9903, \quad a_{1N} = -1.9922$$

$$a_{2D} = 0.9972, \quad a_{2N} = 1 \quad \&$$

Condition  $m = \frac{h_D a_{2N}}{m} > 0$  requires

$$m > \sqrt{h_D a_{2N}} \rightarrow \sqrt{0.8909 \times 1} \rightarrow 0.94387$$

So let  $m = 0.94387 + \alpha$

Condition  $m + \frac{h_D (1 + a_{1N})}{m} > 0$

$$m + \frac{0.8909 (1 - 1.9903)}{m} > 0$$

$$m - \frac{0.8909 \times 0.9903}{m} > 0; \quad m > \sqrt{0.8909 \times 0.9903}$$

$$m > 0.94018 \dots$$

So  $m = 0.94387 + \alpha$  will suffice both conditions

Hence  $\sum C = 5(0.94387 + \alpha) + \frac{h_D (2 + a_{1N} - a_{2N}) + 2 - a_{1D}}{(0.94387 + \alpha)}$

$$\beta = 5 \times 0.94387 = \beta + 5\alpha + \frac{0.8909 (2 - 1.9922 - 1) + 2 - 1.9903}{0.94387 + \alpha}$$

6.8  
(cont.)

$$\sum c = 5(0.94387 + d) + \frac{\ln(2 + a_{1N} - a_{2N}) + 2 - a_{1D}}{0.94387 + d}$$

$\frac{\partial}{\partial d} [\sum c] = 0$  will give a 'real' value of  $d$  provided

$$\ln(2 + a_{1N} - a_{2N}) + 2 - a_{1D} > 0.$$

In the present case, the above is not true. An alternative topology could provide the desired uni-variable optimization solution.

6.9 The transfer function in problem 5.3 is:

$$\frac{600s}{s^2 + 600s + 3 \times 10^8}$$

Thus,  $\omega_p^2 = 3 \times 10^8$ ,  $\omega_p / \zeta_p = 600$ .

Using pre-warping and BLT, the SC-transfer function for  $f_s = 120 \text{ kHz}$  is:

$$H(z) = 2.4809 \times 10^{-3} \frac{1 - z^{-2}}{1 - 1.9744 z^{-1} + 0.99504 z^{-2}}$$

Follow Example 6.3 or Example 6.4 or 6.5.

6.10 The s-domain transfer function is

$$H(s) = \frac{(\omega_p / \zeta_p) s}{s^2 + (\omega_p / \zeta_p) s + \omega_p^2} = \frac{(2\pi \times 10^4 / 10) s}{s^2 + \left(\frac{2\pi \times 10^4}{10}\right) s + (2\pi \times 10^4)^2}$$

The associated SC-TF is, for  $f_s = 100 \text{ kHz}$

$$H(z) = 0.02780182491 \frac{(1 - z^{-2})}{1 - 1.594983015 z^{-1} + 0.9443963502 z^{-2}}$$

Follow up on in P 6.9.

6.11

$$1 \text{ dB} = \text{antilog}_{10}(1/20) = 10^{0.05} = 1.122$$

$$\text{The hpf is then } H(s) = \frac{1.122 s^2}{s^2 + \frac{2\pi \times 1.2 \times 10^3}{\sqrt{2}} s + (2\pi \times 1.2 \times 10^3)^2}$$

Using  $f_s = 256 \text{ kHz}$ , the SC-TF becomes

$$H(z) = 1.110195461 \frac{1 - 2z^{-1} + z^{-2}}{1 - 1.978528770z^{-1} + 0.9793873116z^{-2}}$$

- Follow up as in P 6.9.
- Find the highest valued capacitor, say  $C_{\max}$ .  $\rightarrow$  to be 20 pF. Scale all capacitors as  $[20/C_{\max}]$  pF values.

6.12

The lpf TF is:

$$H(s) = \frac{(2\pi \times 3.4 \times 10^3)^2}{s^2 + \frac{2\pi \times 3.4 \times 10^3}{1.3} s + (2\pi \times 3.4 \times 10^3)^2}, \text{ given l.f. gain of } 0 \text{ dB}$$

The SC-TF is: (with  $f_s = 256 \text{ kHz}$ )

$$H(z) = 0.0016844 \frac{1 + 2z^{-1} + z^{-2}}{1 - 1.93116z^{-1} + 0.937902z^{-2}}$$

Follow the procedure as in P 6.11

6.13

$$\text{Notch filter in P 6.3 is } \frac{0.891975s^2 + 1.140926 \times 10^8}{s^2 + 356.0475s + 1.140926 \times 10^8}$$

Using  $f_s = 64 \text{ kHz}$ ,

$$H(z) = 0.890263 \frac{1 - 1.969014z^{-1} + z^{-2}}{1 - 1.966905z^{-1} + 0.9944904z^{-2}}$$

Use Tables 6.5, 6.6 for further work

6.14

$$T(s) = \frac{12 \times 10^6}{s^2 + 6 \times 10^3 s + 12 \times 10^6}$$

$$\text{So } \omega_p^2 = 12 \times 10^6; \quad \omega_p = \sqrt{12} \times 10^3 = 3.4641 \times 10^3$$

Let us choose  $f_s \approx 5$  times  $\omega_p = 20 \text{ kHz}$ .

We can derive  $H(z) = h_D \frac{1 + a_{1N} z^{-1} + a_{2N} z^{-2}}{1 - a_{1D} z^{-1} + a_{2D} z^{-2}}$

$$\text{So } H(z) = 0.0064795 \frac{1 + 2z^{-1} + z^{-2}}{1 - 1.714903z^{-1} + 0.7408207z^{-2}}$$

Use the method given in Example 6.3 to design the capacitances.

To simulate the 'designed' response, use these capacitance values to re-calculate the coefficients, for example,  $A, B, C, D, \dots$  (eq 6.41) and then find

$H(z)$ .

Compare using MATLAB plots the response  $|H(z)|$  and  $|T(s)|$ .

6.15 In P.6.3

$$H(z) = 0.8909255285 \frac{1 - 1.992198066z^{-1} + z^{-2}}{1 - 1.990275499z^{-1} + 0.9972254644z^{-2}}$$

Using realizations of DA1, DA2, D networks (see eq. 6.55)

$$h_D = \frac{1}{(1 + C_{1N}/C_{IN})(1 + C_{2D}/C_{ID})}$$

$$a_{1N} = \frac{C_{1N}}{C_{IN}}, \quad a_{2N} = \frac{C_{2N}}{C_{IN}}$$

$$a_{1D} = \frac{C_{1D}}{(C_{2D} + C_{ID})}; \quad a_{2D} = \frac{C_{2D}}{C_{2D} + C_{ID}}$$

$$\text{Let } h_D' = \sqrt{0.8909255285} = 0.943888514868$$

$$1/h_D' = 1.05944715318 \rightarrow (1.02929449293)^2$$



6.15  
(cont.)

We can let

$$\frac{C_{0N}}{C_{1N}} = 0.293 = \frac{C_{0D}}{C_{1D}}$$

So that  $h_D = \frac{1}{(1.0293)^2} \approx 0.94387$  is realized

If  $C_{0N} = C_{0D} = 1 \text{ PF}$ ,  $C_{1N} = C_{1D} = 31.1296 \approx 31.13 \text{ PF}$ .

Then  $a_{1N} \approx 1.992 = \frac{C_{1N}}{C_{2N}}$ ;  $C_{1N} = 1.992 \times 31.13 = 62.01 \text{ PF}$ .

$a_{2N} = 1$ ;  $C_{2N} = C_{1N} = 31.13 \text{ PF}$ .

$a_{1D} = \frac{C_{1D}}{C_{0D} + C_{1D}} \approx 1.99 = \frac{C_{1D}}{C_{0D} + 31.13}$ ; ~~Let  $C_{1D} = 1 \text{ PF}$ .~~

~~Then  $\frac{C_{1D}}{C_{0D} + 31.13} = \frac{1}{1.99} = 0.5025$ ;  $C_{1D} = (C_{0D} + C_{1D}) \times 1.99 = 32.13 \times 1.99$ , assuming  $C_{0D} = 1 \text{ PF}$~~

$C_{1D} = (C_{0D} + C_{1D}) \times 1.99 = 32.13 \times 1.99$ , assuming  $C_{0D} = 1 \text{ PF}$

$C_{1D} = 63.94 \text{ PF}$ .

$C_{2D} = 32.13 \times 0.9972 = 32.04 \text{ PF}$ .

$C_{2D} = \frac{C_{2D}}{C_{0D} + C_{1D}} = 0.9972$ ;

So the design capacitances are:

$C_{0N} = C_{0D} = 1 \text{ PF}$ ;  $C_{1N} = 62.01 \text{ PF}$ ;  $C_{2N} = 31.13 \text{ PF}$ .

$C_{1N} = C_{1D} = 31.13 \text{ PF}$ ;  $C_{1D} = 63.94 \text{ PF}$ ;  $C_{2D} = 32.04 \text{ PF}$ .

For 6.4, we have

$$H(z) \approx \frac{0.10995 \times 10^{11} (1 - z^{-1})^5}{D(z)}$$

$$D(z) \approx 0.1570078 \times 10^9 z^5 \dots \text{etc.}$$

Factor  $D(z)$  in  $D_1(z) D_2(z) D_3(z)$  where  $D_1, D_2$  are of second order while  $D_3$  is of order 1.

Then decompose  $H(z)$  as  $h_1 \frac{(1 - z^{-1})^2}{D_1(z)} \cdot h_2 \frac{(1 - z^{-1})^2}{D_2(z)} \cdot h_3 \frac{1 - z^{-1}}{D_3(z)}$

Realize the sub-functions  $h_1 \frac{(1 - z^{-1})^2}{D_1(z)}$ ,  $h_2 \frac{(1 - z^{-1})^2}{D_2(z)}$  ...

as above (using DA1, DA2, D SCF-networks)

6.16

In 6.12 we had

$$H(z) = 0.0016844 \frac{1 + 2z^{-1} + z^{-2}}{1 - 1.93116z^{-1} + 0.937902z^{-2}}$$

In terms of the CDA network

$$H(z)|_{\text{CDA}} = \frac{A_1 + A_2 z^{-1} + A_3 B_3 z^{-2}}{1 - A_3 B_1 z^{-1} + A_3 B_2 z^{-2}}$$

$$\text{Then } A_1 = 0.0016844, \quad A_2 = 2A_1; \quad A_3 = A_1$$

$$A_3 B_1 = 1.93116; \quad A_3 B_2 = 0.937902$$

Design capacitances are given by

$$A_1 = \frac{C_1}{C_1 + C_{S1}}; \quad A_2 = \frac{C_2 C_{S1}}{C_{O1}(C_1 + C_{S1})}; \quad A_3 = \frac{C_3 C_{S1}}{C_{O1}(C_1 + C_{S1})}$$

$$B_1 = \frac{C_4}{C_4 + C_{S2}}; \quad B_2 = \frac{C_5 C_{S2}}{C_{O2}(C_4 + C_{S2})}; \quad B_3 = \frac{C_6 C_{S2}}{C_{O2}(C_4 + C_{S2})}$$

Six equations, ten capacitances; so 4 free choices possible.

$$\text{Let } C_1 = 1 \text{ pF. , then } C_{S1} = \frac{1}{A_1} - C_1 = 592.68 \text{ pF.}$$

$$A_2 = 2 \times 0.0016844 = \frac{C_2}{C_{O1}} \cdot \frac{592.68}{593.68}$$

$$\text{If we let } C_2 = 1 \text{ pF. , } C_{O1} = \frac{592.68}{593.68} \cdot \frac{1}{2 \times 0.0016844} = 296.34 \text{ pF.}$$

$$A_3 = 0.0016844 = \frac{C_3}{C_{O1}} \cdot \frac{C_{S1}}{C_1 + C_{S1}} = \frac{C_3}{296.34} \cdot \frac{592.68}{593.68}; \quad C_3 = 0.5 \text{ pF.}$$

confirm this way. & use capacitance scaling to bring  $C_{\min} = 1 \text{ pF.}$

\* \* Design impossible! Since  $B_1 < 1$  while by the numbers

$$A_3 B_1 = 1.93116 \quad \text{and} \quad A_3 = 0.0016844, \quad B_1 \gg 1.$$