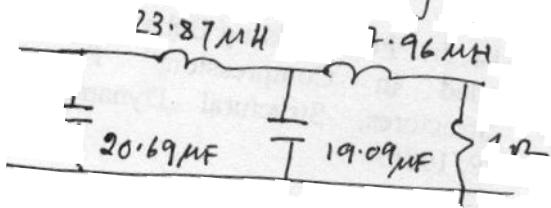


Q1: (a)

1/6

Using frequency scaling by  $\alpha = 2\pi \times 10^9 \text{ rad/s}$




$$1.3F \rightarrow \frac{1.3}{2\pi \times 10^9} F$$

$$1.5H \rightarrow \frac{1.5}{2\pi \times 10^9} H.$$

R → does not change

Using impedance scaling by 75
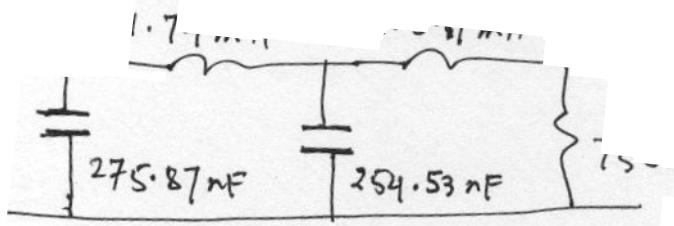
$$C \rightarrow C/75, \quad L \rightarrow L \times 75; \quad R \rightarrow R \times 75$$



is the Final Circuit

(b) For hpf we apply component transformation first

Thus  $\frac{1}{L_i} \rightarrow \frac{C_i}{L_i}, \quad C_i = \frac{1}{L_i \omega_{ch}}; \quad \omega_{ch} = 2\pi \times 400 \text{ rad/s}$

$$\frac{1}{C_j} \rightarrow \frac{1}{L_j}, \quad L_j = \frac{1}{C_j \omega_{ch}}$$

Thus:  $1.3F \rightarrow \text{inductance } L_j = \frac{1}{1.3 \times 2\pi \times 400} = 0.308 \text{ mH}$

$$1.2F \rightarrow 0.331 \text{ mH}$$


$$1.5H \rightarrow C_i = \frac{1}{1.5 \times 2\pi \times 400} = 265.26 \mu\text{F}$$

$$0.5H \rightarrow = 795.77 \mu\text{F}$$

Q1 (b)


First cut

2/6

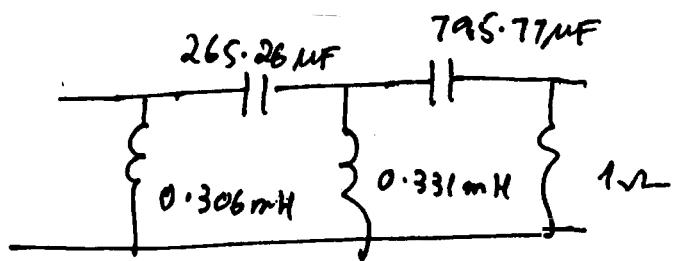

For  $100\ \Omega$  termination, use impedance scaling
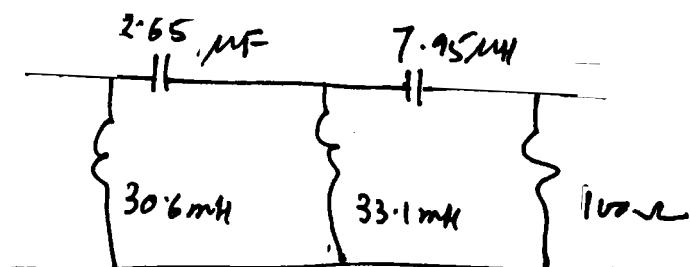
$$L \rightarrow 100 \times L, C \rightarrow C/100, R \rightarrow R \times 100 -$$



Final answer

Q2:

At the passband edge,  $\omega_n = 1$   $A_p = 1 \text{ dB}$

$$\therefore \epsilon = \sqrt{10} - 1 = \sqrt{0.2589} = 0.5088$$

$$(a) |H_N(j\omega_n)|^2 = \frac{1}{1 + 0.5088^2 \omega_n^{2m}} = \frac{1}{1 + 0.2589 \omega_n^{2m}}$$

$$\text{At } f = 10 \text{ kHz}, \quad \omega_n = \frac{10}{1} = 10$$

$$|H_N(j\omega_n)|^2 = \frac{1}{1 + 0.2589 \times 10^{10}} \quad m = \text{order} = 5$$

$$\approx \frac{10^{-10}}{0.2589}$$

$$20 \text{ dB} \rightarrow 10 \log_{10} \left| \frac{1}{1} \right|^2 = -100 \text{ dB} - 10 \log_{10} \frac{0.2589}{94.13} \\ = -100 + 5.87 =$$

$$\text{Attenuation} = -94.13 \text{ dB} \quad \underline{\text{Ans}}$$

$$(b) \text{ Now } 10 \log_{10} |H_N(j\omega_n)|^2 = -40 \text{ at } \omega_n = 40 = \frac{40k}{1k}$$

$$10 \log_{10} \left[ \frac{1}{1 + 0.2589 \times (40)^{2m}} \right] = -40$$

$$-10 \log_{10} [1 + 0.2589 \times (40)^{2m}] = -40 \quad \log_{10} 1 = 0$$

$$10^4 = 1 + 0.2589 \times (40)^{2m}; \quad 0.2589 \times (40)^{2m} \approx 10^4$$

$$(40)^{2m} = \frac{10^4}{0.2589} = 38.6249 \times 10^3$$

$$2m \log_{10}(40) = \log_{10} (38.6249 \times 10^3) = 4.5869$$

$$m = \frac{4.5869}{2 \times 1.6020} = 1.43 \rightarrow 2 \text{ order} \quad \underline{\text{Ans}}$$

Q.3

Passband ripple implies a CHEB approximation  
 $A_p = 0$  and leads to  $\epsilon = 0.3403$

$$D = \frac{10^{14} - 1}{10^{14} - 1} = \frac{10^{3.5} - 1}{\epsilon^2} = 25908.2$$

4/6

$$\frac{\omega_a}{\omega_c} = \frac{15}{7.8} = \omega_s = 1.923$$

$$\sqrt{D} = 160.96$$

$$\cosh^{-1}(160.96) = 5.77 ; \cosh^{-1}(1.923) = 1.271$$

$$\text{Order of filter} > \frac{\cosh^{-1}\sqrt{D}}{\cosh^{-1}(\omega_s)} = 4.539 \rightarrow 5$$

The normalized IIR transfer function is

$$H_N(s) = \frac{1}{\frac{s-1}{2\epsilon}} = \frac{1}{s^5 + 1.17251s^4 + 1.9374s^3 + 1.3096s^2 + 0.7525s + 0.1789}$$


For the HPF with  $\omega_{CH} = 15 \times 10^3 \times 2\pi / 12\pi$ , frequency de-normalized transfer function will be:

$$H(s) = \left[ \frac{0.1789}{\left( \frac{2\pi \times 15 \times 10^3}{s} \right)^5 + 1.1725 \left( \frac{2\pi \times 15 \times 10^3}{s} \right)^4 + 1.9374 \left( \frac{2\pi \times 15 \times 10^3}{s} \right)^3 + 1.3096 \left( \frac{2\pi \times 15 \times 10^3}{s} \right)^2 + 0.7525 \left( \frac{2\pi \times 15 \times 10^3}{s} \right) + 0.1789} \right]$$

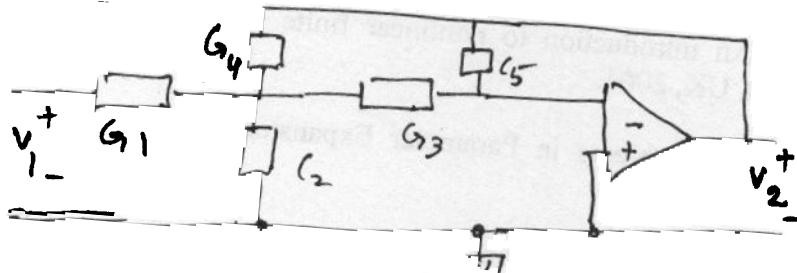Q9

5/6

The given circuit is a LPF using infinite gain voltage amplifier if can be compared with



Thus,

$$\begin{aligned} R_1 &\rightarrow G_1 \\ C_1 &\rightarrow C_2 \\ R_2 &\rightarrow G_4 \\ R_3 &\rightarrow G_3 \\ C_2 &\rightarrow C_5 \end{aligned}$$

Design guidelines for these are given in  
Table 4.3

$$\frac{E_2}{E_1} = \frac{G \omega_0^2}{s^2 + \left(\frac{\omega_0}{\alpha}\right)s + \omega_0^2}$$

Can be compared with

$$\frac{V_2}{V_1} = \frac{H}{s^2 + \left(\frac{\omega_p}{\alpha_p}\right)s + \omega_p^2}$$

$$H = G \omega_0^2 \quad - \quad \omega_0 \equiv \omega_p, \quad \alpha \equiv \alpha_p$$

From given data  $H = 5 \omega_0^2 = 5$   $\omega_0^2 = 1$  given  $= b_0$

$$b_1 = \frac{\omega_0}{\alpha} = \frac{\omega_p}{\alpha_p} = 1 \cdot 2 = \frac{1}{\alpha_p}$$

$$\alpha_p = \frac{1}{1 \cdot 2} = 0.833$$

Let's use the design guidelines

Q4)

(contd.)

$$G_1 = \frac{1}{\omega_p} = \frac{5}{1} = 5 \quad \text{So } R_1 = \frac{1}{5} = 0.2 \Omega$$

6/6

$$G_2 = \frac{\alpha_p (2\omega_p^2 + H)}{\omega_p^2} = \frac{0.833 (2+5)}{1} = 5.831 \text{ F}$$

Thm  $C_2 = \frac{5.831 \text{ F}}{1}$  in the given circuit

$$G_3 = \omega_p = 1 \quad \text{So } R_3 = G_3 = 1 \Omega \text{ in the given circuit}$$

$$G_4 = G_3 = 1, \quad R_2 = 1 \Omega \quad \text{in the given circuit}$$

$$C_5 = \frac{\omega_p^2}{\alpha_p (2\omega_p^2 + H)} = \frac{1}{5.831} = 0.1715 \text{ F}$$

$$C_5 \rightarrow C_2 = 0.1277 \text{ F} \quad \text{in the given circuit}$$

Hence :

$$R_1 = 0.2 \Omega$$

$$R_2 = 1 \Omega$$

$$R_3 = 1 \Omega$$

$$C_1 = 5.831 \text{ F}$$

$$C_2 = 0.1715$$

}

needed  
design  
values

$$\text{Prof. } \frac{1}{R_2 R_3 C_1 C_2} = \frac{1}{1 \cdot 1 \cdot 5.831 \times 0.1715} \approx 1 = b_0 = \omega_0^2$$

$$\frac{1}{C_1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{1}{5.831} (5+1+1) \approx 1.2 = b_1$$

$$\frac{1}{R_1 R_3 C_1 C_2} = \frac{1}{0.2} \cdot \frac{1}{1} \cdot \frac{1}{1} = 5 = 4 b_0$$