

# Table of Contents

<b>Table of Contents</b> .....	<b>i</b>
<b>List of Figures</b> .....	<b>ii</b>
<b>List of Tables</b> .....	<b>ii</b>
<b>1. Introduction</b> .....	<b>3</b>
<b>2. Basic theory of transfer functions</b> .....	<b>2</b>
2.1 Design of Low-pass transfer Function .....	2
2.2 Design of Band-Pass Filter .....	6
2.3 Design of Operational Simulation Principle .....	7
<b>3. Design equations &amp; Calculations used for giveg specifications</b> .....	<b>8</b>
3.1 Cascaded Second-Order RC Active Filter .....	8
3.2 Cascaded Second-Order OTA-C Active Filter .....	10
3.3 Operational Simulation Principle .....	11
<b>4. Schematic of final network</b> .....	<b>14</b>
4.1 Cascaded Second-Order RC Active Filter .....	14
4.2 Cascaded Second-Order OTA-C Active Filter .....	15
4.3 Three stage Operational Simulation Principle Network .....	16
<b>5. Numerical simulation with matlab</b> .....	<b>17</b>
<b>6. Simulation results using pspice</b> .....	<b>19</b>
6.1 Cascaded Second-Order RC Active Filter .....	19
6.2 Cascaded Second-Order OTA-C Active Filter .....	20
<b>Appendix A: MATLAB Code</b> .....	<b>A-1</b>
<b>References</b> .....	<b>1</b>

## List of Figures

---

Figure 1 – BPF Response .....	6
Figure 2 – Low-Pass Filter for Operational Simulation Principle .....	11
Figure 3 – Conversion of LP to BPF , .....	12
Figure 4 – Second-Order RC Active Filter .....	14
Figure 5 – Second- Order RC Active Filter with Practical Values.....	15
Figure 6 – Second-Order OTA-C Active Filter .....	15
Figure 7 – Three stage Operational Simulation Principle network .....	16
Figure 8 – Real part of TF .....	18
Figure 9 – Imaginary part of TF .....	18
Figure 10 – Second-Order RC Active Filter Response .....	19
Figure 11 – Second order RC Active Filter Response with Practical Values.....	20
Figure 12 – Second-Order OTA-C Active Filter Respose .....	20

## List of Tables

---

Table 1 – Variables of $D(s)$ .....	3
Table 2 – Comparison between theoretical and experimental .....	14
Table 3 – Matlab code for TF .....	17

## 2. BASIC THEORY OF TRANSFER FUNCTIONS

We are asked to design a band-pass filter (BPF). First we found the format of transfer function (TF) of BPF as it is shown below:

$$\frac{V_2(s)}{V_1(s)} = H(s) = \frac{H_0(\omega_p/Q_p)s}{s^2 + (\omega_p/Q_p)s + \omega_p^2} \quad (1.1)$$

*Planned eqn ref ?*

In this formula  $\omega_p$  is a pole frequency and  $Q_p$  is a pole-Q of a filter. To design such a filter we have to follow the steps shown below:

### 2.1 Design of Low-pass transfer Function

The base of all kind of filters are low-pass filter, so for designing a band-pass filter we have to start by designing a low-pass filter.

We are given the specifications for band-pass filter. However, we have to find other unknown values.

$$\omega_s = \omega_a / \omega_c = (\Omega_{a2} - \Omega_{a1}) / (\Omega_{p2} - \Omega_{p1}) \quad (1.2)$$

$$\Omega_0 = \sqrt{\Omega_{a2} * \Omega_{a1}} = \sqrt{\Omega_{p2} * \Omega_{p1}} \quad (1.3)$$

$$\Omega_0 = \sqrt{12000 * \Omega_{a1}} = \sqrt{4000 * 1000}$$

$$\Omega_0 = \sqrt{12000 * \Omega_{a1}} = 2000$$

$$\Omega_{a1} = 333.33$$

Now that we have  $\Omega_{a1}$  we can find the order of our filter.

Because in the design we are asked to design a chebyshev we have to follow the formula for chebyshev.

$$D = (10^{0.1A_p} - 1) / (10^{0.1A_p} - 1) \quad (1.4)$$

$$D = (10^3 - 1) / (10^{0.05} - 1) = 8187.286$$

$$n = (\cosh^{-1} \sqrt{D}) / (\cosh^{-1}(\frac{\omega_s}{\omega_c})) \quad (1.5)$$

$$n = \cosh^{-1} \sqrt{8187.286} / \cosh^{-1} 3.889$$

$$n = 2.55 \rightarrow n = 3$$

*Scanned,  
Copied &  
passed  
mark?*

where  $\omega_s$  was found from equation (1.2):

$$\omega_s = (12000 - 333.33) / (4000 - 1000)$$

$$\omega_s = 3.889 \text{ rad/sec}$$

At this point we have all the specification that we need for designing a chebyshev low-pass filter.

$$H_N(s) = \left( \frac{1/e^{2n-1}}{s^2 + a_1 s^2 + a_2 s + a_3} \right) \quad (1.6)$$

Variables  $a_1$ ,  $a_2$  and  $a_3$  are taken from table A.2 from Prof. Raut book.

$a_1$	$a_2$	$a_3$
1.2353	1.535	0.716

Table 1 – Variables of D(s)

$$H_N(s) = \frac{0.716}{s^2 + 1.2353s^2 + 1.535s + 0.716}$$

The low-pass transfer function of H(s) is:

## 3. DESIGN EQUATIONS & CALCULATIONS USED FOR GIVEG SPECIFICATIONS

### 3.1 Cascaded Second-Order RC Active Filter

In this design we use Infinite Gain from table 4.3 in Prof. Raut book. The calculation of this design is shown below:

$$\frac{1878s}{s^2 + 1878s + 4 \cdot 10^3}$$

$$H = 1878$$

$$\omega p = 2 \cdot 10^3$$

$$Qp = \frac{\omega p}{1878} = 1.065$$

$$G1 = H = 1878$$

$$G2 = 2\omega p Qp - H = 2(2 \cdot 10^3)(1.065) - 1878 = 2382$$

$$C3 = C4 = 1F$$

$$G5 = \frac{\omega p}{2Qp} = 939$$

$$R1 = \frac{1}{1878} = 0.0005\Omega$$

$$R2 = \frac{1}{2382} = 0.0004\Omega$$

$$R5 = \frac{1}{939} = 0.0011\Omega$$

$$a = 10^6$$

$$R1_{new} = aR1 = 500\Omega$$

$$R2_{new} = aR2 = 400\Omega$$

$$R5_{new} = aR5 = 1100\Omega$$

$$C1_{new} = \frac{C}{10^6} = \frac{1}{10^6} = 10^{-6}F = 1\mu F$$

$$C2_{new} = \frac{C}{10^6} = \frac{1}{10^6} = 10^{-6}F = 1\mu F$$

*This is not identical with the expression on p. 6 of this report. Why did you change?*

*Three are different TF from p6 expression*

$$H_2(s) = \frac{(3.2059 \cdot 10^3)s}{s^2 + 361.5718s + 9.5375 \cdot 10^3} = \frac{-Hs}{s^2 + \frac{\omega p}{Qp} + \omega p^2}$$

$$H = 3.2059 \cdot 10^3$$

$$\omega p^2 = 976.6(\text{rad} / \text{sec})$$

$$Qp = \frac{\omega p}{361.5718} = 2.7$$

$$G1 = H = 3.2059 \cdot 10^3$$

$$G2 = 2\omega p Qp - H = 2(976.6)(2.7) - 3.2059 \cdot 10^3 = 2387.74$$

$$G5 = \frac{\omega p}{2Qp} = 180.78$$

$$R1 = 312 \cdot 10^{-6}$$

$$R2 = 484 \cdot 10^{-6}$$

$$R5 = 5531 \cdot 10^{-6}$$

$$C3 = C4 = 1F$$

$$a = 10^6$$

$$R1_{new} = aR1 = 312\Omega$$

$$R2_{new} = aR2 = 484\Omega$$

$$R5_{new} = aR5 = 5531\Omega$$

$$C3_{new} = \frac{C}{10^6} = \frac{1}{10^6} = 10^{-6}F = 1\mu F$$

$$C4_{new} = \frac{C}{10^6} = \frac{1}{10^6} = 10^{-6}F = 1\mu F$$

$$T_3(s) = \frac{3.2059 * 10^3 s}{s^2 + 1.5164 * 10^3 s + 1.6776 * 10^7} = \frac{H \frac{\omega p s}{Qp}}{s^2 + \frac{\omega p}{Qp} + \omega p^2}$$

$$\omega p = 4.096 * 10^3 \text{ (rad / sec)}$$

$$\frac{\omega p}{Qp} = 1.5164 * 10^3$$

$$H = \frac{3.2059 * 10^3}{1.5164 * 10^3} = 2.114$$

$$\text{Let } C_1 = C_2 = 100 \mu F = C \quad \& \quad g_{m1} = g_{m2} = g_m$$

$$\omega p = \frac{g_m}{C} \rightarrow g_m = 409.6 m$$

$$\frac{g_{m3}}{C} = \frac{\omega p}{Qp} \rightarrow g_{m3} = 151.64 m$$

$$H = \frac{g_{m4}}{g_{m3}} = 2.114 \rightarrow g_{m4} = 320.567 m$$

$$C_1 = C_2 = 100 \mu F$$

$$g_{m1} = g_{m2} = 409.6 m$$

$$g_{m3} = 151.64 m$$

$$g_{m4} = 320.569 m$$

*Tabulate the values!*

### 3.3 Operational Simulation Principle

To complete the final circuit, we have to follow the steps that are described below:

Step 1)

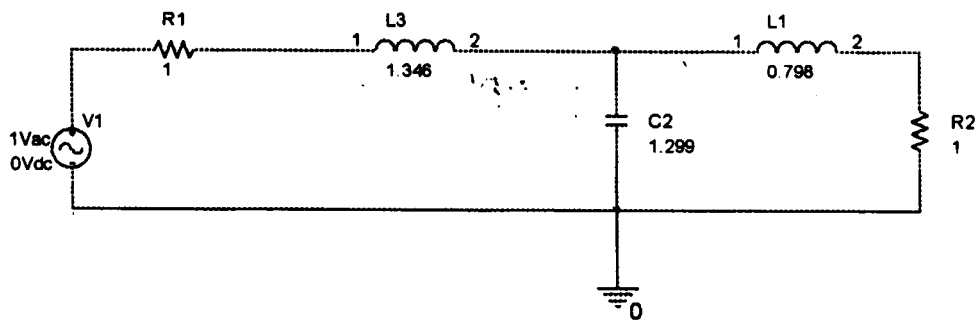


Figure 2 – Low-Pass Filter for Operational Simulation Principle

Step 2) In this step, we have to denormalize the above circuit.

Unclear  
steps  
& procedure  
shown with  
diagram

$$Y_1(s) = \frac{1}{Z(s)} = \frac{1}{R_1 + sL_1 + \frac{1}{sC_{p1}}}$$

$$t_y(s) = R_p Y(s) = \frac{1}{\frac{R_1}{R_p} + \frac{sL_1}{R_p} + \frac{1}{sC_{p1}R_p}} = \frac{1}{1 + s718.4 \cdot 10^{-6} + \frac{1}{s(923.2 \cdot 10^{-6})}}$$

$$Z_2(s) = \frac{1}{sC_{p2} + \frac{1}{L_2s}}$$

$$-t_z(s) = \frac{-Z(s)}{R_p} = \frac{1}{sC_{p2}R_p + \frac{R_p}{L_2s}} = \frac{1}{s(928 \cdot 10^{-6}) + \frac{1}{s(923.2 \cdot 10^{-6})}}$$

$$Y_3(s) = \frac{1}{R_1 + sL_3 + \frac{1}{sC_{p3}}}$$

$$t_y(s) = R_p Y_3(s) = \frac{1}{\frac{R_3}{R_p} + \frac{sL_3}{R_p} + \frac{1}{sC_{p3}R_p}} = \frac{1}{1 + s425.6 \cdot 10^{-6} + \frac{1}{s(1504 \cdot 10^{-6})}}$$

## 5. NUMERICAL SIMULATION WITH MATLAB

We use Matlab to draw the transfer function of our design. The Matlab code is shown in the table below.

```

i=[100:10:5000];
r=zeros(size(i));

s=complex(r,i);
n=((1878*s).*(3.2059e3*s).*(3.2059e3*s));
d=((s.^2+1878*s+4e6).*(s.^2+361.5718*s+9.5375e5).*(s.^2+1.5164e3*s+1.6776e7));
hs=n./d;
figure(1);plot(real(hs));
figure(2);plot(imag(hs));

```

*You need to calculate the coefficients with practical R, C values inserted*

Table 3 – Matlab code for TF

*You got to do it for each case*

- 1) Active RC
- 2) OTA-C
- 3) OP-simulation with the designed component values.



## 6. SIMULATION RESULTS USING PSPICE

### 6.1 Cascaded Second-Order RC Active Filter

In our specification, we were supposed to get a bandwidth of 3000Hz; however, we did not observe that. If we change the value of the capacitors or we did frequency scaling, we could expect a better result.

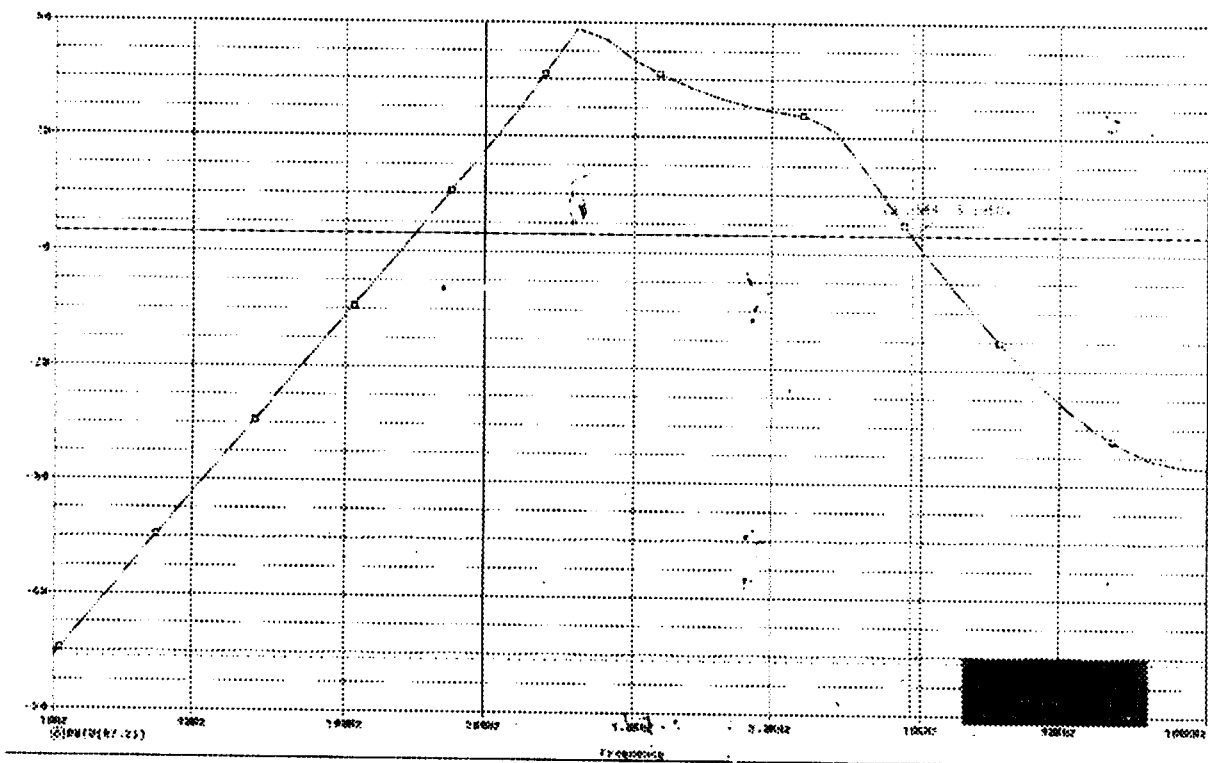


Figure 10 – Second-Order RC Active Filter Response