

## Experiment 4

### Comparison of frequency response of Common-Emitter (CE) and Common-Base (CB) amplifiers

**Objective** – Measure the frequency response of CE and CB amplifiers.

**Introduction** – An amplifier has a frequency-dependant gain. In the mid-band region the gain is largest and at lower frequency the gain starts to decrease. The point at which the gain reduces to 71% of the highest value is called the lower 3dB point ( $f_L$ ). At high frequencies the gain also goes down and the point where the gain is reduced to 71% of the highest value is called the upper 3dB point ( $f_H$ ).


The mid-band gain for a CE amplifier is given by the expression  $A_v = -g_m R_C / R_L$ . Here,  $R_C$  and  $R_L$  are collector and load resistance, respectively. The negative sign in the gain indicates that the input and output are out of phase.

The mid-band gain for a CB amplifier is given by the expression  $A_v = g_m R_C / R_L$ . Here, the gain is same as the case of the CE configuration except for the negative sign.

The lower 3 dB frequency is determined by coupling and bypass capacitors. The upper 3 dB frequency is determined by the internal capacitance of the BJT. These capacitors arise because of junction capacitors. More specifically, these capacitors are emitter-base capacitance ( $C_{\pi}$ ) and collector-base capacitance ( $C_{\mu}$ ). The expression of gain for mid-band region ( $A_v$ ) is no longer correct because the small-signal model for the BJT includes junction capacitors such as  $C_{\mu}$  and  $C_{\pi}$ . In this experiment we would like to see the frequency response of CE and CB amplifiers through simulation and then actual measurement.

**Experimental Procedure** –

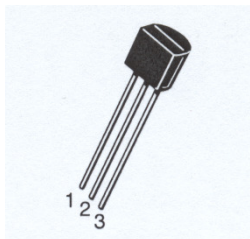**CE amplifier (Measurement)** – Assemble the circuit in Fig.2 on the circuit-board using BJT P2N2222A. The pin-out for this BJT is shown in Fig. 1.



Pin No.	P2N2222A BJT
1	Collector
2	Base
3	Emitter

Fig. 1

In Fig. 2  $V_{in}$  should be replaced with a Function Generator with input as a sine wave.  $V_{in}$  (p-p) should be in around 40mV.

1. Using the DMM, measure  $V_C$ . From this measurement calculate  $I_C$  and then  $g_m$  ( $g_m = I_C/25mV$ ). This information will be useful in answering questions.
2. Measure  $V_E$  and then calculate  $V_{CE} = V_C - V_E$ . This value should be greater than 0.3V so that the BJT is in the active mode. This is a necessary requirement for amplifier action.
3. Set the function generator to frequency,  $f=1$  kHz,  $V_{in}$  (p-p) =40 mV and  $V_{OFF} = 0$ . In the oscilloscope observe  $V_{in}$  and  $V_{out}$  simultaneously. Note down the phase relationship between input and the output.
4. Now do a “ $V_{out}$  vs.  $f$ ” measurement. Be prepared to reduce  $V_{in}$  (p-p) if the output saturates. On the other hand you could increase it if the output signal is noisy. The frequency  $f$  is given on the Function Generator while  $V_{out}$  is found from the oscilloscope. Start at  $f=30$  Hz and increase it by a factor of 3 (Approximately). For example, you could go for  $f = 30$  Hz, 100Hz, 300Hz, 1 kHz, 3 kHz etc. You should cover (i.e. exceed) the frequency range that gives you  $f_L$  and  $f_H$ .
5. Plot Gain ( $G_v$ ) vs.  $f$  on a semi-log graph. Determine  $f_L$  and  $f_H$ .

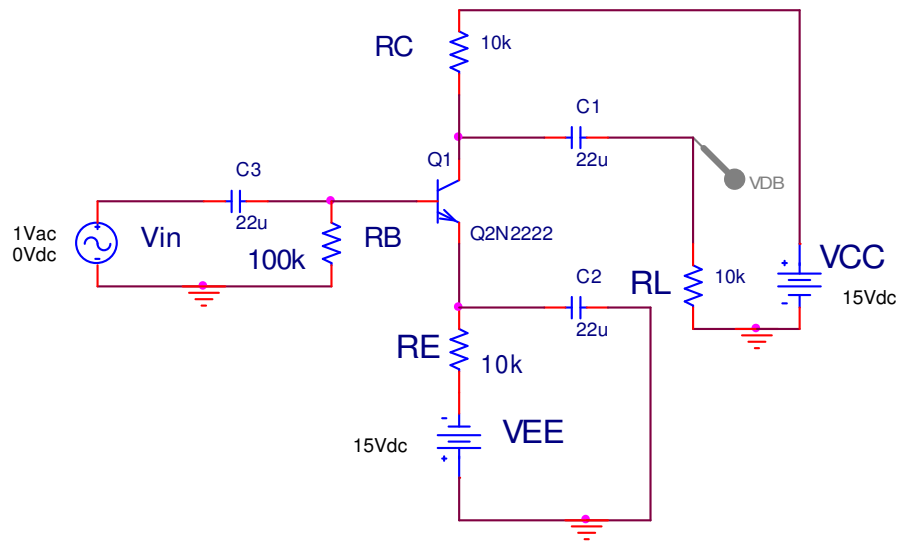


Fig. 2

**CB amplifier (Measurement)** - Assemble the circuit in Fig.3. In Fig.3  $V_{in}$  should be replaced with the Function Generator, where the input should be  $V_{in}(p-p)$  should be in around 40mV.

Repeat steps 1-5 from above.

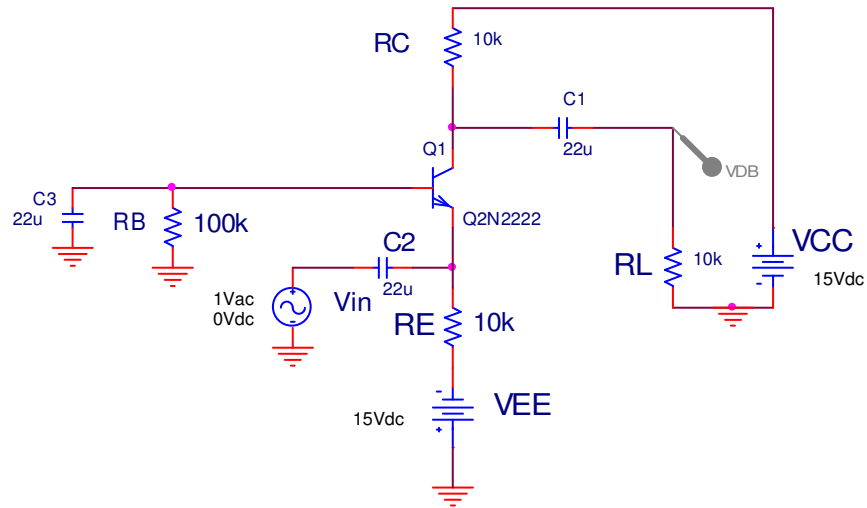


Fig. 3

**Questions –**

1. Comment on the mid-band gains obtained for the CE and CB amplifiers obtained by simulation. If they are very different (more than 10%) explain why?
2. Provide the mid-band gains obtained for the CE and CB amplifiers obtained by lab bench work. If they are very different (more than 10%) explain why?
3. Comment on the phase relation of the signals at the output and input for the CE and CB amplifiers (use the lab bench results).
4. Do the  $f_H$  values of the CE and CB amplifiers differ in the lab bench work? If yes, why?
5. What is the role of the transistor ‘beta’ ( $h_{fe}$ ) on the values of (i)  $f_L$ , (ii)  $f_H$ ? Justify by proper analysis. Consider only the CE amplifier.
6. What is the role of the transistor ‘ $g_m$ ’ on the values of (i)  $f_L$ , (ii)  $f_H$ ? Justify by proper analysis. Consider only the CE amplifier.