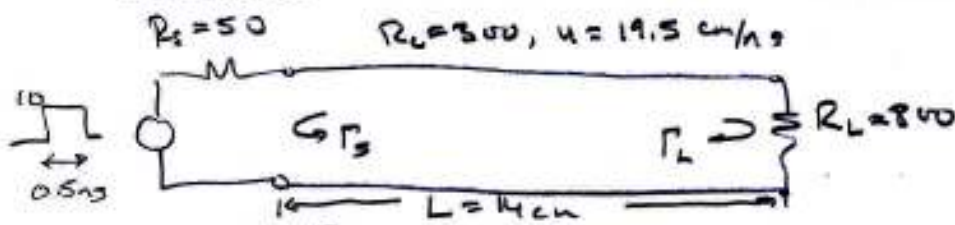


ELEC351 Class Test Solution – 2007

SOLUTION



(1)


$$V(0) = \frac{V_s R_L}{R_s + R_L} = \frac{10 \times 800}{300 + 50} = 8.57 \text{ volts}$$

$$T = \frac{L}{u} = \frac{4}{19.5} = 0.718 \text{ ns}$$

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = \frac{800 - 300}{800 + 300} = 0.455$$

$$\Gamma_s = \frac{R_s - Z_0}{R_s + Z_0} = \frac{50 - 300}{50 + 300} = \frac{-250}{350} = -0.714$$

1)

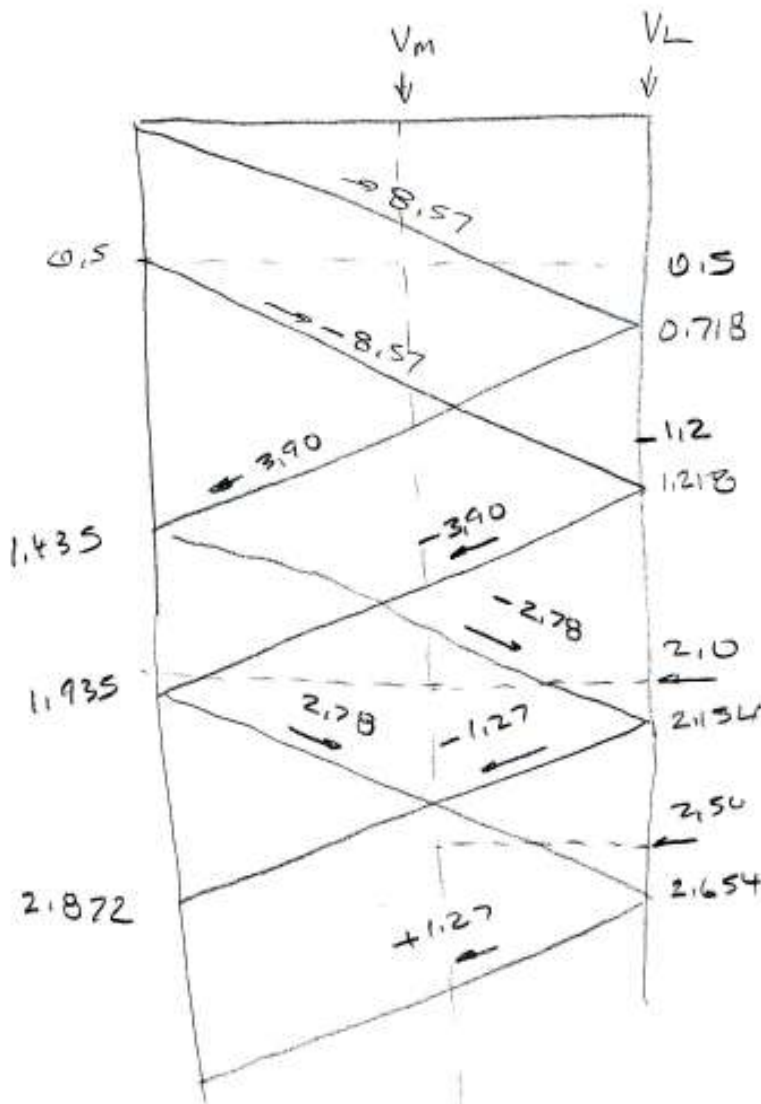

(2)

11) V_M at 0.5 ns

$$V_M = 8.57 \text{ V. } \textcircled{a}$$

112) V_L at 1.12 ns


$$V_L = 8.57 + 3.90 = 12.47 \text{ V. } \textcircled{d}$$

113) V_M at 2.10 ns

$$V_M = (+8.57 - 8.57) + (3.90 - 3.90) - 2.78 = -2.78 \text{ volts } \textcircled{b}$$

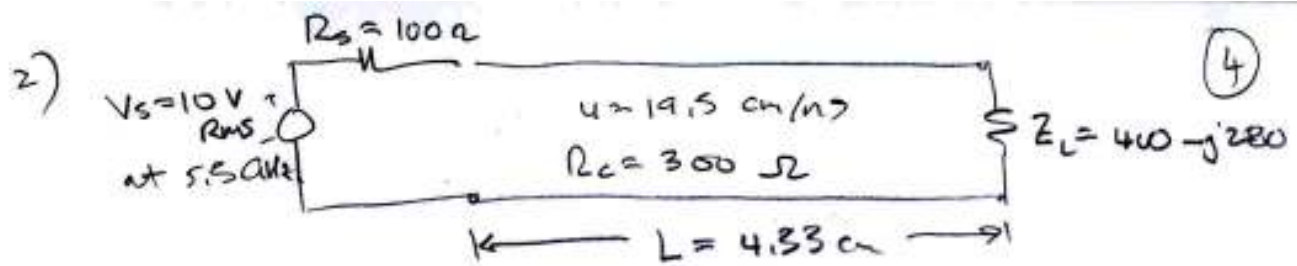114) V_L at 2.5 ns

$$V_L = (+8.57 + 3.90) + (-8.57 - 3.90) + (-2.78 - 1.27) = -4.05 \text{ volts}$$



2.1) $\beta = \frac{2\pi}{\lambda}$ where $\lambda = \frac{u}{f}$ $\therefore \beta = \frac{2\pi f}{u}$

$$= \frac{2\pi \times 5.5}{19.5}$$

$$= 1.772\text{ rad/cm} \quad (b)$$

2.2) $\tan \beta L = \tan 1.772 \times \frac{180}{\pi} \times 4.33 = 439.6^\circ$

$$\tan \beta L = 5.458$$

$$Z_m = Z_c \frac{Z_L + j Z_c \tan \beta L}{Z_c + j Z_L \tan \beta L}$$

$$= 300 \frac{(400 - j280) + j 300 \times 5.458}{300 + j (400 - j280) \times 5.458}$$

$$= 300 \frac{400 + j 1357.4}{300 + j 1828.2 + j 2183.2}$$

$$= 300 \frac{4415.1 \angle 73.6^\circ}{2847.6 \angle 50.0^\circ}$$


$$= 149.1 \angle 23.6^\circ$$

$$= 136.6 + j 59.7\ \Omega \quad (c)$$

$$= 136.6 + j 59.7\ \Omega$$

$$\frac{50}{1-1}$$

2.3)

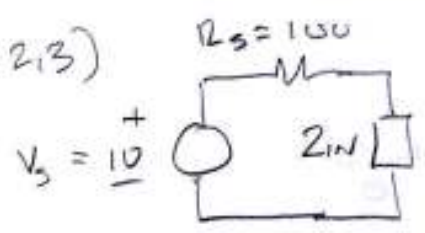

$$\begin{aligned}
 V(u) &= \frac{Z_{in} V_s}{Z_{in} + R_s} \\
 &= \frac{(1136.6 + j 59.7) \times 10}{1136.6 + j 59.7 + 100} \\
 &= \frac{(1491.4 \angle 23.6^\circ) \times 10}{1236.6 + j 59.7} \\
 &= \frac{1491.6 \angle 23.6^\circ}{244.0 \angle 14.2^\circ} \\
 &= 6.11 \angle 9.4^\circ \text{ (b)}
 \end{aligned}$$

2.4)

$$\begin{aligned}
 \Gamma_L &= \frac{Z_L - R_c}{Z_L + R_c} = \frac{400 - j 280 - 300}{400 - j 280 + 300} \\
 &= \frac{100 - j 280}{700 - j 280} = \frac{297.3 \angle -70.3}{753.9 \angle -21.8} \\
 &= 0.394 \angle -48.5 \\
 &= 0.261 - j 0.295 \text{ (d)}
 \end{aligned}$$

2.5)

$$\begin{aligned}
 V^+ &= \frac{V(u)}{1 + \Gamma_L e^{-2j\beta L}} \\
 \beta L &= 489.6 \quad \text{so } -2\beta L = -979.2^\circ \\
 1 + \Gamma_L e^{-2j\beta L} &= 1 + (0.394 \angle -48.5^\circ) (1 \angle -879.2^\circ) \\
 &= 1 + 0.394 \angle -927.7^\circ \\
 &= 1 + (-0.3488 + j 0.1831) \\
 &= 0.6512 + j 0.1831 = 0.6765 \angle 15.7^\circ
 \end{aligned}$$

$$V^+ = \frac{V(0)}{1 + \Gamma_L e^{-2j\beta L}}$$

(6)

$$= \frac{6.11 \angle 9.4^\circ}{0.6765 \angle 15.7^\circ} = 9.03 \angle -6.3^\circ = 8.98 - 0.99j$$

$$V^- = V^+ \Gamma_L e^{-2j\beta L}$$

$$= (9.03 \angle -6.3^\circ) (0.394 \angle -92.77^\circ)$$

$$= 3.58 \angle -93.4^\circ = -2.97 + 2.00j$$

$$V(z) = (9.03 \angle -6.3^\circ) e^{-j\beta z} + (3.58 \angle -93.4^\circ) e^{j\beta z}$$

$$V(L) = (9.03 \angle -6.3^\circ) e^{-j\beta L} + (3.58 \angle -93.4^\circ) e^{j\beta L}$$

$$e^{-j\beta L} = 1 \angle (-\beta L) = 1 \angle -439.6^\circ$$

$$V(L) = (9.03 \angle -6.3^\circ) (1 \angle -439.6^\circ) + (3.58 \angle -93.4^\circ) (1 \angle 439.6^\circ)$$

$$= 9.03 \angle -445.9^\circ + 3.58 \angle -494.4^\circ$$


$$= 0.6456 + 9.007j + (-12.505 - j2.558)$$

$$= -11.859 + j6.449$$

$$= 11.67 \angle 97.8^\circ$$

(b)


3

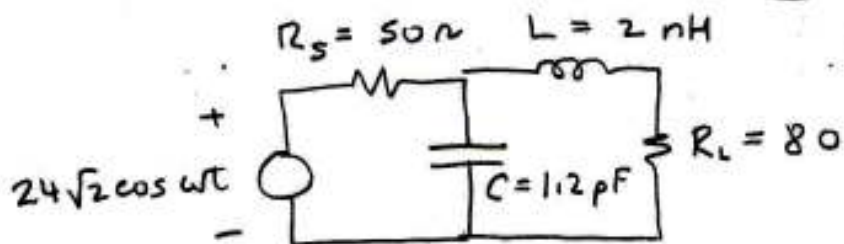


$$f = 2450 \text{ MHz} \Rightarrow \omega = 2\pi f = 1.539 \times 10^{10} \text{ rad/s}$$

$$3.1 \quad Z_L = j\omega L = j \cdot 1.539 \times 10^{10} \times 2 \times 10^{-9} = j 30.79 \quad \text{(b)}$$
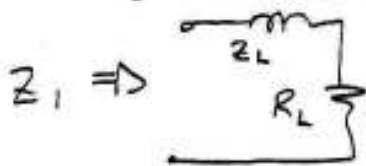
$$3.2 \quad Z_C = \frac{1}{j\omega C} = \frac{-j}{1.539 \times 10^{10} \times 1.2 \times 10^{-12}} = -j 54.15$$



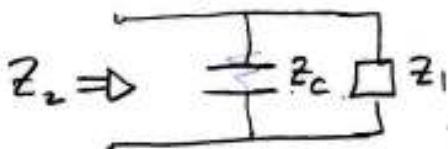
$$Z_1 = Z_L + R_L = 80 + j 30.79 \ \Omega$$



$$Z_2 = Z_1 \parallel Z_C = \frac{(80 + j 30.79)(-j 54.15)}{80 + j 30.79 - j 54.15}$$

$$= 33.77 - j 44.29 \ \Omega$$

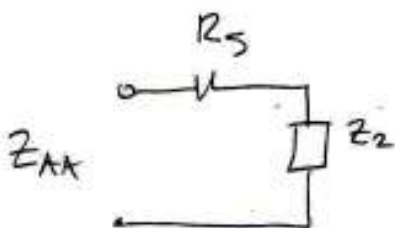


$$Z_{AA} = R_s + Z_2$$

$$= 50 + 33.77 - j 44.29$$

$$= 83.77 - j 44.29 \ \Omega \quad \text{(c)}$$


3.3

(6)

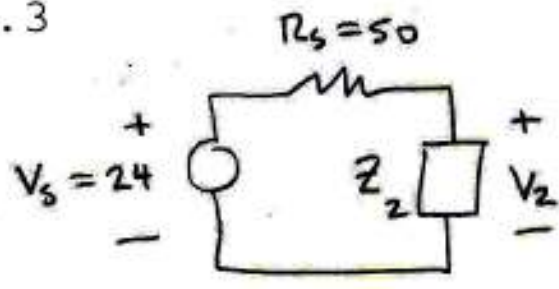

$$V_2 = \frac{Z_2 V_s}{Z_2 + R_s} = \frac{(33.77 - j44.29) \times 24}{33.77 - j44.29 + 50}$$

$$V_2 = 12.80 - j5.92$$

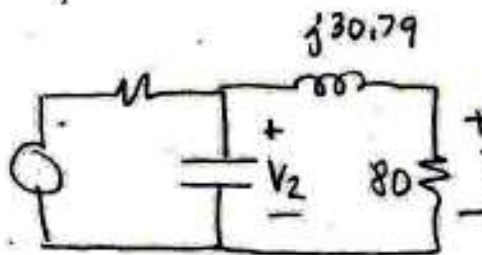

$$V_L = \frac{80 \times V_2}{80 + j30.79}$$

$$V_L = \frac{80 \times (12.80 - j5.92)}{80 + j30.79}$$

$$= 9.17 - j9.45$$

$$= 13.17 \angle -45.9^\circ$$

(a)