


February 16, 2011

Closed book exam! No books or notes allowed!

Cell phones and other wireless devices are forbidden in examinations. You are not permitted to have a cell phone in your possession, even if it is turned off.

You are permitted to use an ENCS-approved electronic calculator, either the Sharp EL 531 and the Casio FX-300 MS. No other calculator is permitted.

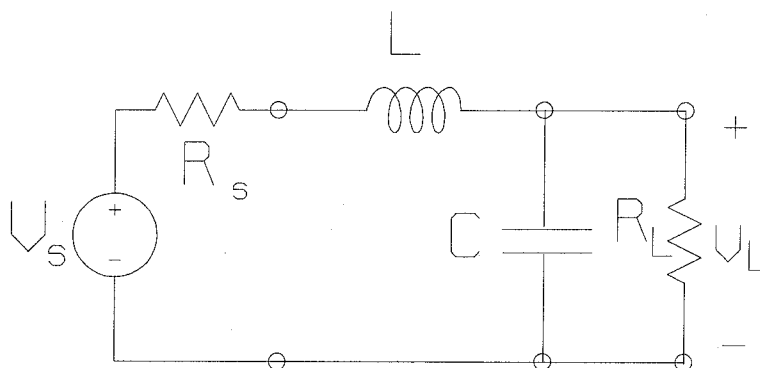**Circle the correct answer directly on the examination paper.** The exam booklet is for rough work. If your answer is within 3% of one of the given answers, then choose that answer.



1. The figure shows an equivalent circuit model for a transmission line, in which the line is represented with a series inductor  $L$  and a shunt capacitor  $C$ . The transmission line has inductance per unit length  $\ell = 0.429$  microHenries/meter and capacitance per unit length  $c = 80.6$  picoFarads/meter. The length of the line is 14 cm. The generator is sinusoidal with amplitude  $V_s = 10$  volts and frequency 2450 MHz. The internal resistance of the generator is  $R_s = 40 \Omega$ . The load resistance is  $R_L = 120 \Omega$ .

1.1) Find the inductance  $L$  for the equivalent circuit.

21.4 nH	60	42.9	429	none of these
---------	----	------	-----	---------------

1.2) Find the impedance of the capacitor at the operating frequency.


$-j5.76 \Omega$	$-j5.04$	$-j6.41$	$-j7.05$	none of these
-----------------	----------	----------	----------	---------------

1.3) Find the input impedance at the generator terminals.

$40.4 + j748 \Omega$	$40.3 + j919$	$40.2 + j10.51$	$40.3 + j823$	none of these
----------------------	---------------	-----------------	---------------	---------------

1.4) Find the voltage across the load.

47.8 mV	94.0	62.5	77.6	none of these
---------	------	------	------	---------------

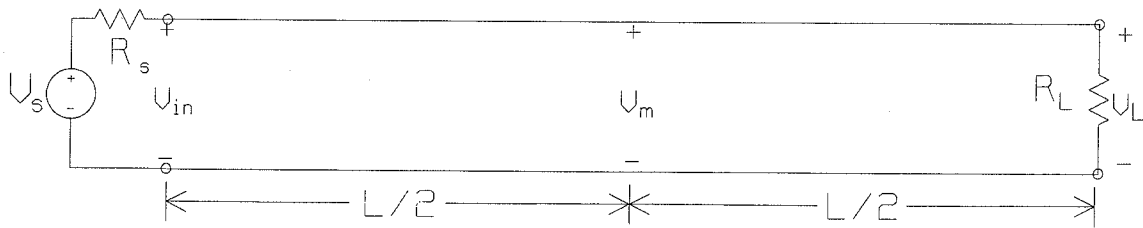

2.A transmission line has characteristic resistance 70 ohms and speed of travel 15 cm/ns. The length of the line is  $L=22$  cm. The generator produces a step function starting at  $t = 0$  of amplitude  $V_s = 5$  volts. The internal resistance of the generator is  $R_s=2 \Omega$ . The load resistance is  $R_L =125 \Omega$ .

2.1) Find the voltage  $V_m$  at the middle of the transmission line at  $t = 0.8$  ns.

4.38 V	4.86	2.19	4.12	none of these
--------	------	------	------	---------------

2.2) Find the voltage  $V_L$  at the load at  $t = 1.6$  ns.

3.42 V	1.03	6.23	6.84	none of these
--------	------	------	------	---------------

2.3) Find the voltage  $V_{in}$  at the generator terminals at  $t = 3.2$  ns.


3.02 V	4.98	5.42	4.14	none of these
--------	------	------	------	---------------

2.4) Find the voltage  $V_L$  at  $t = 4.8$  ns.

3.96 V	1.53	4.57	0.95	none of these
--------	------	------	------	---------------

2.5) Find the voltage at the load as  $t \rightarrow \infty$ .

2.00 V	2.50	4.09	4.89	none of these
--------	------	------	------	---------------

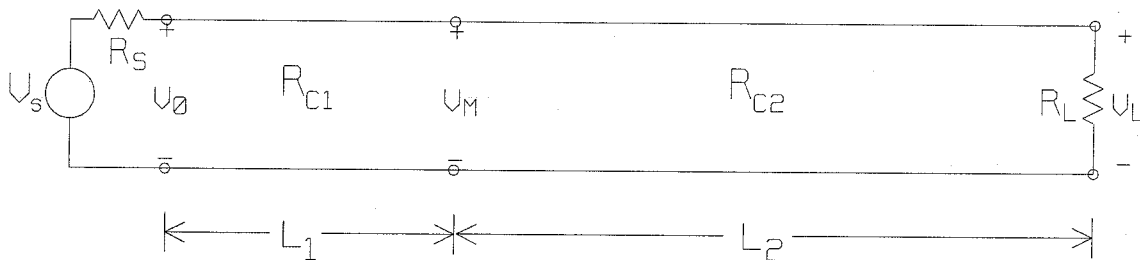

3.The transmission-line circuit shown above is driven by a step-function generator that switches on at  $t = 0$ , with  $V_s = 10$  volts and  $R_s = 5$  ohms. The two transmission lines have characteristic resistance  $R_{c1} = 200$  ohms and  $R_{c2} = 400$  ohms, and speed-of-travel  $u = 20$  cm/ns. Line #1 has length  $L_1 = 1$  cm and line #2 has  $L_2 = 4$  cm. The circuit is terminated by a load resistor of value  $R_L = 1000$  ohms.

3.1) Find the voltage  $V_0$  across the generator terminals at  $t = 0.05$  ns.

9.76 V	3.33	8.00	6.67	none of these
--------	------	------	------	---------------

3.2) Find the voltage  $V_M$  across the junction at  $t = 0.10$  ns.

4.44 V	8.89	13.0	10.7	none of these
--------	------	------	------	---------------

3.3) Find the voltage  $V_0$  at  $t = 0.12$  ns.

9.07 V	4.81	8.14	9.92	none of these
--------	------	------	------	---------------


3.4) Find the voltage  $V_M$  across the junction at  $t = 0.27$  ns.

8.01 V	10.2	8.96	4.99	none of these
--------	------	------	------	---------------

3.5) Find the voltage  $V_L$  across the load at  $t = 0.27$  ns.

18.6 V	15.2	12.7	6.34	none of these
--------	------	------	------	---------------

1.

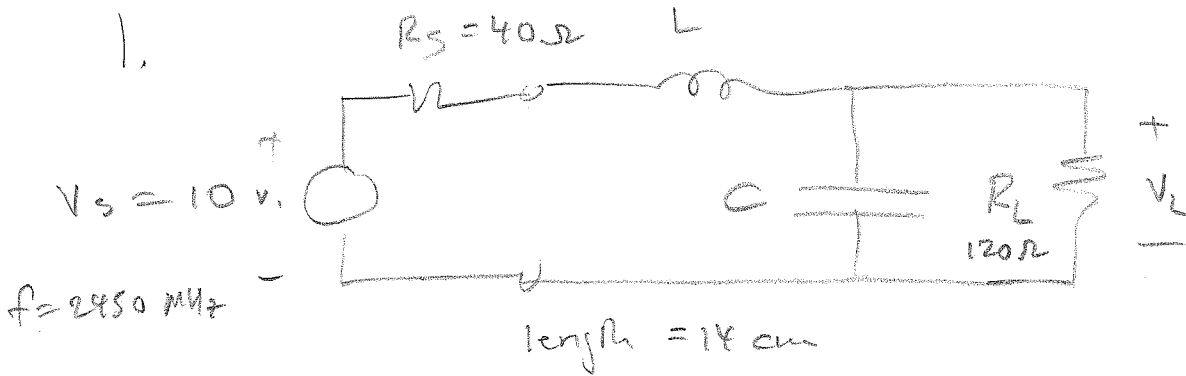

1.1)  $L = 0.429 \mu\text{H}/\text{m} = 4.29 \text{ nH}/\text{cm}$

$C = 80.6 \text{ pF}/\text{m}$

$L = 4.29 \text{ nH}/\text{cm} \times 14 \text{ cm} = 60.06 \text{ nH}$

$C = 80.6 \times 0.14 = 11.28 \text{ pF}$


1.2)  $Z_C = \frac{1}{j\omega C}$        $\omega = 2\pi \times 2450 \times 10^6 = 1.539 \times 10^{10}$

$= -j \frac{1}{1.539 \times 10^{10} \times 11.28 \times 10^{-12}}$

$= -j 5.760$

1.3)  $Z_L = j\omega L = j 1.539 \times 10^{10} \times 60.06 \times 10^{-9}$


$= j 924.3$

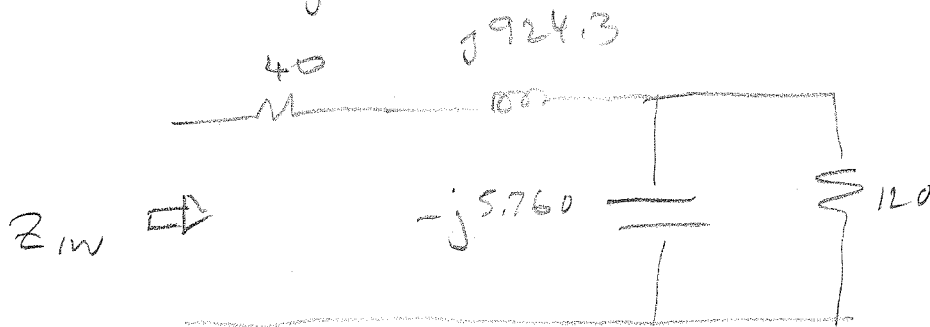


$$Z_p = -j5.760 \parallel 120 = \frac{120 \times (-j5.760)}{120 - j5.760} = 0.2758 - j5.746 \quad (2)$$

$$\begin{aligned} Z_{in} &= 40 + j924.3 + 0.2758 - j5.746 \\ &= 40.2758 + j918.6 \end{aligned}$$

1.4)

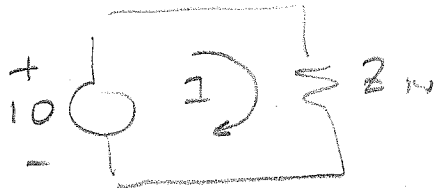

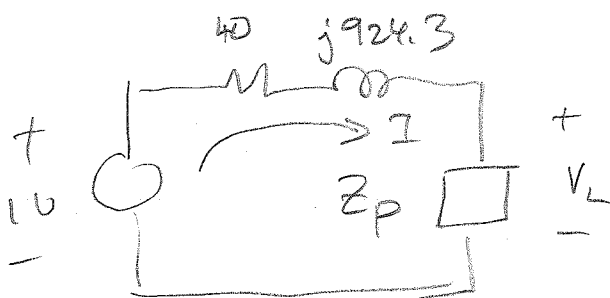
$$I = \frac{10}{Z_{in}} = 4.764 \times 10^{-4} - j0.01086$$



$$\begin{aligned} V_L &= Z_p I = (0.2758 - j5.746)(4.764 \times 10^{-4} - j0.01086) \\ &= -0.06227 - j5.733 \times 10^{-3} \\ &= 0.06253 \angle -174.7 \text{ volts} \end{aligned}$$

hence the amplitude is 62.5 mV.

2.

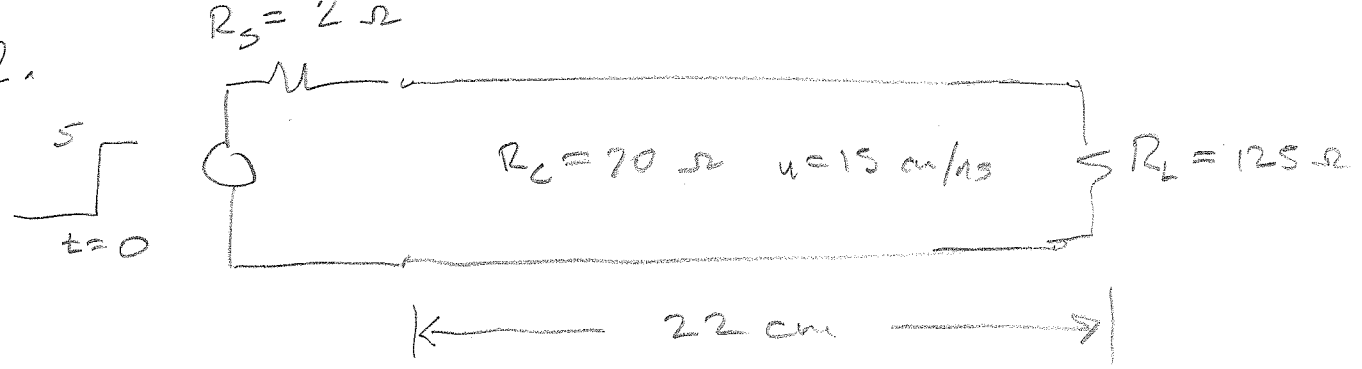


$$T = \frac{L}{u} = \frac{22}{15} = 1.47 \text{ ns}$$

$$V(0) = \frac{V_s \times R_c}{R_s + R_c} = \frac{5 \times 70}{2 + 70} = 4.861 \text{ V}$$

$$\Gamma_L = \frac{R_L - R_c}{R_L + R_c} = \frac{125 - 70}{125 + 70} = 0.2821$$
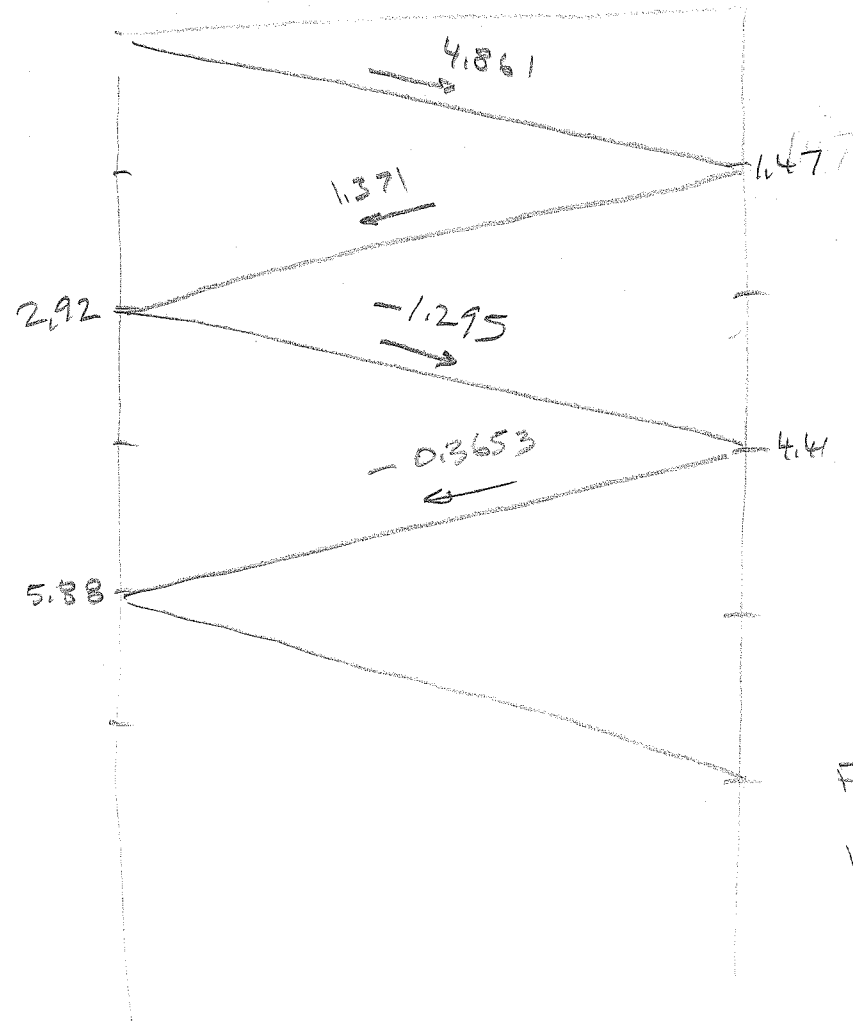
$$\Gamma_s = \frac{R_s - R_c}{R_s + R_c} = \frac{2 - 70}{2 + 70} = -0.9444$$



2.1)  $V_m @ 0.8 \text{ ns}$

$$V_m = 4.861 \text{ V}$$

2.2)  $V_L @ 1.6 \text{ ns}$

$$V_L = 4.861 + 1.371 = 6.232$$

2.3)  $V_m @ 3.2$


$$V_m = 4.861 + 1.371 - 1.295 = 4.937$$

2.4)  $V_L @ 4.8$

$$V_L = 6.232 - 1.295 - 0.3653 = 4.572$$

Final Value
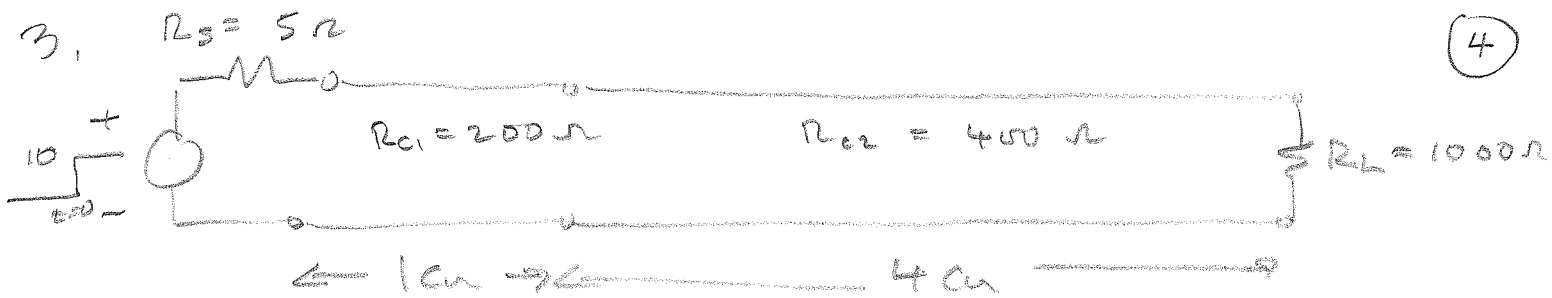
$$V_L = \frac{125 \times 5}{2 + 125} = 4.921 \text{ V}$$




$$u = 20 \text{ cm/ns} \quad T_1 = \frac{1}{20} = 0.05 \text{ ns} \quad T_2 = \frac{4}{20} = 0.20 \text{ ns}$$

$$V(0) = \frac{V_s R_{c1}}{R_s + R_{c1}} = \frac{10 \times 200}{5 + 200} = 9.756$$

$$\Gamma_s = \frac{R_s - R_{c1}}{R_s + R_{c1}} = \frac{5 - 200}{5 + 200} = \frac{-195}{205} = -0.9512$$
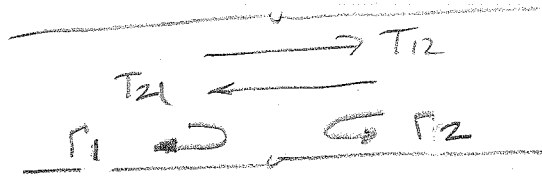
$$\Gamma_L = \frac{R_L - R_{c2}}{R_L + R_{c2}} = \frac{1000 - 400}{1000 + 400} = 0.4286$$



From the left


$$\Gamma_1 = \frac{R_{c2} - R_{c1}}{R_{c2} + R_{c1}} = \frac{400 - 200}{400 + 200} = 0.3333$$

$$T_{12} = \frac{2R_{c2}}{R_{c1} + R_{c2}} = \frac{2 \times 400}{400 + 200} = 1.333$$

From the right

$$\Gamma_2 = \frac{R_{c1} - R_{c2}}{R_{c1} + R_{c2}} = -0.3333$$
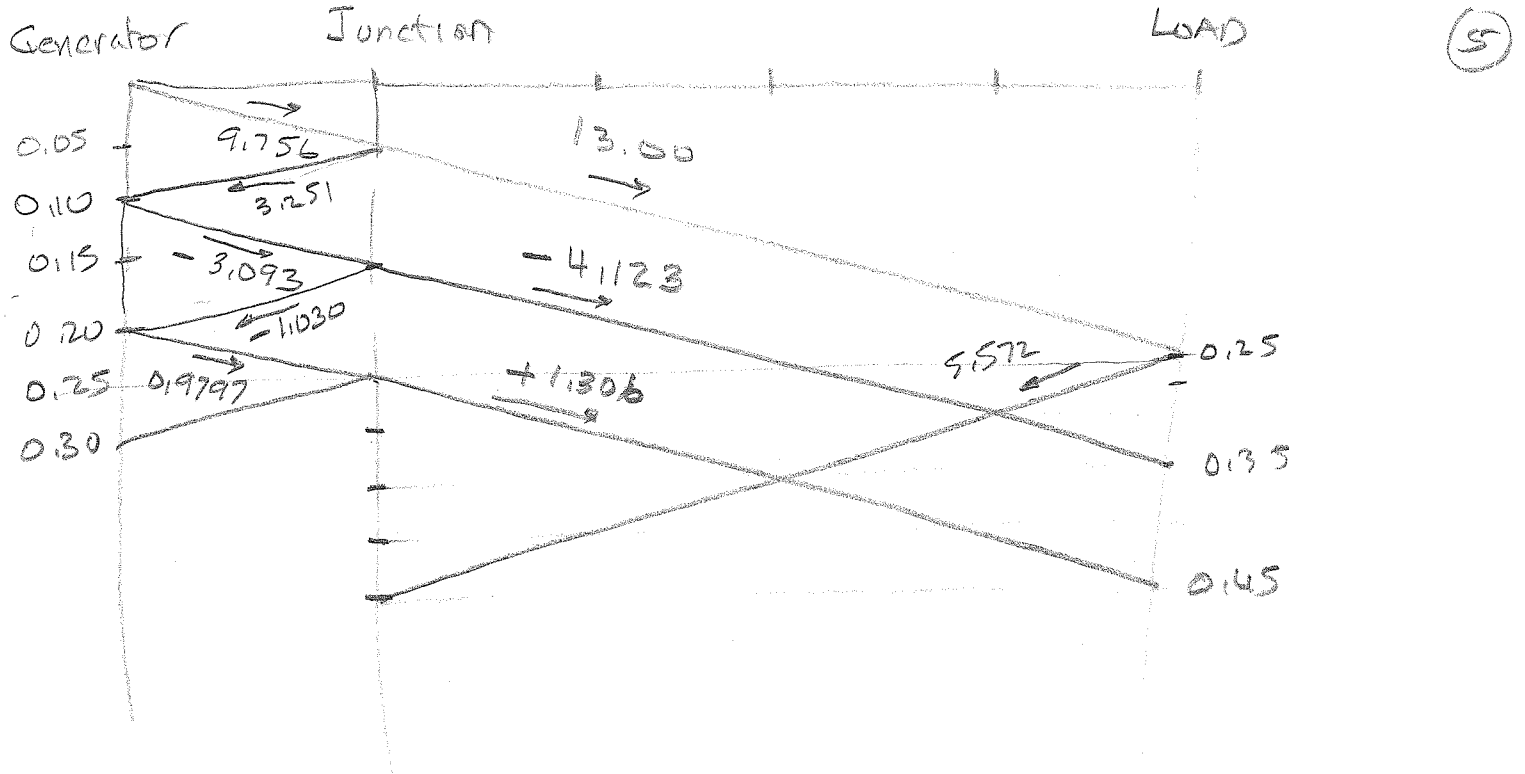
$$T_{21} = \frac{2R_{c1}}{R_{c1} + R_{c2}} = \frac{2 \times 200}{400 + 200} = 0.6667$$



3.1)  $V_s$  @  $t = 0.05$  ns  $V_s = 9.756$  v.

3.2)  $V_m$  @  $t = 0.10$  ns  $V_m = 13.00$  v

3.3)  $V_s$  @  $t = 0.12$  ns

$$V_s = 9.756 + 3.251 - 3.093 = 9.914$$

3.4)  $V_m$  @  $0.27$  ns

$$V_m = 13.00 - 4.123 + 1.306 = 10.18 \text{ v,}$$

3.5)  $V_L$  @  $0.27$  ns

$$V_L = 13.00 + 5.57 = 18.57 \text{ volts}$$